

N26F300  
VLSI SYSTEM DESIGN  
(GRADUATE LEVEL)

Fall 2010

Verilog (II)

# Outline

2

- Behavioral Models of Sequential Logics
  - ▣ Latches and Flip-flops
  - ▣ Procedural assignment
  - ▣ Non-blocking assignment
- Basic Finite State Machine
  - ▣ Moore and Mealy
  - ▣ State Diagram
  - ▣ EXM2 and EXM3
  - ▣ Controller FSM

3


# Behavioral Models of Sequential Logic

Latches and Flip-flops


Procedural assignment

Non-blocking assignment

# Latches

 


$S'$	$R'$	$Q_{\text{next}}$	$Q'_{\text{next}}$	
0	0	1	1	Not allowed
0	1	1	0	Set
1	0	0	1	Reset
1	1	$Q$	$Q'$	Hold

 


# Edge-Triggered D Flip-flop

5

 

$D$	$Q$	$Q_{next}$
0	0	0
0	1	0
1	0	1
1	1	1

 


# Differences between a latch and a flip-flop(1 / 2)

6

- A latch does not have a clock signal
- Latches does not need synchronized with the clock, i.e., they are asynchronous.
  - the output changes soon after the input changes
- A flip-flop is a synchronous version of the latch
- Most of the digital designs today are synchronous

# Differences between a latch and a flip-flop (2/2)

7

 

# Behavioral DFF

8

```
module df_behav (q, q_bar, data, set, reset, clk);  
input          data, set, clk, reset;  
output         q, q_bar;  
reg            q;  
  
assign q_bar = ~ q;  
  
always @ (posedge clk) // Flip-flop with synchronous set/reset  
begin  
    if (reset == 0) q <= 0;  
    else if (set == 0) q <= 1;  
    else q <= data;  
end  
endmodule
```



# Procedural Blocks

9

- Procedural blocks are the basis for behavioral modeling
- Procedural blocks are of two types
  - 
  -
- Procedural blocks have the following components
  - **Procedural assignment statements**
  - **Timing controls**
  - **High-level programming language constructs.**

initial		c
C	-----	
C	-----	
C	-----	
C	-----	
C	-----	

always		c
C	-----	
C	-----	
C	-----	
C	-----	
C	-----	

# Coding Notes

10

## □ Edge-sensitive behavior



- Use procedural statements, statements of an ordinary procedural language (e.g., C)

## □ Procedural assignment operator

- operator(=)



- Register variables store information during simulation, NOT necessary implying hardware registers

# Procedural assignment

11

- **Blocked assignment**
- **=** is the assignment operator. It copies the value of the RHS of the expression to the LHS.
- A statement must complete execution before the next statement in the behavior can execute

# Nonblocking (concurrent) assignment

12

- **Operator(<=)**
- Statements will be execute **concurrently** (in parallel), NOT sequentially. So the order in which they are listed has no effect.

```
module swap_vals;
    reg a, b, c;
    initial
    begin
        a = 0;
        b = 1;
        c = 0;

    end
    always #5 c = ~c;
    always @(posedge c)
    begin
        a <= b; //Nonblocking procedural assignment
        b <= a; //swaps the values of a and b.


    end
endmodule
```

# Blocking and Non-Blocking Assignments

13

 
## Blocking

```
always @(posedge clk)
begin
    b = a;
    c = b;
end
```


 
## Non-blocking

```
always @(posedge clock)
begin
    b <= a;
    c <= b;
end
```



# Register File (1 / 2)

14

```
`timescale 1ns/10ps
module Mreg_4for32(OUT_1, OUT_2, Write, Read, Read_ADDR_1,
Read_ADDR_2, Write_ADDR, DIN, enable, clk, rst);
```

```
parameter ASize = 13;           //13 bits
parameter REGSize = 32;         //32
parameter DSize = 32;           //32bits
```

```
input clk;
input rst;
input enable;
```

```
input [ASize-1:0]Read_ADDR_1;
input [ASize-1:0]Read_ADDR_2;
input [ASize-1:0]Write_ADDR;
```

```
input [DSize-1:0]DIN;
```


```
input      Write;
input      Read;
```

```
output [DSize-1:0]OUT_1;
output [DSize-1:0]OUT_2;
```

```
reg [DSize-1:0]OUT_1;
reg [DSize-1:0]OUT_2;
```

```
reg [DSize-1:0] Mreg[REGSize-1:0];
```

```
integer i;
```

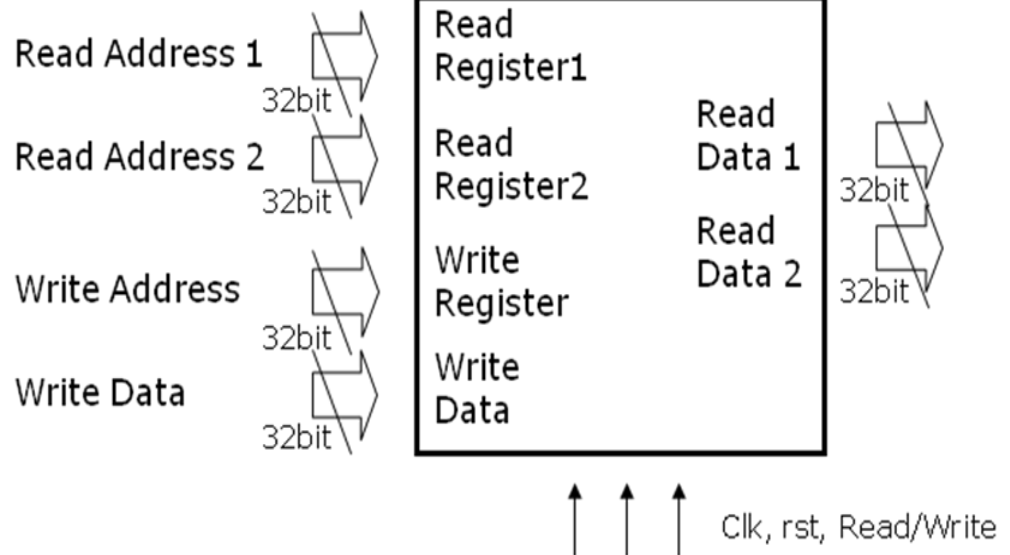

# Register File (2/2)

15

```
always@(posedge clk)begin
    if( rst )begin
        for(i=0 ; i<REGSize ; i=i+1)
            Mreg[i] = 0;
        end

    else
        begin
            if(enable)begin
                if( Write )
                    Mreg[Write_ADDR] = DIN;
                else if( Read )begin
                    OUT_1 = Mreg[Read_ADDR_1];
                    OUT_2 = Mreg[Read_ADDR_2];
                end
            end
        end
    end
end

endmodule
```

# Parallel and Serial Statements

16

## □ Continuous assignment statements

```
assign A_lt_B = (A < B);  
assign A_gt_B = (A > B);  
assign A_eq_B = (A == B);
```



## □ Procedural block

```
always @ (reset or enable or data)  
begin  
    if(reset) q_out = 0;  
    else if (enable)  
        q_out = data;  
end
```





# Parallel and Serial Statements

17

- Mixed continuous, procedural, gate-level

```
assign mux_out = enable ? mux_int : 32'bz;  
always @ (data_3 or data_2 or data_1 or data_0 or select)  
begin  
    .....  
end  
  
xor      mxor (mux_int, a1, b1);  
add_full mfadd (a1, c_in, y, z);
```

18

# Basic Finite State Machine

Moore and Mealy


Controller FSM

Read Memory


# Moore and Mealy Machines

19

- **Moore model**

 


- **Mealy model**

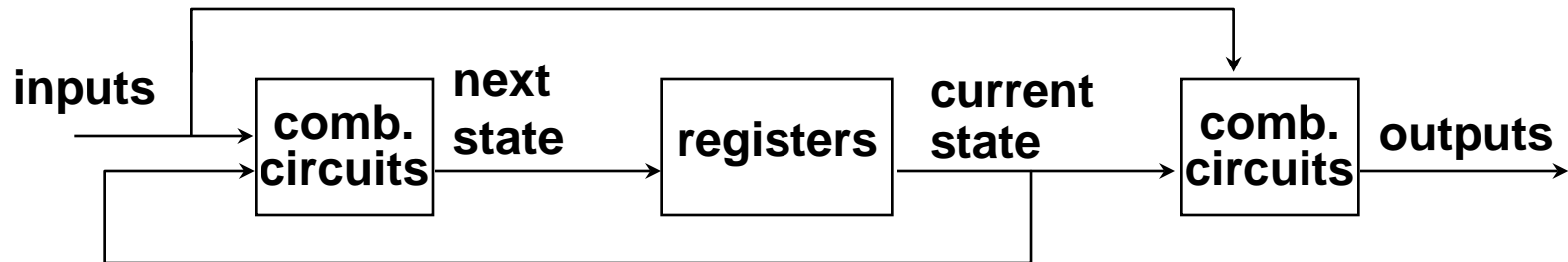

# Moore Machine

20

 

Current State	Next State		Qout
	Din=0	Din=1	
S0=00			0
S1=01			1
S2=10			1
S3=11	-	-	0

- Use binary numbers to represent each state  
parameter [1:0] S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11;
- Reading data input and changes state for every clock cycles
- Upon reset, machine goes back to state S0
- Next state will be determined by current state and input

# Verilog Code (1 / 3)

21

```
`timescale 1ns/10ps
module moore (Qout, clk, rst, Din);
output Qout;
input clk, rst, Din;
parameter [1:0] S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11;
reg Qout;
reg [1:0] CS, NS; // CS: current state; NS: next state

always @ (posedge clk or posedge rst)
begin
if (rst==1'b1) CS=S0;
else CS = NS;
end
```

# Verilog Code (2/3)

22

```
always @ (CS or Din)
begin
case (CS)
  S0: begin
      Qout=1'b0;
      if (Din==1'b0) NS=S0;
      else NS = S2;
    end
  S1: begin
      Qout=1'b1;
      if (Din==1'b0) NS=S0;
      else NS = S2;
    end
end
```

# Verilog Code (3/3)


23

```
S2: begin
    // fill the rest of the code
end
S3: begin
    // fill the rest of the code
end
endcase
end // always(cs or din)
endmodule
```
 
# Mealy Machine

24

Construct the state diagram and state table as below:



Current State	Next State	
	Din=0	Din=1
S0=00	S0,0	S1,0
S1=01	S2,0	S1,0
S2=11	S0,0	S1,1




# Reference Code

25

```
always@(CS or Din)
begin
    case (CS)
        s0: begin
            if (Din==1'b0)
            begin
                NS=s0;
                Qout=1'b0;
            end
            else begin
                NS = s1;
                Qout=1'b0;
            end
            end
        s1:begin
            ... //complete the rest of the code
            end
        s2:begin
            ... //complete the rest of the code
            end
        default:
            begin
                ...
            end
    endcase
end
endmodule
```

# Controller FSM (1 / 3)

26

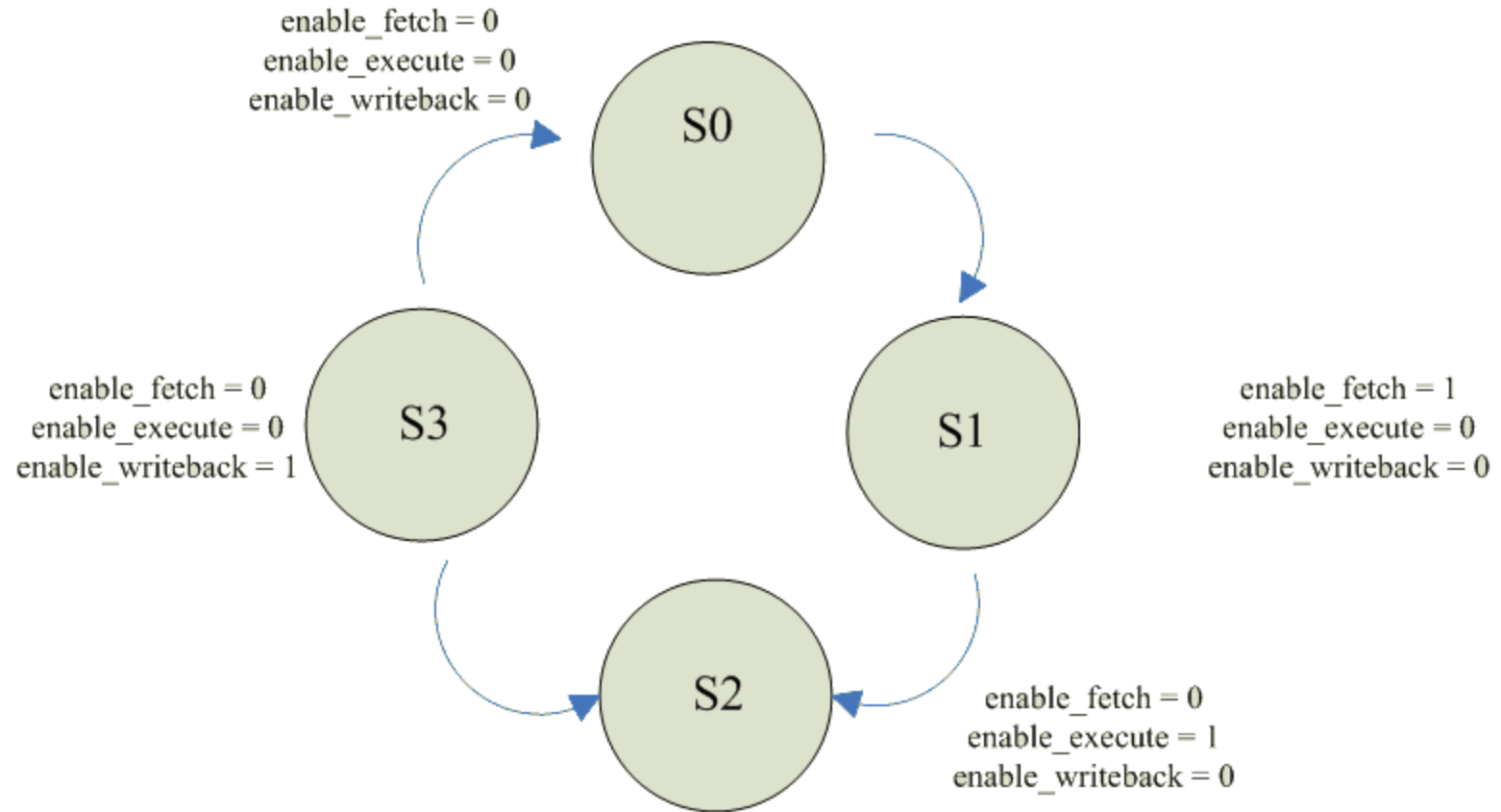

# Controller FSM (2/3)

27

```
module ctrl_state(clk, reset, enable_fetch,
enable_execute, enable_writeback, ir, PC_adjust, pc);
`define OPCODE ir[31:28]
`define SRCTYPE ir[27] //1= imm; 0 = reg
`define DSTTYPE ir[26] //1 = Data Mem; 0 = reg
`define SRC ir[25:13]
`define DST ir[12:0]
input [31:0] ir;
input [4:0] pc;
input clk,reset;
output enable_fetch, enable_execute;
output enable_writeback, PC_adjust;
reg enable_fetch, enable_execute;
reg enable_writeback, PC_adjust;
reg [1:0] current_state, next_state;
reg [31:0] pre_opcode;

parameter S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11;

always @(posedge clk)
begin
    if(reset) begin
        current_state= S0;
    end
    else begin
        current_state=next_state;
    end
end
end
```

# Controller FSM (3/3)

28

```
always @(current_state)
begin
  case(current_state)
    2'b00: begin
      next_t_state= S1;
      enable_fetch= 0;
      enable_execute= 0;
      enable_writeback= 0;
    end
    .
    .
    .
    default: next_t_state= S0; //avoid unknown state
  endcase
end

always @(posedge enable_fetch)
begin
  if(pc== 0) pre_opcode= 0;
  else pre_opcode= ir;
end
```

# Loading a Memory Array

29

- Assigning values to each word of the memory array.
- Call to **\$readmem** system task to initialize memory from file

**MUST**

**\$readmem**<base>(" "<filename>",<mem\_name>,<start>,<finish>);

**optional**

```
parameter memsize = 256;
reg [7:0] mema [memsize-1:0];
...
initial
    for (i = 0; i < memsize; i = i + 1)
        mema[i] = 8'b0;
...

initial
    $readmemb("mem_file.txt", mema);
    ....
```

# \$readmemb and &readmemb

30

□ \$readmemb("mem\_file.txt",mem);


UNIX Text File

mem\_file.txt

```
0000_0000
0110_0001 0011_0010
//addresses 3-255 are not
//defined
@100
1111_1100
/*addresses 257-1022 are
not defined */
@3FF
1110_0010
```

Declared Memory Array

reg[0:7] mem [1023:0]

 

# Memory Addressing

31

- A memory element is addressed by giving the location to the memory array.

```
reg [8:1] mema [0:255]; //declare memory called mema
reg [8:1] mem_word; // temp register called mem_word
...
// Display contents of the 6th memory address
$displayb(mema[5]);
...
//Display the msb of the 6th memory word
mem_word = mema[5];
$displayb(mem_word[8]);
...
```

**// It is incorrect to use mema[5][8];**

# Memory

32

```
module memory(data,addr,read,write);  
input read,write;  
input [4:0] addr;  
inout [7:0] data;  
reg [7:0] data_reg;  
reg [7:0] memory [0:8'hff];  
parameter load_file = "cput1.txt";  
assign data=(read)?memory [addr]:8'hz;  
always @(posedge write)  
    memory[addr]=data;  
initial  
    $readmemb(load_file,memory);  
endmodule
```



# Reading in Verification Vector Files

33

```
module test;
  parameter N = 5;
  ....
  reg [7:0] mult1 [0:N], m1;
  reg [7:0] mult2 [0:N], m2;
  reg [15:0] prod [0:N];
  wire [15:0] p;
  ....
  init begin
    $readmemh("s1_vec.dat", mult1);
    $readmemh("s2_vec.dat", mult2);
    $readmemh("prod_vec.dat", prod);
  end
  init begin
    reset = 1, clock = 0, load = 0;
```

```
    for (i=0;i<=N;i=i+1) begin
      m1 = mult1[i];
      m2 = mult2[i];
      #10 load = 1;
      #10 load = 0;
      #120 if (p!=prod[i])
        $display("Error! @ %i\n", i);
      end
      $finish;
    end
    always #5 clock = ~ clock;

    PSMult u1 (clock, reset, load, m1,m2,p);
  endmodule
```

# s\_vec.dat

34

**// vector inputs**

**73hf**

**beef**

**1234**

**5678**

**9ABC**

**BEF0**

**FFFF**

**0000**

**7923**

**8943**

# Looping Statements

35

- For Loops (within procedural blocks or generate blocks)

```
for (index = 0; index < size; index = index + 1)  
    if (val[index] === 1'bx)  
        $display ("found an X");
```

```
for (i = 10; i > index; i = i - 1)  
    memory[i] = 0;
```

-- repeat (num\_Of\_execution) begin ...; ...; ...;...; end

-- while (control\_expression) begin ...; ...; ...;...; end

# For Loop

36

- Provide a shorthand way of writing a series of statements
- Loop index variable must be integer type
- Step, start & end value must be constant
- In synthesis, for-loop loops are “unrolled”, and then synthesized

```
always @(a or b) begin
  for (k = 0; k <= 3; k = k + 1)
    begin
      out[k] = a[k] ^ b[k];
      c = (a[k] | b[k]) & c;
    end
end
```

```
out[0] = a[0] ^ b[0];
out[1] = a[1] ^ b[1];
out[2] = a[2] ^ b[2];
out[3] = a[3] ^ b[3];
c = (a[0] | b[0]) & (a[1] | b[1]) &
    (a[2] | b[2]) & (a[3] | b[3]) & c
```