 


Lab 1

CPU Architecture, ALU, Register Files

Fall 2008



低功率高效能VLSI設計實驗室

NCKU, Low power, high performance VLSI design lab


Lab Overview

- Target Design
 - A datapath consisting of ALU and register file
- This ppt first reviews the architecture for SMILE CPU. An data_flow.pps file is given for you to observe the behavior of the architecture.
- Instruction set is then defined for SMILE
- Major components like ALU and register file are explained and described.
- Detailed description for each step are in Lab1_handout.



Outline

 - CPU Architecture
- Instruction Format
- Arithmetic Logic Unit
- Register File
- Reference Codes



CPU Architecture (1/4)

- Central Processor Unit (CPU) – An active part in the computer which adds numbers, tests numbers, signal I/O devices to activate, and so on....
- CPU architecture is a high level description of the hardware to implement the CPU
- 3 different architectures:
 - Single cycle CPU
 - – An instruction is executed in one clock cycle
 - Multicycle CPU
 - – An instruction is executed in multiple clock cycles
 - Superscalar CPU
 - – An advance pipelining CPU architecture that execute more than one instruction per clock cycle




CPU Architecture (2/4)

- CPU consists of three main blocks:
 - Datapath – The component that performs arithmetic and logical operations, e.g. ALU
 - Controller – The component that commands the datapath, memory, and I/O devices according to the instructions of the program
 - Memory – A storage area in which programs and data are stored, e.g. Register Files, Instruction Memory...
- **In this homework1, a Multicycle CPU will be designed and synthesized**




CPU Architecture (3/4)

Overall CPU Architecture

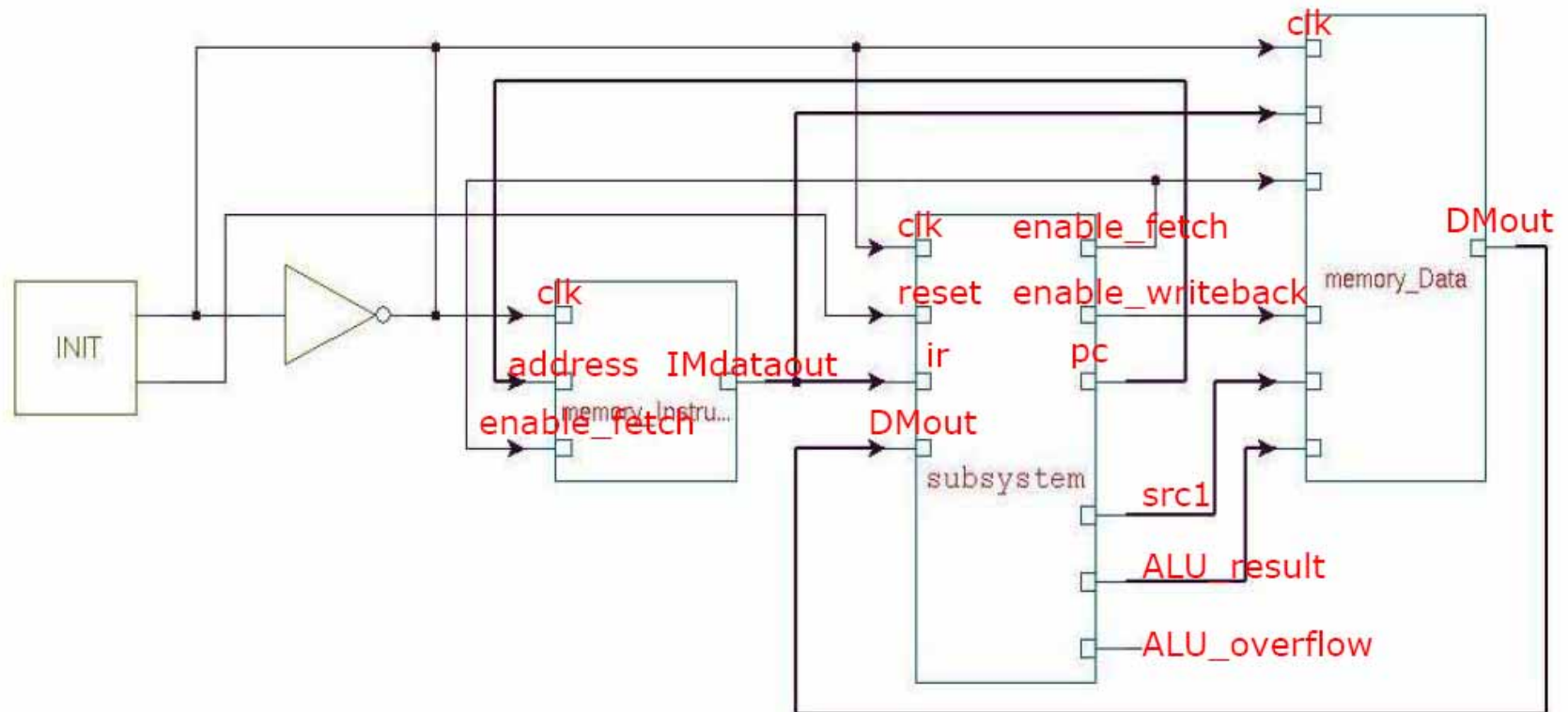

CPU Architecture (4/4)

Subsystem Block Diagram

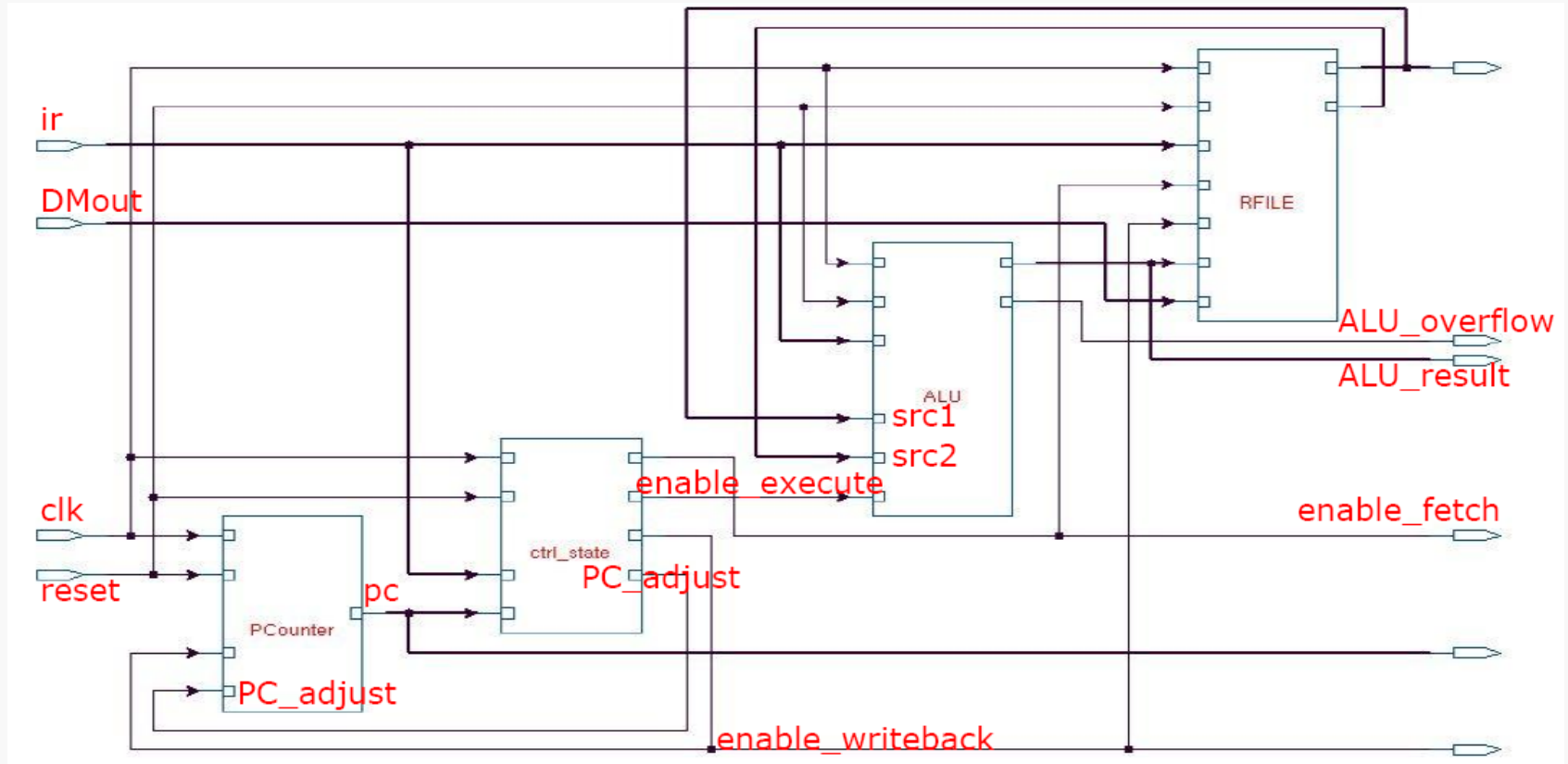


For animation of SMILE CPU, please open [data_flow.pps](#).



Instruction Format (1/5)

 - Instruction range:
 - `define OPCODE ir[31:28]
 - `define SRCTYPE ir[27]
 - `define DSTTYPE ir[26]
 - `define SRC ir[25:13]
 - `define DST ir[12:0]



- SRC Types: 1: Immediate value, 0: Register File type
- DST Types: 1: Data Memory type, 0: Register File type,




Instruction Format (2/5)

Opcode [31:28]	Mnemonics	SRC [25:13]	DST [12:0]	Description
0000	NOP	00000	00000	No operation
0001	LD	\$rs	\$rd	$rd = \text{imm or mem}[rs]$
0010	SW	\$rs	\$rd	$\text{mem}[rd] = rs \text{ or } \text{imm}$
0011	ADD	\$rs	\$rd	$rd = rs + rd$
0100	SUB	\$rs	\$rd	$rd = rd - rs$
0101	AND	\$rs	\$rd	$rd = rs \& rd$
0110	OR	\$rs	\$rd	$rd = rs \parallel rd$
0111	XOR	\$rs	\$rd	$rd = rs \wedge rd$
1000	SLL	imm	\$rd	Shift Left: $rd = rd \ll \text{imm}$
1001	SRL	imm	\$rd	Shift Right: $rd = rd \gg \text{imm}$
1010	RLL	imm	\$rd	Rotate Left: $rd = rd \ll \text{imm}$
1011	RRL	imm	\$rd	Rotate Right: $rd = rd \gg \text{imm}$



Instruction Format (3/5)

Example

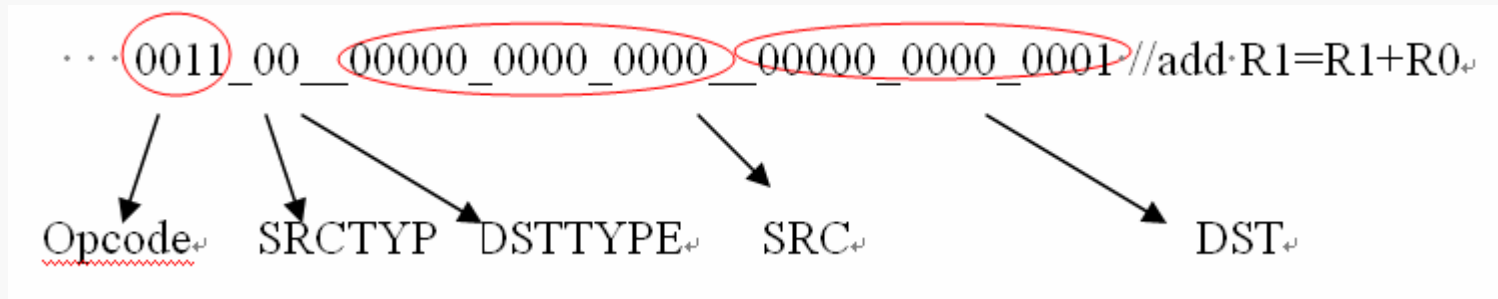

- 0011_10_00000_0000_1101_00000_0000_0000 //add R0=R0+13
- 0001_10_00000_0000_0111_00000_0000_0000 //LD R0<=7
- 0001_00_00000_0000_0000_00000_0000_0010 //LD R2<=M0
- 0010_00_00000_0000_0000_00000_0000_0000 //SW M0<=R0
- 0010_10_00000_1111_1111_00000_0000_0001 //SW M1<=2'hff



Instruction Format (4/5)

- Instruction Decoder – A datapath unit that will decode the an instruction by generating the corresponding fields to be used by the controller to carry out the corresponding operations

```
`define OPCODE ir[31:28]
`define SRCTYPE ir[27]
`define DSTTYPE ir[26]
`define SRC ir[25:13]
`define DST ir[12:0]
```

- Shift Operation
 - data “0” will replace the shifted position
- Rotate Operation
 - data is rotated from one end to the other end



Instruction Format (5/5)

LD – Loading data to Register File

– `DSTTYPE = 0

0001_10__00000_0001_0101__00000_0000_0000 //LD R0 21

0001_00__00000_0000_0001__00000_0000_0001 //LD R1 <= M1

If(`SRCTYPE==1) RFILE_array[`DST]=`SRC;
else RFILE_array[`DST]=the value from Data Memory

SW – Store a word to Data Memory

– `DSTTYPE = 1


0010_01__00000_0000_0000__00000_0000_0000 //SW M0=R0

0010_11__00000_1111_1111__00000_0000_0001 //SW M1=2'hff

If(`SRCTYPE==1) mem_data[`DST]=`SRC;
else mem_data[`DST]=the value from RFILEIn



Arithmetic Logic Unit (1/3)

 

- Combinational circuit performs a set of basic operation using two inputs to generate the result



Arithmetic Logic Unit (2/3)

- ALU unit will read the data from SCR1 & SCR2 and perform the designated operation
- Output contains the ALU_Result and ALU_Overflow
- *opcode* will be used to select which operation to be executed
- Control line signals to control ALU operation
- Consists of three different combinational circuit building blocks:
 - Add/Sub to perform addition and subtraction arithmetic operations
 - Logic block to perform logical operations
 - Barrel Shifter to perform shift and rotate operations



Arithmetic Logic Unit (3/3)

- Add/Sub block:

```
assign result=(control == 0)?(operand2+operand1):(operand2-operand1);
```

- Logic block

```
and_result=src2&src1;  
or_result=src2|src1;  
xor_result=src2^src1;
```

- Shift block

- Rotate Operation:


```
output [31:0] result; // result operand  
reg [95:0] rotate_reg;  
rotate_reg=(direction)?rotate_reg>>in1:rotate_reg<<in1;  
result=rotate_reg[63:32];
```

- Shift Operation:

```
result=(direction)?in2>>in1:in2<<in1;
```



Register File (1/3)

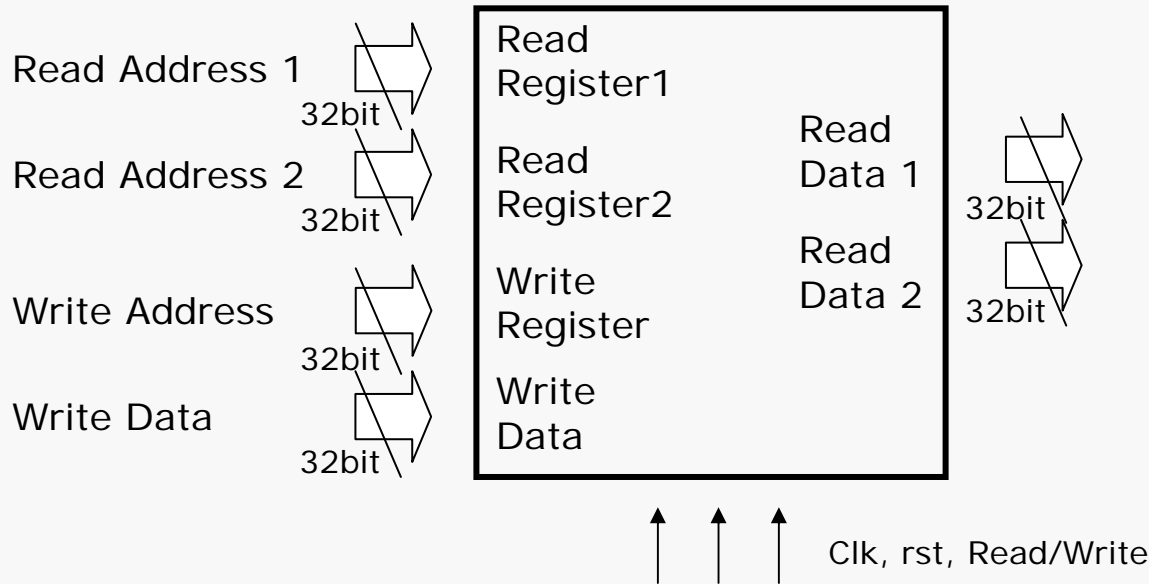

- Special type of fast memory that permits one or more words to be read and one or more words to be written simultaneously
- For this CPU design, consists of 32 registers:
 - Two Read Ports and two data output ports (for source register and destination register)
 - One Write Port and one Write Data Port




Register File (2/3)

- Working at positive edge of clock
- When reset, data values in all registers are reset to zero
- When enable is high and write is asserted, the write_data is stored into the register as pointed by write_address
- When enable is high and read is asserted, the data that are stored in registers as pointed by read_address1 & read_address2 are written to src1 & src2



Register File (3/3)

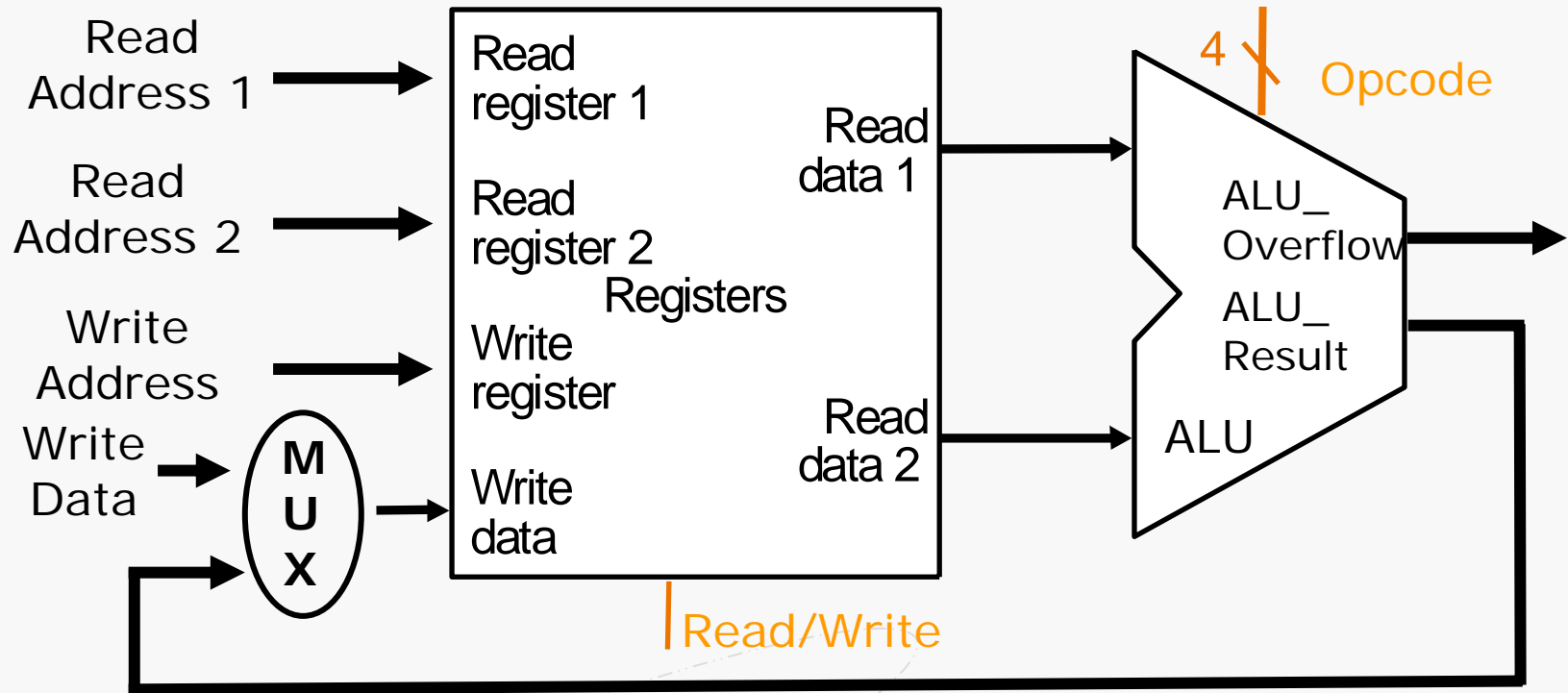

- Combining a Register File and an ALU unit to form a subsystem that could carry out the basic operation of a CPU



Reference Code 1 (ALU)

```
module ALU (opcode, src1, src2, enable_execute, alu_result, alu_overflow);
input  enable_execute;
input  [31:0] src1, src2;
Input  [3:0] opcode;
output [31:0] alu_result;
output alu_overflow;
reg    alu_overflow;
reg    [31:0] alu_result;
wire   [32:0] addsub_result;
wire   [31:0] shf_result;
wire   [31:0] and_result=src2&src1;
wire   [31:0] or_result=src2|src1;
wire   [31:0] xor_result=src2^src1;
wire   add_control=(`OPCODE==`ADD)?1'b0:1'b1;
wire   shf_type=(`OPCODE==`SLL || `OPCODE==`SRL)?1'b0:1'b1;
wire   shf_dir=(`OPCODE==`SLL || `OPCODE==`RLL)?1'b0:1'b1;
add_sub ADDSUB(src1, src2, addsub_result, add_control);
barrel_shifter SHT_ROT(src1, src2, shf_dir, shf_type, shf_result);
...
always @(opcode or enable_execute)
begin
    if(enable_execute)
    begin
        case(`OPCODE)
        `ADD: begin {alu_overflow, alu_result}=addsub_result;
            end
        `SUB: begin {alu_overflow, alu_result}=addsub_result;
            end
        ... (Please add-in your own codes)
        default:{alu_overflow, alu_result}=0;
        endcase
    end
end
```

```
//adder and substator
module add_sub (operand1,operand2,result,control);
input  [31:0] operand1,operand2;
input  control;
output [32:0] result;
wire   [32:0] result;

assign result=(control == 0)?(operand2+operand1):(operand2-operand1);
endmodule

//Barrel_shifter
module barrel_shifter (in1,in2,direction,type,result);
input  [31:0] in1,in2;// input operand
input  direction;    // left or right
input  type;         // shift or rotate
output [31:0] result; // result operand

reg    [31:0] result; // shift/rotate result
reg    [95:0] rotate_reg;

always @(in1 or in2 or direction or type)
begin
    rotate_reg={in2,in2,in2};
    if(type) begin
        rotate_reg=(direction)?rotate_reg>>in1:rotate_reg<<in1;
        result=rotate_reg[63:32];
    end
    else begin
        result=(direction)?in2>>in1:in2<<in1;
    end
end
endmoduleArithmetic Logic Unit
```



Reference Code 2 (ALU)

```
`timescale 1ns/10ps
module ALU( OverFlow, OUT, in_a, in_b, OP, enable);
parameter ISize = 32;
parameter OSize = 4; //2^3>6
input      enable;
input      [ISize-1:0] in_a;
input      [ISize-1:0] in_b;
input      [OSize-1:0] OP;
output     [ISize-1:0] OUT;           //33bits
output     OverFlow;
reg        [ISize-1:0] OUT;
reg        [2*ISize-1:0] temp;
reg        OverFlow;
```

```
always@(OP or enable)begin
```

```
    OverFlow = 0;
```

```
    if(enable)begin
```

```
        case(OP)
```

```
            4'b0000 :    OUT = OUT;           //NOP
```

```
            4'b0001 :    OUT = in_a;          //load
```

```
            4'b0010 :    OUT = in_a;          //store
```

```
            4'b0011 :    begin
                            OUT = in_a + in_b;    //ADD
```

```
                            if( -(2^31-1)<= OUT <=2^31-1)
```

```
                                OverFlow =0;
```

```
                            else
```

```
                                OverFlow =1;
```

```
                            end
```

```
            4'b0100 : begin
```

```
                OUT = in_a - in_b;           //SUB
```

```
                if( -(2^31-1)<= OUT <=2^31-1)
```

```
                    OverFlow =0;
```

```
                else
```

```
                    OverFlow =1;
```

```
                end
```

```
            4'b0101 :    OUT = in_a & in_b;    //AND
```

```
            4'b0110 :    OUT = in_a | in_b;    //OR
```

```
            4'b0111 :    OUT = in_a ^ in_b;    //XOR
```

```
            4'b1000 :    OUT = in_b<<in_a;     //left shift
```

```
            4'b1001 :    OUT = in_b>>in_a;     //right shift
```

```
            4'b1011 : begin
```

```
                //<<??rotate right 1 bit
```

```
                temp = {in_b,in_b};
```

```
                temp = temp>>in_a;
```

```
                OUT = {temp[31:0]};
```

```
            end
```

```
            4'b1010 : begin
```

```
                //<<??rotate left 1 bit
```

```
                temp = {in_b,in_b};
```

```
                temp = temp<<in_a;
```

```
                OUT = {temp[63:32]};
```

```
            end
```

```
        endcase
```

```
    end
```

```
end
```

```
endmodule
```



Reference Code 3 (Register File)

```
`timescale 1ns/10ps
module Mreg_4for32(OUT_1, OUT_2, Write, Read, Read_ADDR_1,
Read_ADDR_2, Write_ADDR, DIN, enable, clk, rst);
```

```
parameter ADSize = 13;           //13 bits
parameter REGSize = 32;          //32
parameter DASize = 32;           //32bits
```

```
input clk;
input rst;
input enable;
```

```
input [ADSize-1:0]Read_ADDR_1;
input [ADSize-1:0]Read_ADDR_2;
input [ADSize-1:0]Write_ADDR;
```

```
input [DASize-1:0]DIN;
```

```
input    Write;
input    Read;
```

```
output [DASize-1:0]OUT_1;
output [DASize-1:0]OUT_2;
```

```
reg [DASize-1:0]OUT_1;
reg [DASize-1:0]OUT_2;
```

```
reg [DASize-1:0] Mreg[REGSize-1:0];
```

```
integer i;
```

```
always@(posedge clk)begin
    if( rst )begin
        for(i=0 ; i<REGSize ; i=i+1)
            Mreg[i] = 0;
        end
    else
        begin
            if(enable)begin
                if( Write )
                    Mreg[Write_ADDR] = DIN;
                else if( Read )begin
                    OUT_1 = Mreg[Read_ADDR_1];
                    OUT_2 = Mreg[Read_ADDR_2];
                end
            end
        end
    end
endmodule
```

