
 


VLSI System Design (Graduate Level)

Digital Design with HDL- Verilog(1)

 [Material adapted from “Advanced Digital Design with the Verilog
HDL” by M.D. Ciletti and lecture notes of Prof. KJ Lee]






Outline

- History of Verilog
- Design-Order Strategy
- Structural Models of Combinational Logic
- Logic Simulation, Design Verification and Test Methodology
- Propagation Delay
- Truth Table Model


[Reading: Ciletti's Chap 4]

What you shall know after this course

 


- Basic rules of Verilog language
- Writing a combinational module using
 - Schematic/gates
 - Truth tables
- Writing a testbench to verify a module

History of Verilog

 

Hardware Description Languages (HDL)

 


- Similarity and Uniqueness
 - Similar to general-purpose languages like C
 - Additional features
 - Modeling and simulation of the functionality of combinational and sequential circuits
 - Parallel vs. sequential behaviors
- Two competitive forces
 - Verilog: C-like language
 - VHDL: ADA-like language



What HDL can do?

- Simulate the behavior of a circuit before it is actually realized.
 - Describe models in common language
 -
 - Execute the models as if they are hardware
 -
 - Be translated into gate-level designs
 -

Development of Verilog

 

1984	Gateway Design Automation, Phil Moorby
1986	Verilog-XL: an efficient gate-level simulator
1988	Verilog logic synthesizer, Synopsys
1989	Cadence Data System Inc. acquired Gateway
1990	Verilog HDL is released to public domain
1991	Open Verilog International (OVI)
1994	IEEE 1364 Working group
1995	December : Verilog becomes an IEEE standard (IEEE Std. 1364)
2001	SystemVerilog

Verilog HDL and Verilog-XL



Verilog HDL


A hardware description language that allows one to describe circuits at different levels of abstraction.

Verilog-XL software:

A high speed, event-driven logic simulator for Verilog HDL





- . **Event-driven simulator** : Evaluate an element only when its inputs change states. Most practical and widely used simulation algorithm.
- . **Verilog-XL** : Incorporates Turbo algorithm, XL algorithm, Switch-XL Algorithm, Caxl algorithm.

Design Order Strategies

 





Typical VLSI Design Cycle

   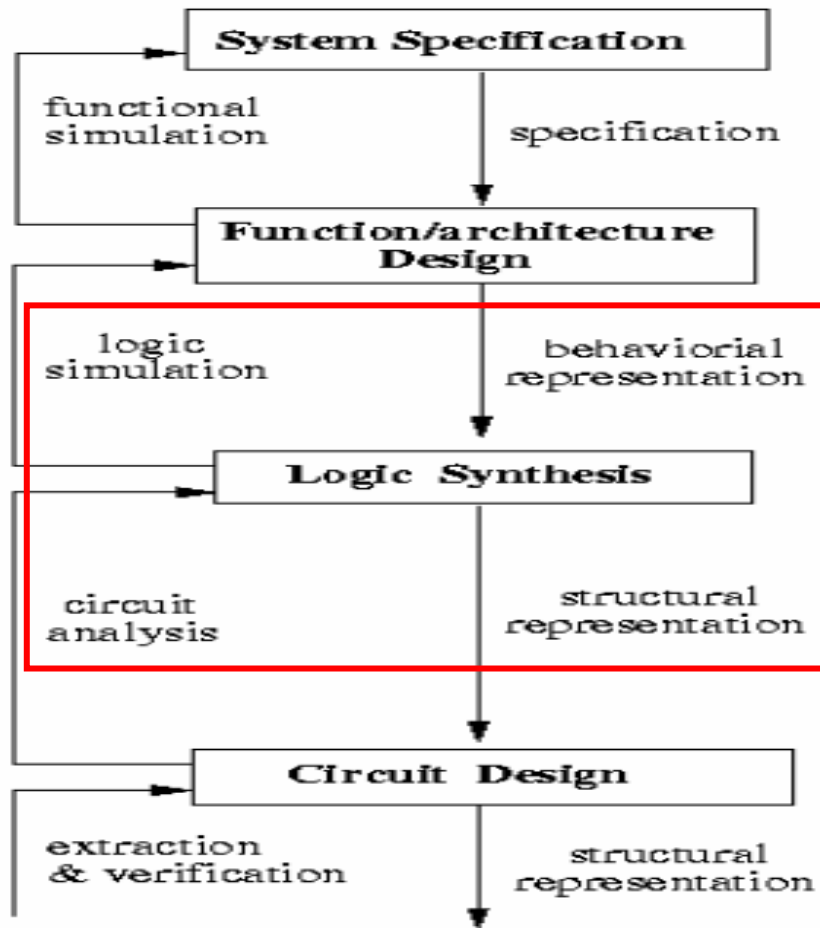

Typical VLSI Design Flow (Cont'd)


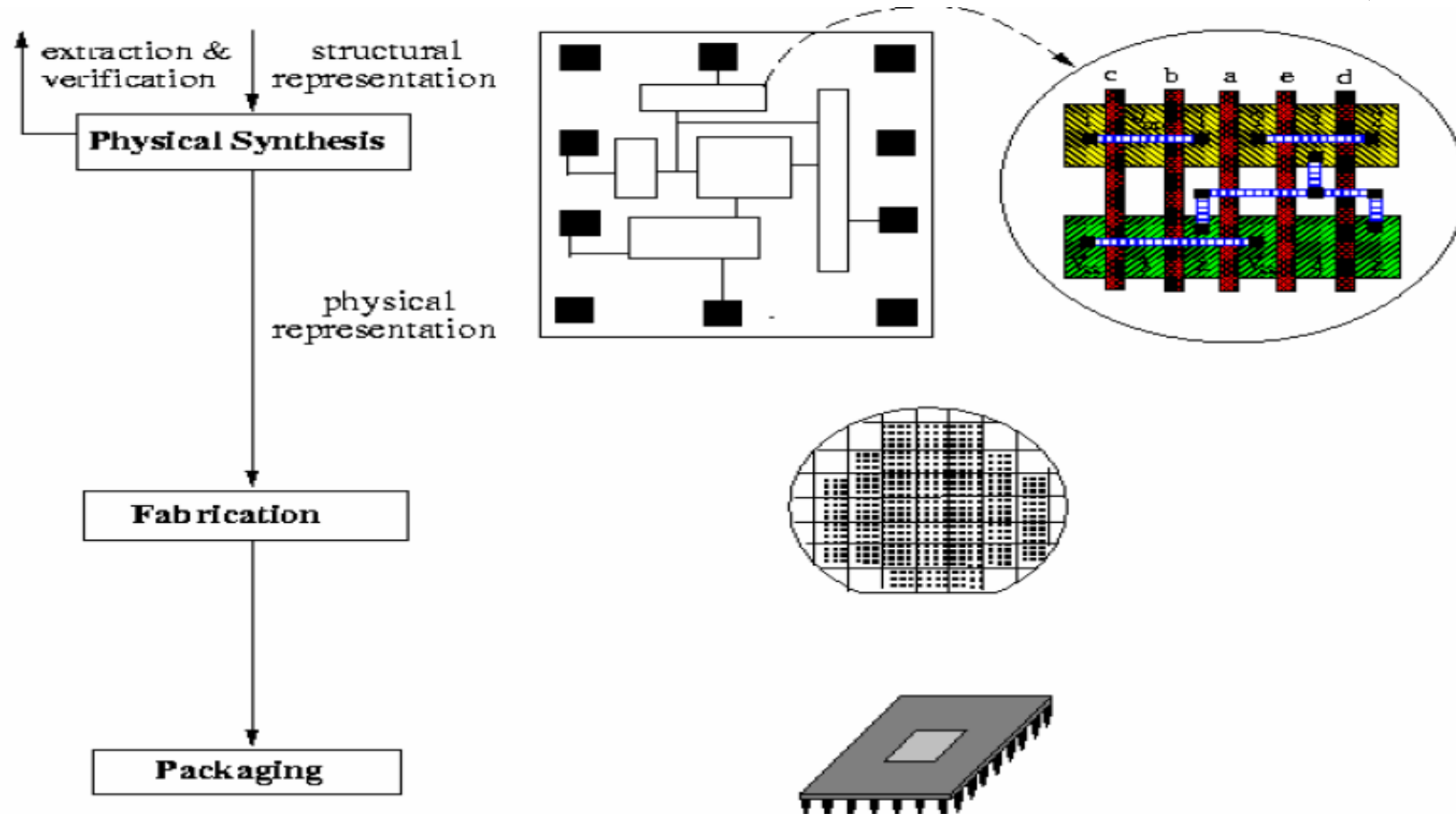


 


Hierarchical Modeling Concepts

- Bottom-up
 - Identify building blocks available
 - Build bigger cells using these building blocks
 - These cells then used for higher-level blocks
- Top-down design methodologies
 - Define the top-level block first
 - Identify the sub-blocks necessary to build the top-level block
 - Further subdivide the sub-blocks until leaf cells
- Hybrid
 - A combination of top-down and bottom-up flows


Bottom-up Design

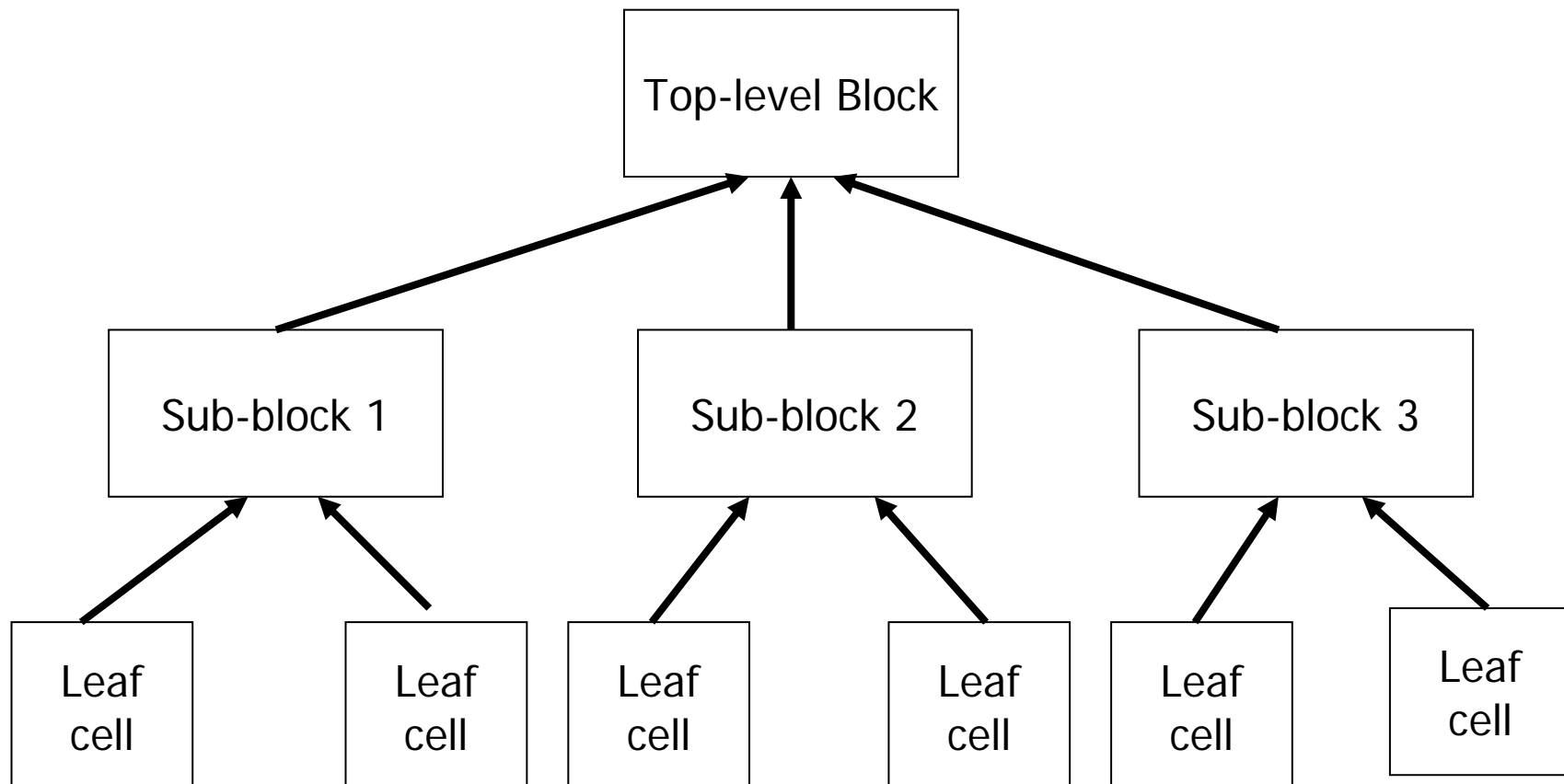 


Bottom-Up Design Flow

 



 
- 4 **Timing, performance, and testability are analyzed.**
- 3 **The complete design is modeled and tested.**
- 2 **Intermediate level components are modeled at the gate level and tested.**
- 1 **Lowest level components are modeled at the gate or circuit level and tested.**





Register

 


ALU

   




Top-down Design

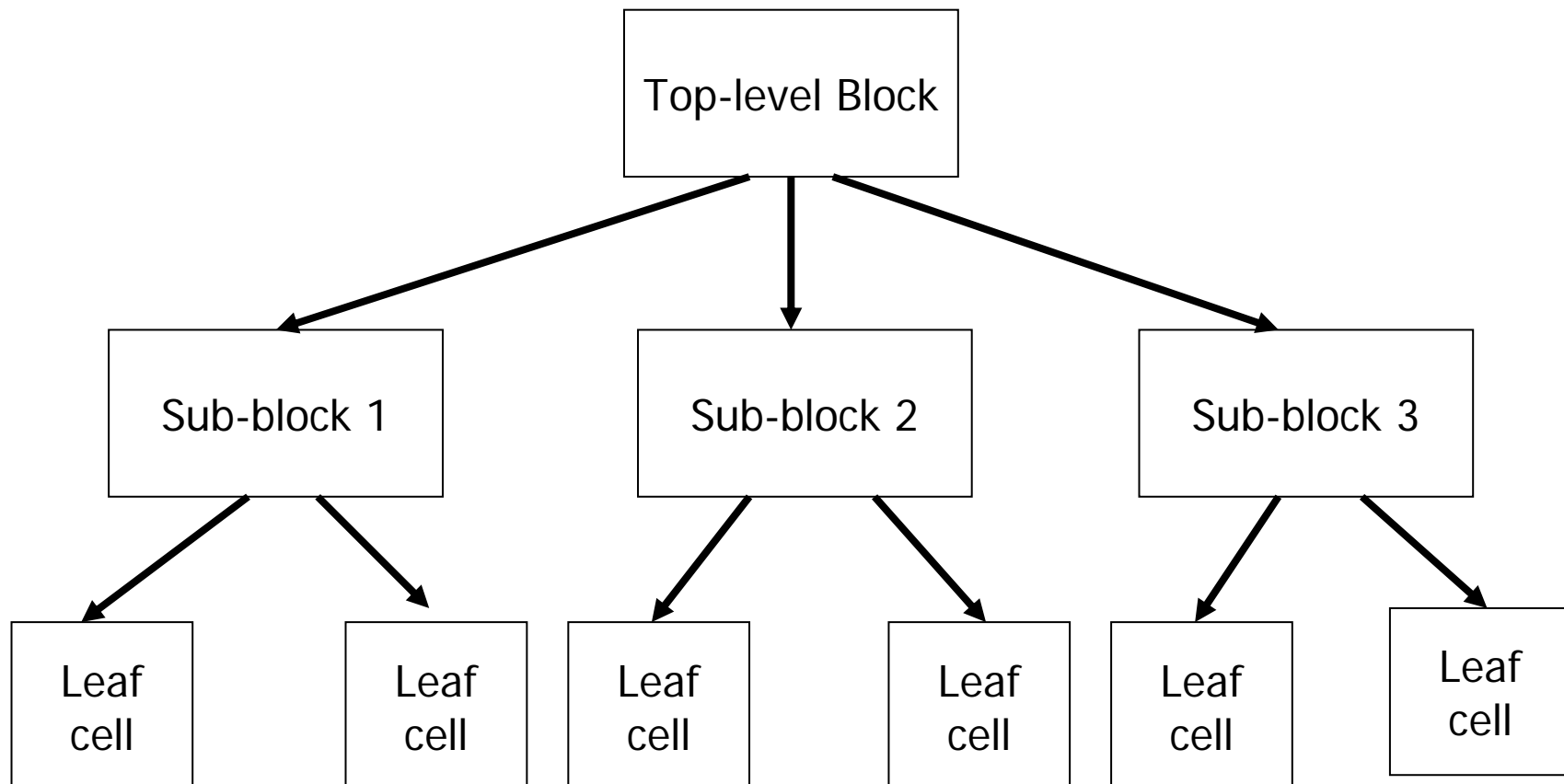 


Top-Down Design Flow

 

   - 1 The top-level system is modeled using a high-level behavioral description.
- 2 Each major component is modeled and simulated at the register transfer level.
- 3 Each major component is modeled and simulated at the gate level.




Structural Models of Combinational Logic

 





Example: Half-adder

a	b	sum	c_out
0	0		
0	1		
1	0		
1	1		


 



```
module Add_half (sum, c_out, a, b);  
  input  a, b;  
  output c_out, sum;  
  
  and    (c_out, a, b);  
endmodule
```

3-bit mux


 
 


3-bit 2x1 Multiplexier

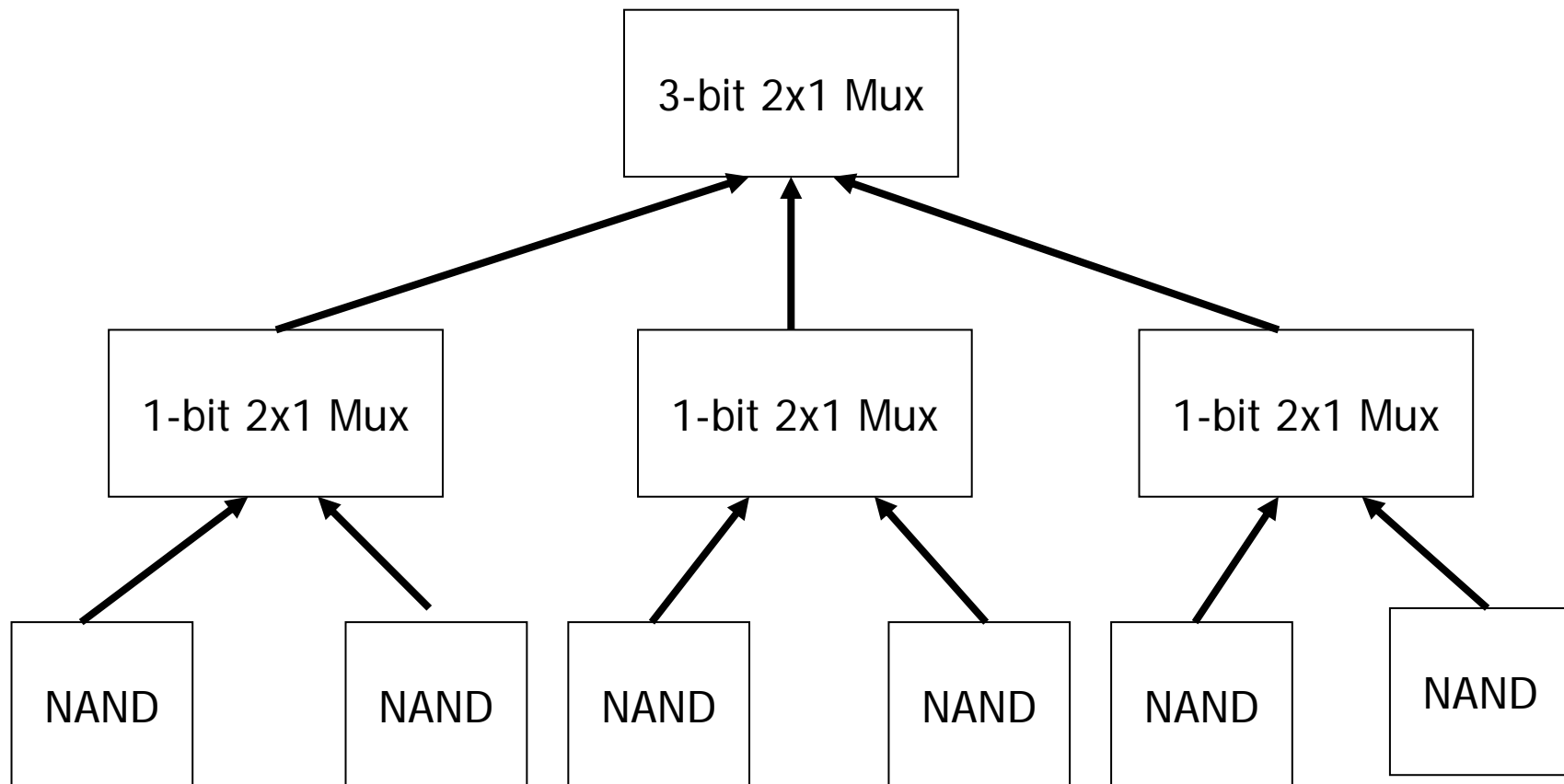 

 


Concepts of Modules

   

Design of a 2x1 Multiplexier




 A multiplexier:
select a signal from available inputs





s	a	b	f
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Boolean Eq. of a MUX

 

- $F = s'a + sb$
- Implement using NAND gates
- $F = ?$

One-bit mux

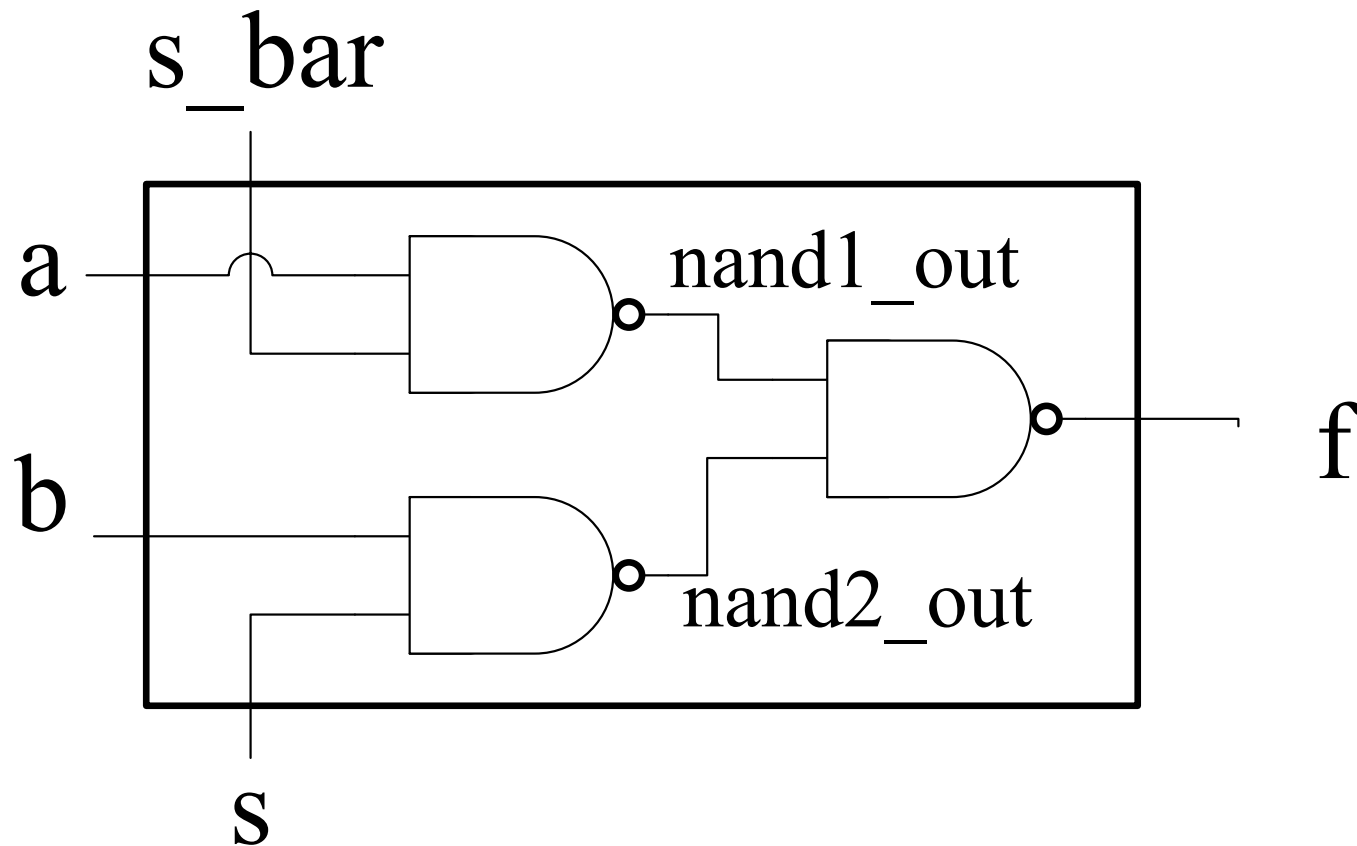 

 


Verilog Implementation

Main frame

Variable declaration

Main body

 

```
module mux2x1(f, s ,s_bar, a, b);
```

```
    output f;
```

```
    input s, s_bar;
```

```
    input a, b;
```

```
    wire nand1_out, nand2_out;
```

```
    // boolean function
```

```
    nand(nand1_out, s_bar, a);
```

```
    nand(nand2_out, s, b);
```


```
    nand(f, nand1_out, nand2_out);
```

```
endmodule
```



Connectivity

 - Wire
 - Its value is determined during simulation
 - The default type for an undeclared identifier
- Port
 - Position sensitive
 - Add_half_0_delay M1(w1, w2, a, b);
 - Explicitly declared
 - Add_half_0_delay M1(.b(b), .c_out(w2), .a(a), .sum(w1));



Verilog Implementation


```
module mux_3b (f2,f1,f0,a0,b0,a1,b1,a2,b2,  
select,select_bar);
```


```
    input a0,b0,a1,b1,a2,b2;  
    input select, select_bar;  
    output f2,f1,f0;
```

```
    mux2x1  M0(f0,select, select_bar, a0,b0);  
    mux2x1  M1(f1,select, select_bar, a1,b1);  
    mux2x1  M2(f2,select, select_bar, a2,b2);
```

```
endmodule
```

Full adder

 

 

Coding Notes

```
module Add_full_0_delay(sum, c_out, a, b, c_in);
```

```
    output                sum, c_out;
```

```
    input                 a, b, c_in;
```

```
    wire                  w1, w2, w3;
```


```
    Add_half_0_delay      M1 (w1, w2, a, b);
```

```
    Add_half_0_delay      M2 (sum, w3, w2, c_in);
```

```
    or                    M3 (c_out, w2, w3);
```

```
endmodule
```

Module instance
name

 

Example: 4-bit RCA



```
module Add_rca_4 (sum, c_out, a, b, c_in);  
    output      [3: 0]    sum;  
    output      c_out;  
    input       [3: 0]    a, b;  
    input       c_in;  
    wire        c_in2, c_in3, c_in4;  
  
    Add_full M1 (sum[0], c_in2, a[0], b[0], c_in);  
    Add_full M2 (sum[1], c_in3, a[1], b[1], c_in2);  
    Add_full M3 (sum[2], c_in4, a[2], b[2], c_in3);  
    Add_full M4 (sum[3], c_out, a[3], b[3], c_in4);  
endmodule
```




Vectors in Verilog


- e.g., `output[15:0] sum;`
- Leftmost index bit is the most significant bit
- Rightmost index bit is the least significant bit
- If out of bounds, x is returned
 - X: unknown value

Example: 16-bit RCA

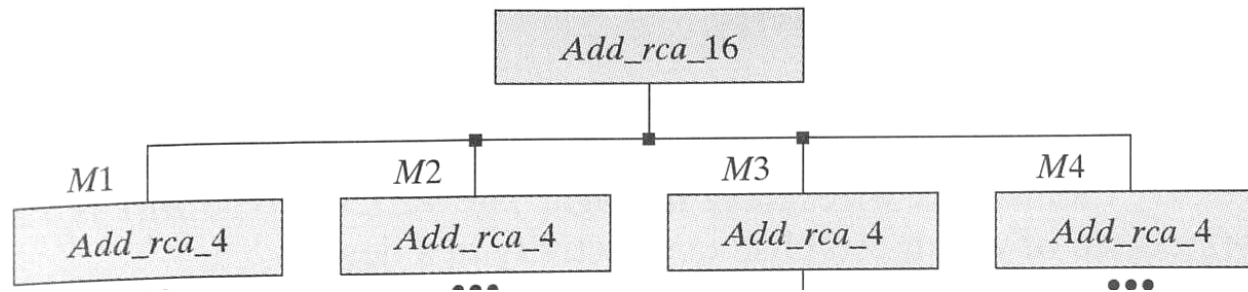 

 
Logic Simulation, Design Verification and Test Methodology





 


Logic values of the signal

 - 4 valued logic: 0, 1, x, and z
 - x: unknow
 - z: high impedance



Signal Contention and Resolution

   




Test Methodology

- Input pins of 16-bit RCA: 33
- Require 2^{33} input patterns → difficult to realize
- Suggestions
 - Verify basic components first: half-adder/ fulladder
 - Then composite components: 4-bit slice units
 - Chose set of patterns carefully



Testbench

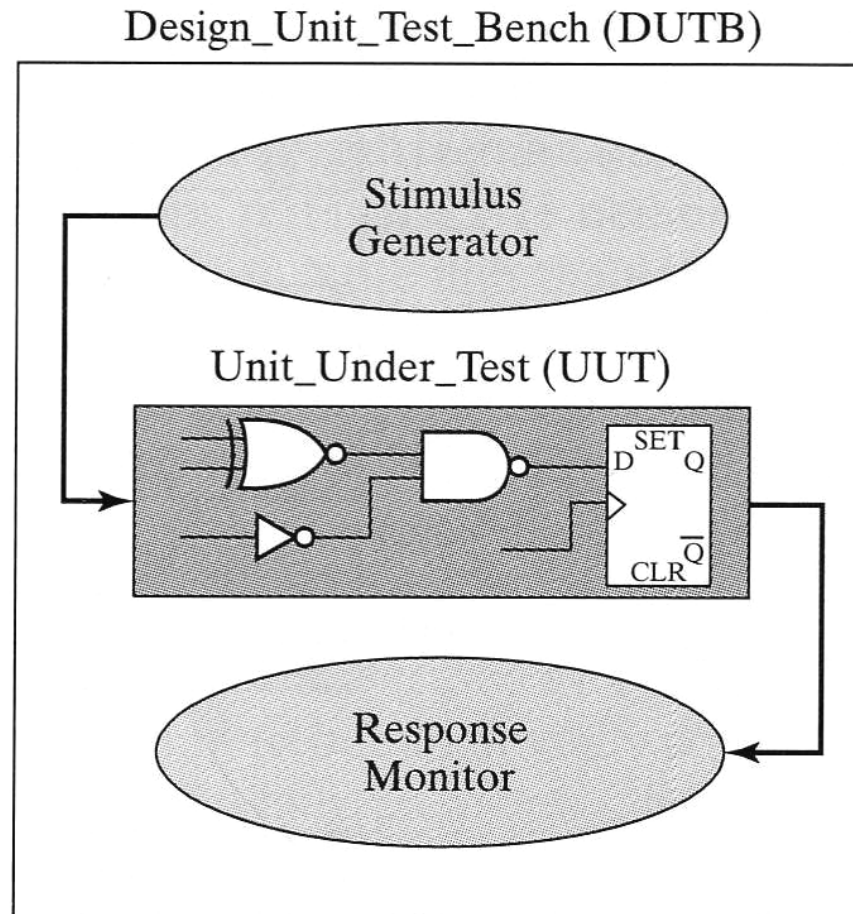


- Generate test patterns
 - Waveforms to inputs
- Timing of applying patterns
 - Delay in signals
 - Clock generation
- Start/end time for simulation
 - \$initial
 - \$finish



 Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay  M1 (sum, c_out, a, b);    // UUT  
    initial begin                               // Time Out  
        #100 $finish;  
    end  
  
    initial begin  
        #10  a = 0; b = 0;  
        #10  b = 1;  
        #10  a = 1;  
        #10  b = 0;  
    end  
endmodule
```



Signal Generators

- *initial*:
 - A single-pass behavior
 - Let the simulator starting from $t_{sim} = 0$
 - Procedural statements enclosed in `begin ... end`
- Delay time
 - Proceeding the statement: `#10 b = 1;`
 - Delay the execution until specified time
- Signal type: *reg*
 - Retain its value from the moment assigned by the procedural statement until change by the next statement
 - Initially given the value *x*
- Stop: *\$finish* == return control to the OS

Test Fixture Template




```
module testfixture ;
```

```
    // Data type  
    declaration
```

```
    // Instantiate modules
```


```
    // Apply stimulus
```
 
```
    // Display results  
endmodule
```




There are no ports for test fixture

Test Fixture - Making an Instance

 
 
```
module testfixture ;  
  
    // Data type declaration  
  
    // MUX instance  
        MUX2_1 mux (out, a, b, sel) ;  
    // Apply stimulus  
  
    // Display results  
  
endmodule
```



Propagation Delay


- For functionality, verification with 0 delay is quick.
- For physical logic gate, verification with unit delay can expose the time sequence of signal activity.
- For timing verification, simulation must obtain cell delay to account for real delay.



Types of Delay

- Inertial Delay
 - Delay due to gate itself
 - Input pulse width must larger than

 - Transport delay
 - Delay due to the a wire of circuit





Truth Table Models

```
primitive AOI_UDP (y, x_in1, x_in2, x_in3, x_in4, x_in5);
    output      y;
    input x_in1, x_in2, x_in3, x_in4, x_in5;
```

table

// x1 x2 x3 x4 x5

0 0 0 0 0 : 1;

0 0 0 0 1 : 1;

0 0 0 1 0 : 1;

0 0 0 1 1 : 1;

0 0 1 0 0 : 1;

0 0 1 0 1 : 1;

0 0 1 1 0 : 1;

0 0 1 1 1 : 0;

0 1 0 0 0 : 1;

0 1 0 0 1 : 1;

0 1 0 1 0 : 1;


0 1 0 1 1 : 1;

0 1 1 0 0 : 1;

0 1 1 0 1 : 1;

0 1 1 1 0 : 1;

0 1 1 1 1 : 0;

 

- Build user-defined primitives (UDP)

Mux_prim

```
primitive mux_prim (mux_out, select, a, b);
```

```
    output      mux_out;
```

```
    input      select, a, b;
```

```
    table
```

```
// select      a      b      :      mux_out
```

```
    0           0      0      :      0;
```

```
    0           0      1      :      0;
```

```
    0           0      x      :      0;
```

```
    0           1      0      :      1;
```

```
    0           1      1      :      1;
```

```
    0           1      x      :      1;
```

```
// select      a      b      :      mux_out
```

```
    1           0      0      :      0;
```

```
    1           1      0      :      0;
```

```
    1           x      0      :      0;
```

```
    1           0      1      :      1;
```

```
    1           1      1      :      1;
```


```
    1           x      1      :      1;
```

```
    x           0      0      :      0;
```

```
    x           1      1      :      1;
```

```
    endtable
```

```
endprimitive
```

 

- Reduce ambiguousness in last two rows

