
 


# VLSI System Design (Graduate Level)

**QuickStart – Verilog Basics**


**Fall 2008**

 


 
# Outline


- Overview
- From RTL to Gate Level
- Quick Start for Verilog
- 9/25 Tutorial
  - Basics of Unix, Environment in SoC Lab, Verilog-XL simulator, Debussy, Design Vision
  - 9:10-10:00 Overview
  - 10:10-noon Hand-on practices @CIC or SoC Lab
    - If your last digit of your student ID is even, please go to CIC.
    - If odd, go to SoC Lab, please.
  - Watch video last year first




# Things to Learn

- What position is the course in the digital design flow?
- What is RTL?
- What is hierarchical design?
- What is testbench?
- What are basic elements of Verilog language?

# Target Digital Design Implementation


 

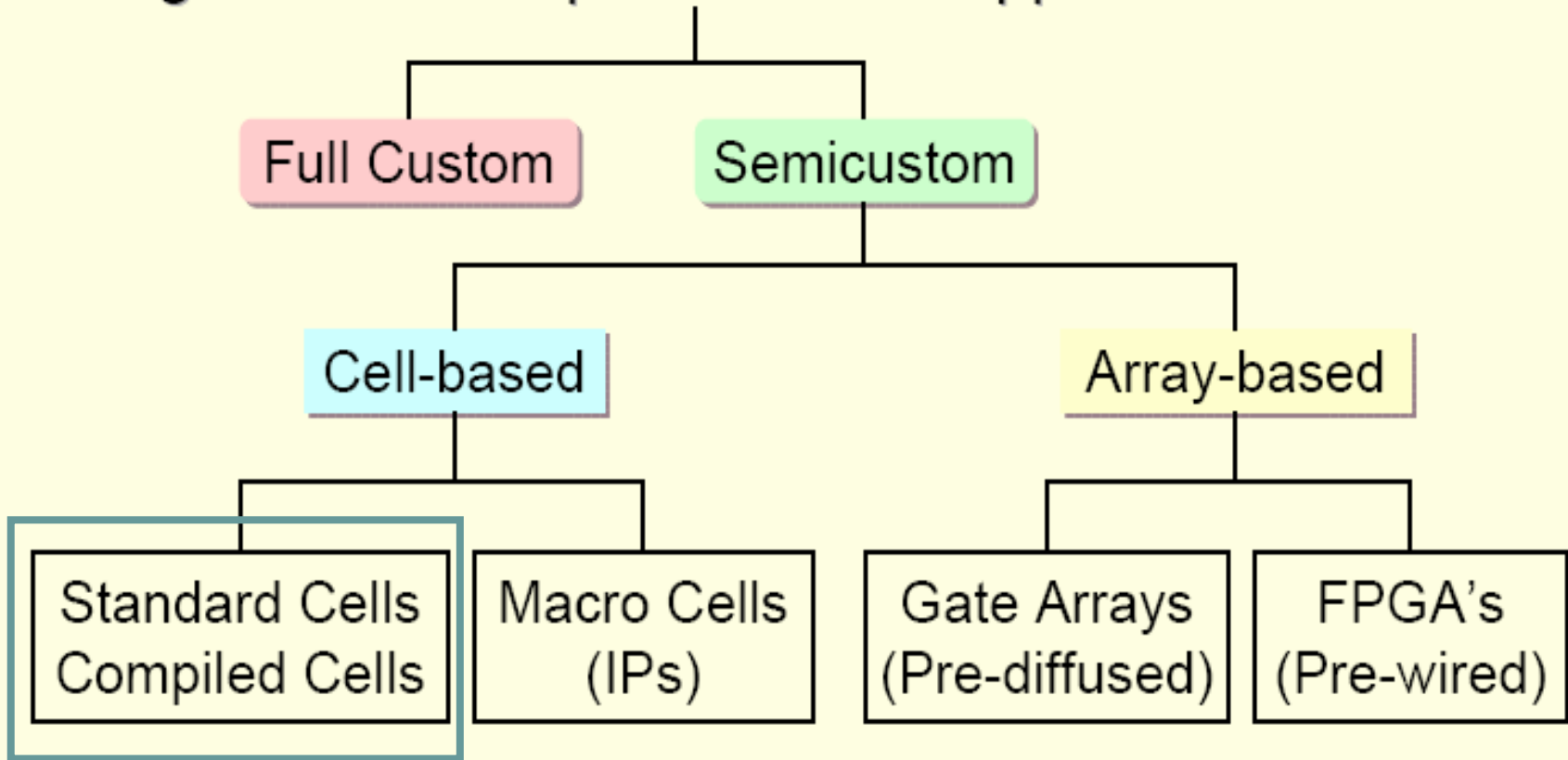
## Digital Circuit Implementation Approaches





# Standard Cell Design Style

 
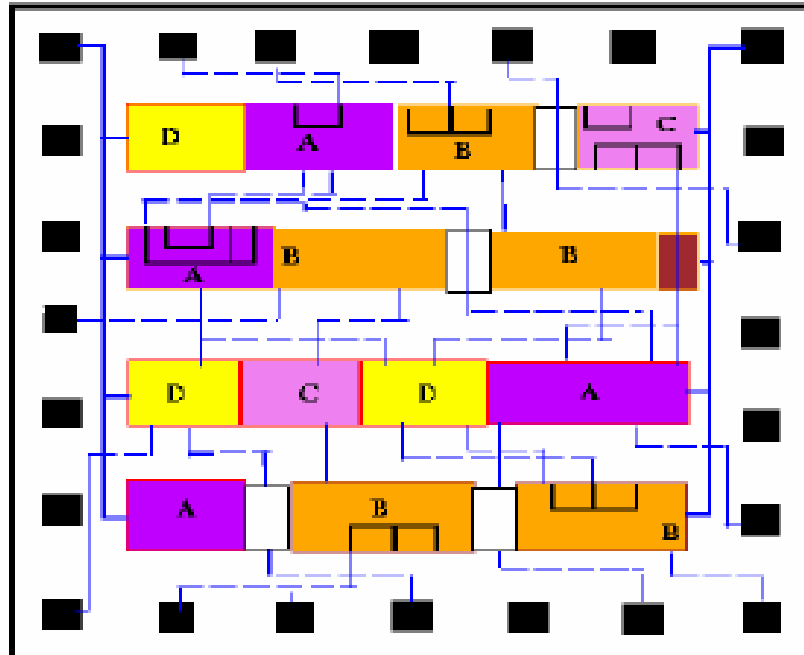


Selects pre-design cells (of the same height) to implement logic

These cells may be


- Logic gates: nand2, NOT, and2, and4, nor2, mux2, decoder etc.
- Latches: latchx1, latchrx2, ...
- Flip-flops: pdffx1, pdffx2, ...
- Basic blocks: fulladder

# Target Levels of Design Abstractions

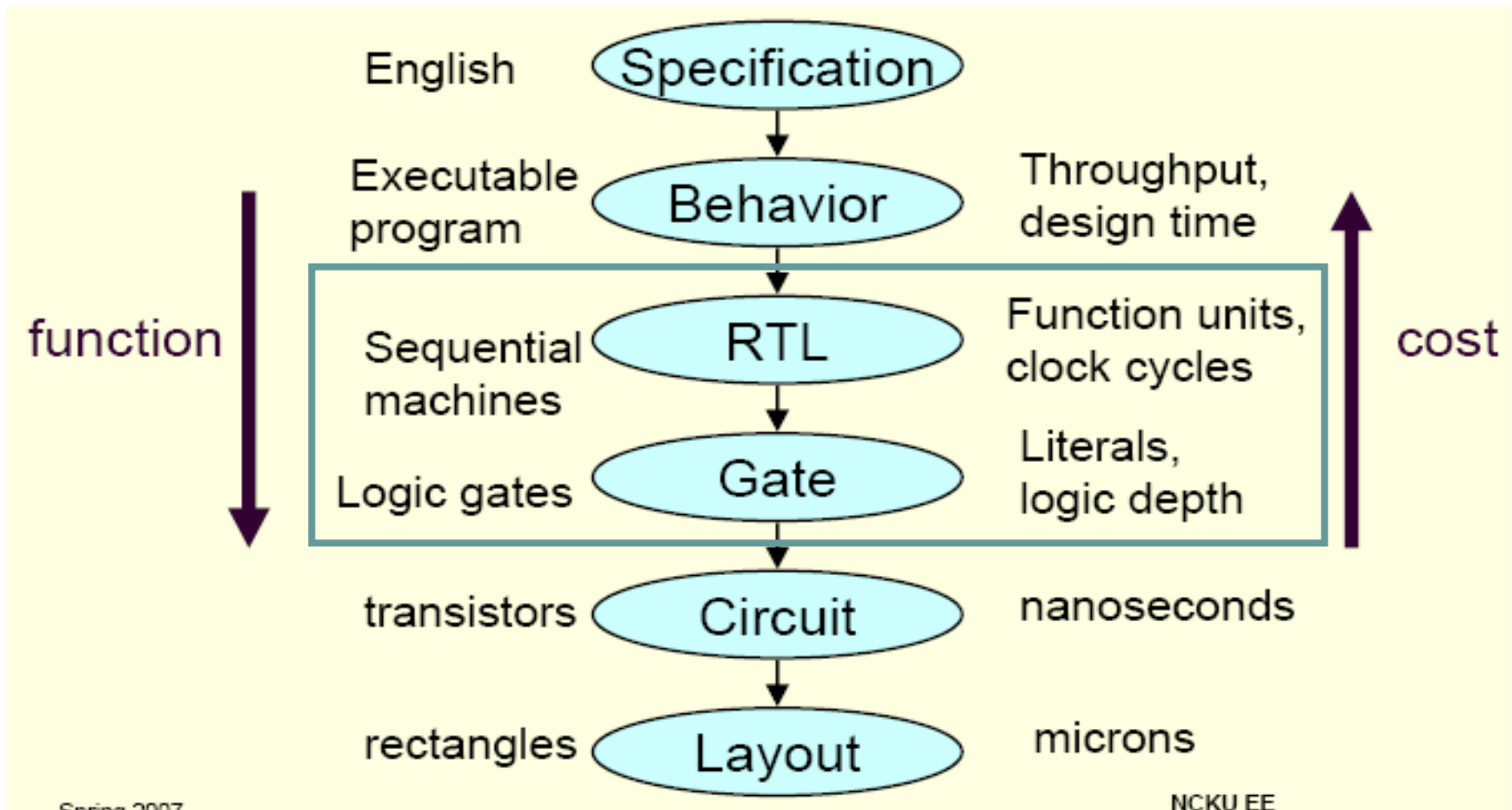 


Spring 2007

NCKU EE

 

 
# Register-Transfer Level


- RTL description is a way of describing the operation of a synchronous machine.
- The behavior of a machine is defined by the flow of signals (or transfer of data) between hardware registers and the logical operations (+, -, not, ....)



A simple RTL design

 


# A Complex RTL Design -- CPU

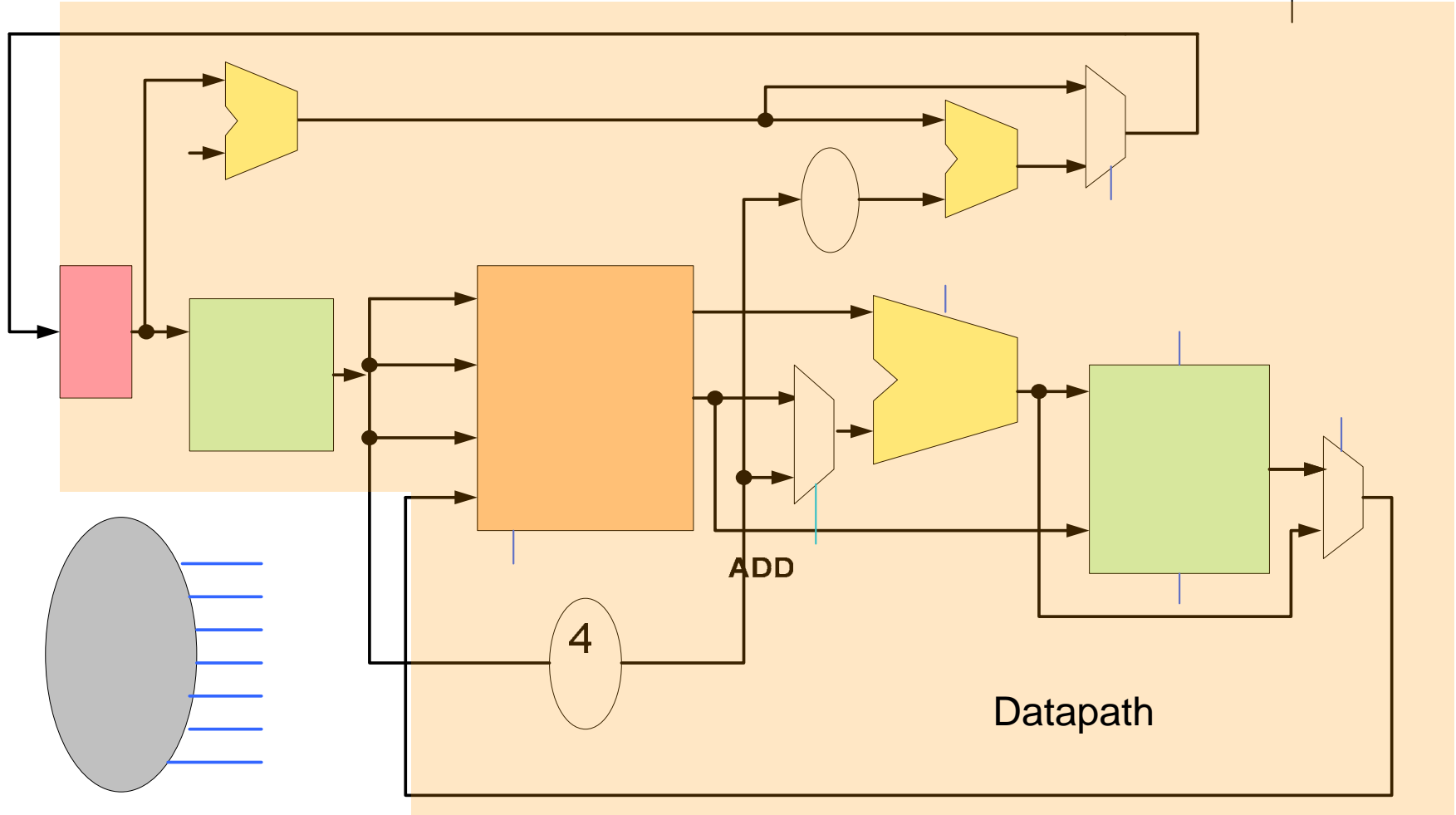






# CPU in Action (ALU REG <- REG )

 


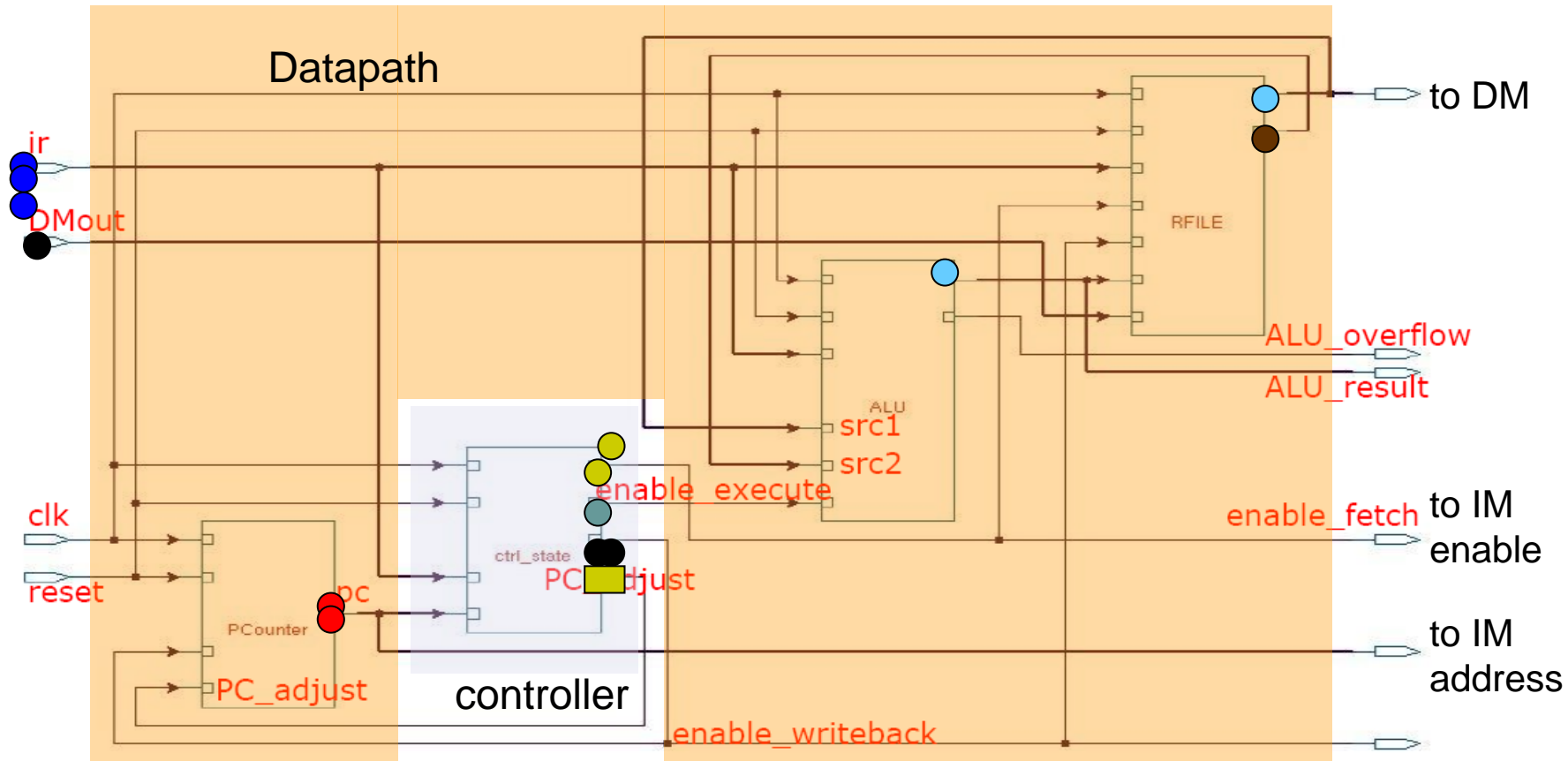- $RF[dst] \leftarrow ALU(RF(src), RF(dst))$



# One-bit Multiplexer

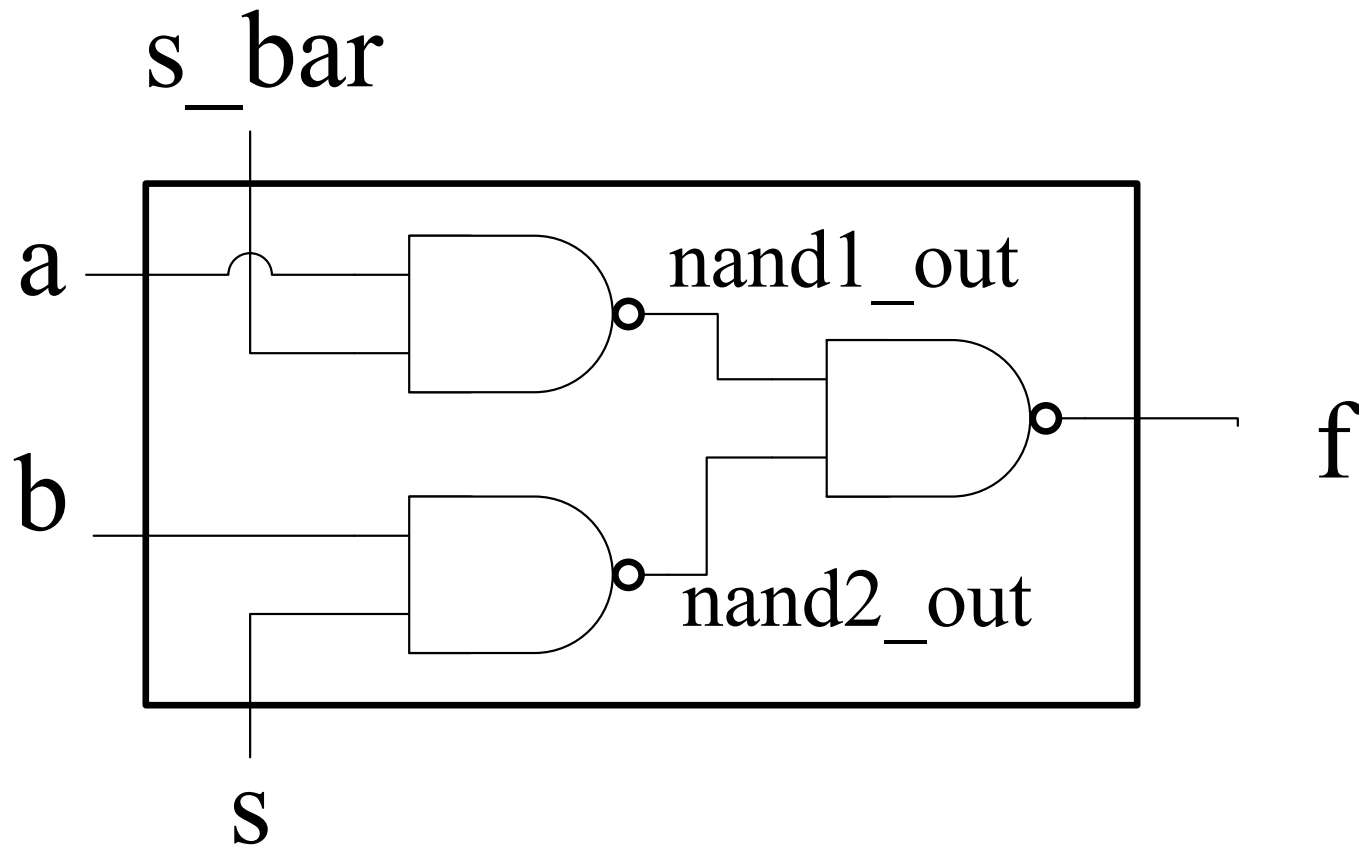 

 


# First Look at Verilog (1/2)

Main frame

Variable declaration

Main body

 

```
module mux2x1(f, s, s_bar, a, b);
```

```
    output f;
```

```
    input s, s_bar;
```

```
    input a, b;
```

```
    wire nand1_out, nand2_out;
```


```
    // boolean function
```

```
    nand(nand1_out, s_bar, a);
```

```
    nand(nand2_out, s, b);
```

```
    nand(f, nand1_out, nand2_out);
```

```
endmodule
```

 

# First Look at Verilog (2/2)

## Variable declaration

output

Input

wire

```
module mux2x1(f, s, s_bar, a, b);
```

```
    output f;
```

```
    input s, s_bar;
```

```
    input a, b;
```

```
    wire nand1_out, nand2_out;
```

```
    // boolean function
```

```
    nand(nand1_out, s_bar, a);
```

```
    nand(nand2_out, s, b);
```

```
    nand(f, nand1_out, nand2_out);
```


```
endmodule
```

## Main body



 
# Basic Language Rules

- General
  - A statement shall **terminate with semicolon (;), except *endmodule***
  - Comments: (//) for single line and {/\*, \*/} for multiple lines
- Naming
- Number representation
- Primitive operators
- First examples



 
# Naming

- Case sensitive
  - C\_out\_bar and C\_OUT\_BAR: two different identifiers
- NO whitespace
- Accepted chars
  - Lower/upper case letters
  - Digits (0,1,...,9)
  - Underscore (\_)
  - Dollar sign (\$)
  - Max characters: 1024


 
# Number Representation

- May be represented using
  - Binary, octonary, decimal, hexadecimal,
- Format
  - `<size>'<base_format> <number>`
  - base\_format:
    - b, o, d, h
- Example
  - `4'b1111; -16'd255`
  - `23456` (32-bit decimal # by default); `'hc3` (32 bit)
  - `12'b1111_0000_1010`




# Primitive Operator

- Most basic functional models of combinational logic gates
- Built in the Verilog


TABLE 4-1 Verilog primitives for modeling combinational logic gates.

<i>n</i> -Input	<i>n</i> -Output, 3-state
and	buf
nand	not
or	bufif0
nor	bufif1
xor	notif0
xnor	notif0




 

# Example: AOI Gate

 

 
Output ports of a primitive first, followed by its input port(s)!


 
# Module Ports

- Interface to the environment
- Mode
  - Input
  - Output
  - Inout: bidirectional
- Not order sensitive in declaration

```
module AOI (y_out,x_in1,x_in2,x_in3,x_in4,x_in5);  
  
    input x_in1,x_in2;  
    input x_in5,x_in4,x_in3;  
    output y_out;  
  
    // ...  
endmodule
```



# Module Ports

- Order sensitive when used

- Position sensitive



AOI M1(w1, a1, a2, b1, b2, b3);


- Explicitly declared

**AOI** M1 ( .x\_in3(b1), .y\_out(w1), .x\_in2(a2), .x\_in1(a1),.x\_in4(b2), .x\_in5(b3));

```
module AOI (y_out,x_in1,x_in2,x_in3,x_in4,x_in5);  
  
    input x_in1,x_in2;  
    input x_in5,x_in4,x_in3;  
    output y_out;  
  
    // ...  
endmodule
```

# Testbench

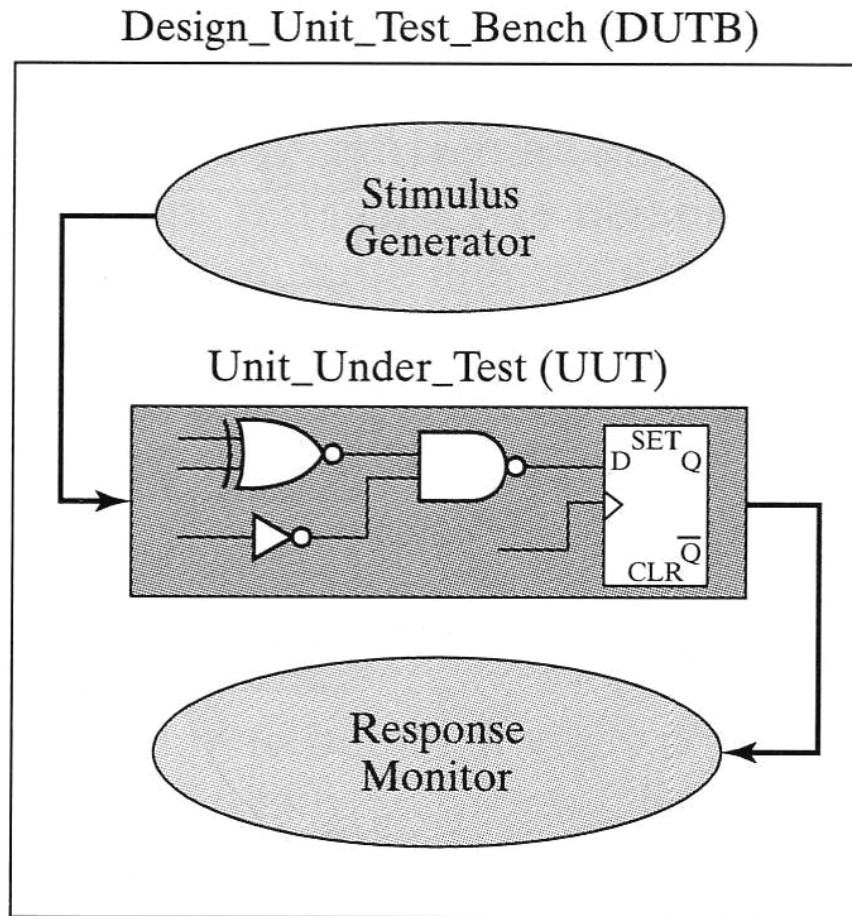 

 


# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay  M1 (sum, c_out, a, b);    // UUT  
    initial begin                                // Time Out  
        #100 $finish;  
    end
```

 **Unit under test**


```
    initial begin  
        #10  a = 0; b = 0;  
        #10  b = 1;  
        #10  a = 1;  
        #10  b = 0;  
    end  
endmodule
```


 
# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay M1 (sum, c_out, a, b);    // UUT  
    initial begin                               // Time Out  
        #100 $finish;  
    end  
  
    initial begin  
        #10 a = 0; b = 0;  
        #10 b = 1;  
        #10 a = 1;  
        #10 b = 0;  
    end  
endmodule
```


**Module name:**  
a module called  
Add\_half\_0\_delay is  
used


 
# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay M1 (sum, c_out, a, b);    // UUT  
    initial begin                               // Time Out  
        #100 $finish;  
    end  
  
    initial begin  
        #10 a = 0; b = 0;  
        #10 b = 1;  
        #10 a = 1;  
        #10 b = 0;  
    end  
endmodule
```

**User defined name:**  
M1 is for internal  
identification only.  
you may name is as  
X1, or hadd1, or ....




# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay  M1 (sum, c_out, a, b);    // UUT  
    initial begin                               // Time Out  
        #100 $finish;  
    end
```

 **Define length of simulation**

```
    initial begin  
        #10  a = 0; b = 0;  
        #10  b = 1;  
        #10  a = 1;  
        #10  b = 0;  
    end  
endmodule
```






# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay M1 (sum, c_out, a, b);    // UUT  
    initial begin                               // Time Out  
        #100 $finish;  
    end
```

```
    initial begin  
        #10 a = 0; b = 0;  
        #10 b = 1;  
        #10 a = 1;  
        #10 b = 0;  
    end  
endmodule
```
 
## *initial:*

- A single-pass behavior
- Let the simulator starting from  $t_{sim} = 0$
- Procedural statements enclosed in `begin ... end`



# Example 4.7


```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay  M1 (sum, c_out, a, b);    // UUT  
    initial begin                                // Time Out  
#100 $finish;  
    end
```

```
    initial begin  
#10  a = 0; b = 0;  
#10  b = 1;  
#10  a = 1;  
#10  b = 0;  
    end  
endmodule
```

***\$finish***

**== STOP**

**== return control  
to the OS**

 


# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay  M1 (sum, c_out, a, b);    // UUT  
    initial begin                                // Time Out  
        #100 $finish;  
    end  
  
    initial begin  
        #10  a = 0; b = 0;  
        #10  b = 1;  
        #10  a = 1;  
        #10  b = 0;  
    end  
endmodule
```

 **Delay time**

- Proceeding the statement: #10 b = 1;
- Delay the execution until specified time



# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay M1 (sum, c_out, a, b);    // UUT  
    initial begin                               // Time Out  
        #100 $finish;  
    end
```


```
    initial begin
```

```
        #10  a = 0; b = 0;  
        #10  b = 1;  
        #10  a = 1;  
        #10  b = 0;
```

```
    end
```

```
endmodule
```

**Define Inputs**

 


# Example 4.7

```
module t_Add_half();  
    wire      sum, c_out;  
    reg       a, b;  
    Add_half_0_delay M1 (sum, c_out, a, b);    // UUT  
    initial begin                               // Time Out  
        #100 $finish;  
    end
```

```
    initial begin  
        #10 a = 0; b = 0;  
        #10 b = 1;  
        #10 a = 1;  
        #10 b = 0;  
    end  
endmodule
```


a	0	0	1	1	1	1
b	0	1	1	0	0	0

time →

 
 
# Signal Generators


- **initial:**
  - A single-pass behavior
  - Let the simulator starting from  $t_{\text{sim}} = 0$
  - Procedural statements enclosed in begin ... end
- Delay time
  - Proceeding the statement: `#10 b = 1;`
  - Delay the execution until specified time
- Signal type: **reg**
  - Retain its value from the moment assigned by the procedural statement until change by the next statement
  - Initially given the value  $x$
- **\$finish** == return control to the OS




# Data Types

- Net: **wire**
  - Acts like wires in a physical circuit
  - Connects design objects
  - Needs for a driver
- Register: **reg, integer**
  - Acts like variables in ordinary procedural languages
  - Stores information while the program executes
  - No needs for a driver, changes its value as wish

# Nets

 

 - Nets are continuously driven by the devices that drive them.
- Verilog automatically propagates a new value onto a net when the drivers on the net change value.





# Registers



- A register is merely a variable, which holds its value until a new value is assigned to it. It is different from a hardware register.

