

N26F300
VLSI SYSTEM DESIGN
(GRADUATE LEVEL)

Fall 2010

Synthesis for Verilog (I)

Outline

2

- Synthesis Tasks
- Unsupported Verilog Constructs
- Supported Verilog Constructs
- Synthesis of Combinational Blocks

Things That Synthesis Does

3

- Detect and eliminate redundant logic
- Detect combinational feedback loops
- Exploit don't care conditions
- Detect unused states
- Detect and collapse equivalent states
- Make state assignments
- Synthesize optimal, multilevel realizations of logic subject to constraints in a physical technology

Synthesizable Verilog Codes

4

- Synopsys can't accept all kinds of Verilog constructs
- Synopsys can only accept a subset of Verilog syntax and this subset is called “Synthesizable Verilog Code”
- Understanding how to write synthesis-friendly Verilog models is the key to automated design methods.

Unsupported Verilog Constructs (1 / 5)

5

□ Definitions and Declarations

- **primitive** definition
- **real** declaration
- **time** declaration
- **event** declaration
- **triand**, **trior**, **tri1**, **tri0**, and **triereg** net types
- ranges and arrays for **integers**
- **specify** and **endspecify**

Unsupported Verilog Constructs (2/5)

6

□ Statements (1 / 2)

- **defparam**

- **initial**

- **repeat** (they are not supported because equivalent functionality can be constructed by other constructs)

- **delay** (delay-based timing control, intra-assignment timing control)

- **event** (named event control)

- **wait** (level-sensitive timing control)

- **forever**

Unsupported Verilog Constructs (3/5)

7

□ Statements (2/2)

- **fork/join** (helpful in modeling complex waveform in testbenches and abstract models of behavior)
- **assign/deassign** for register type (commonly used for controlled periods of time inside a procedural block)
- **force/release** for registers and nets (typically used in the interactive debugging process)
 - * Recommended to be used in stimulus or as debug statement.
- Assignment statements with a variable used as a bit-select on the left side of the equal sign.

Unsupported Verilog Constructs (4/5)

8

□ Operators

- **case equality** (===) and **case inequality** (!==)
- division and modulus operators for variables (?)

□ Miscellaneous constructs

- hierarchical names within a module
- **'ifdef**, **'endif**, and **'else** **compiler directives**

Unsupported Verilog Constructs (5/5)

9

□ Switch-level Constructs

- **nmos, pmos, cmos**

- **rnmos, rpmos, rcmos**

- **tran, tranif0, trnaif1**

- **rtran, rtranif0, rtranif1**

- **pullup, pulldown**

Language Constructs commonly supported by Synthesis Tools (I)

10

- Module declaration
- Port name: **input**, **output**, and **inout**
- Port binding by name
- Port binding by position
- Local parameter declaration
- Connectivity nets: **wire**, **tri**, **wand**, **wor**, **supply0**, and **supply1**
- Register variables: **reg**, **integer**
- integer types in binary, decimal, octal, hex format
- Scalar and vector nets
- Sub_range of vector nets on RHS of assignment
- Module and macro_module instantiation
- Primitive instantiation

Language Constructs commonly supported by Synthesis Tools (II)

11

- Continuous assignments
- Shift operator
- Conditional operator
- Concatenation operator (including nesting)
- Arithmetic, bitwise, reduction, logical and relational operators
- Procedure block assignments (**begin ... end**)
- **case**, ~~casex~~, **casez**, **default**
- Branching: **if**, **if ... else**, **if ... else ... if**
- **disable** (of procedure block)
- **for** loop
- Tasks: **task ... endtask** (no timing or event control)
- Functions: **function ... endfunction**

Practical considerations

12

- Non-blocking & blocking statements
- Resource sharing
- Conditional operator
- If, case, for statements
- Parenthesis – multi-level circuit
- Minimizing registers
- Don't care inference
- Sharing complex operators
- Finite state machine
- Latches & Flip-flops
- Synopsys compiler directives
- Some Synthesis tips

13

Synthesis of Combinational Logic


Synthesizable Statements for Combinational Logic

14


- a netlist of structural primitives
 - ▣ A design that is expressed as a netlist of primitives should be synthesized to **remove any redundant logic** before mapping the design into a technology.
- a set of continuous assignment statements
 - ▣ The expression that assigns value to a net variable in a continuous assignment statement will be translated by the synthesis tool to an equivalent Boolean equation.
- a level-sensitive cyclic behavior (e.g., **always @(a or b)**)
 - ▣ It will be synthesized to combinational logic if it assigns a value to each output for every possible value of its inputs.

Structural primitives

Before
synthesis

 

After synthesis

 

```
module boole_opt (y_out1, y_out2, a,
b, c, d, e);
```

```
output      y_out1, y_out2;
```

```
input       a, b, c, d, e;
```

```
and         (y1, a, c);
```

```
and         (y2, a, d);
```

```
and         (y3, a, e);
```

```
or          (y4, y1, y2);
```

```
or          (y_out1, y3, y4);
```

```
and         (y5, b, c);
```

```
and         (y6, b, d);
```

```
and         (y7, b, e);
```


```
or          (y8, y5, y6);
```

```
or          (y_out2, y7, y8);
```

```
endmodule
```

Continuous Assignment

```
module or_nand (y, enable, x1, x2, x3, x4);  
  output y;  
  input  enable, x1, x2, x3, x4;  
  
  assign y = ~(enable & (x1 | x2) & (x3 | x4));  
endmodule
```

 


Blocking and non-Blocking (1 / 2)

17

- Use non_blocking assignments within sequential always block.


```
always @(posedge clock) begin
    x <= a;
    y <= x;
    z <= y;
end
```

expect

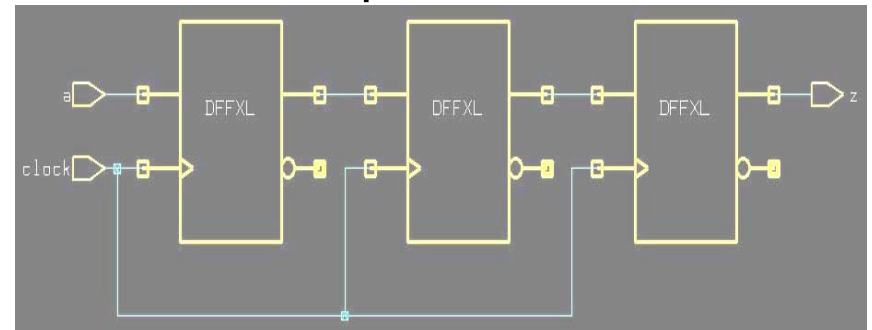

```
always @(posedge clock) begin
    x = a;
    y = x;
    z = y;
end
```

may not expect

 


Blocking and non-Blocking (2/2)

18


- Use blocking assignments within combinational always block expect

```
always @(a or b or x) begin
    x = a & b;
    y = x | b;
    x = a;
end
```

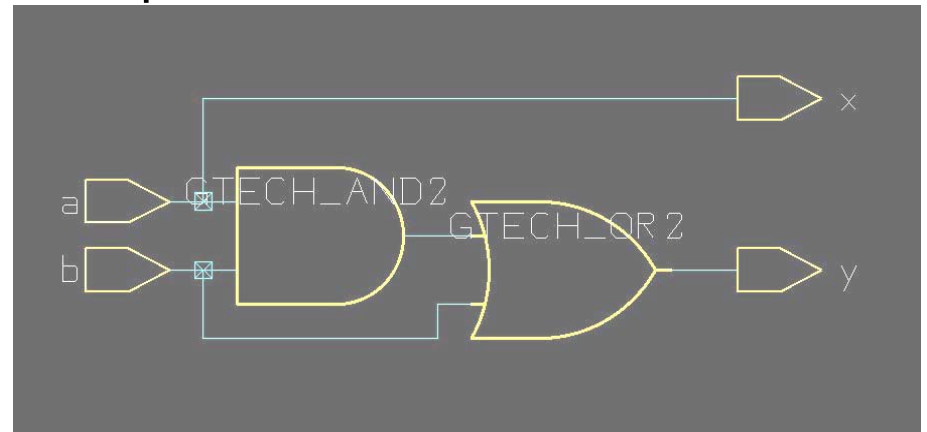

```
always @(a or b or x) begin
    x <= a & b;
    y <= x | b;
    x <= a;
end
```

may not expect

 


Combinational Always Block

19

- Sensitivity list must be specified completely, otherwise synthesis may mismatch with simulation


```
always @(a or b or c)  
  f = a&b|c;
```

```
always @(a or b)  
  f = a&b|c;
```

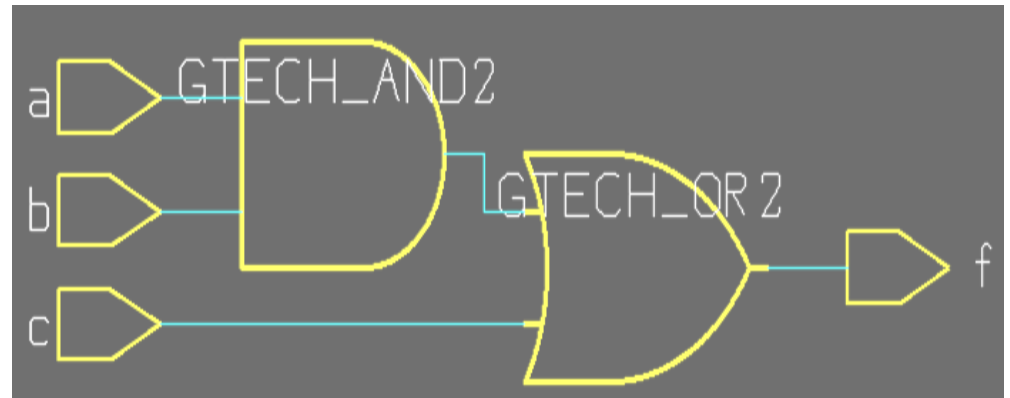

Warning: Variable 'c' is being read
in routine train line 6 in file but does not occur in the timing
control of the block which begins there. (HDL-180)

MUX with Selector Logic

 

```
module mux_logic (y, select, sig_G, sig_max,  
sig_a, sig_b);  
output y;  
input select, sig_G, sig_max, sig_a, sig_b;  
  
assign y = (select == 1) || (sig_G == 1) ||  
(sig_max == 0) ? sig_a : sig_b;  
  
endmodule
```

Note: Mux_logic has logic to determine where *sig_a* or *sig_b* is selected.

If Statement (1 / 2)

21

- What's the difference between these two coding styles?


```
module mult_if(a, b, c, d, e, sel, z);
input a, b, c, d, e;
input [3:0] sel;
output z;
reg z;
always @(a or b or c or d or e or sel)
begin
    z = e;
    if(sel[0]) z = a;
    if(sel[1]) z = b;
    if(sel[2]) z = c;
    if(sel[3]) z = d;
end
endmodule
```

```
module single_if(a, b, c, d, e, sel, z);
input a, b, c, d, e;
input [3:0] sel;
output z;
reg z;
always @(a or b or c or d or e or sel)
begin
    z = e;
    if(sel[3]) z = d;
    else if(sel[2]) z = c;
    else if(sel[1]) z = b;
    else if(sel[0]) z = a;
end
endmodule
```


If Statement (2/2)

22

mult_if

 

single_if

 

Priority / Non-Priority Circuit

23

priority
encoded

```
always @(X or Y or Z) begin
    if (Z) value = result4;
    else if (Y) value = result3;
    else if (X) value =
result2;
    else value = result1;
end
```

No priority
encoded


```
always @(X or Y or Z)
case(1`b1) //synopsys parallel_case
    X: value = result2;
    Y: value = result3;
    Z: value = result4;
    default: value = result1;
endcase
```

Case Statement (1 / 4)

24

- A case statement is called a full case if all possible branches are specified
 
```
always @(bcd) begin
  case (bcd)
    4'd0: out = 3'b001;
    4'd1: out = 3'b010;
    4'd2: out = 3'b100;
    default: out = 3'bxxx;
  endcase
end
```




Case Statement (2/4)

25

- If a case statement is not a full case, it will infer a *latch* to retain its previous value (as inferred by the semantic).
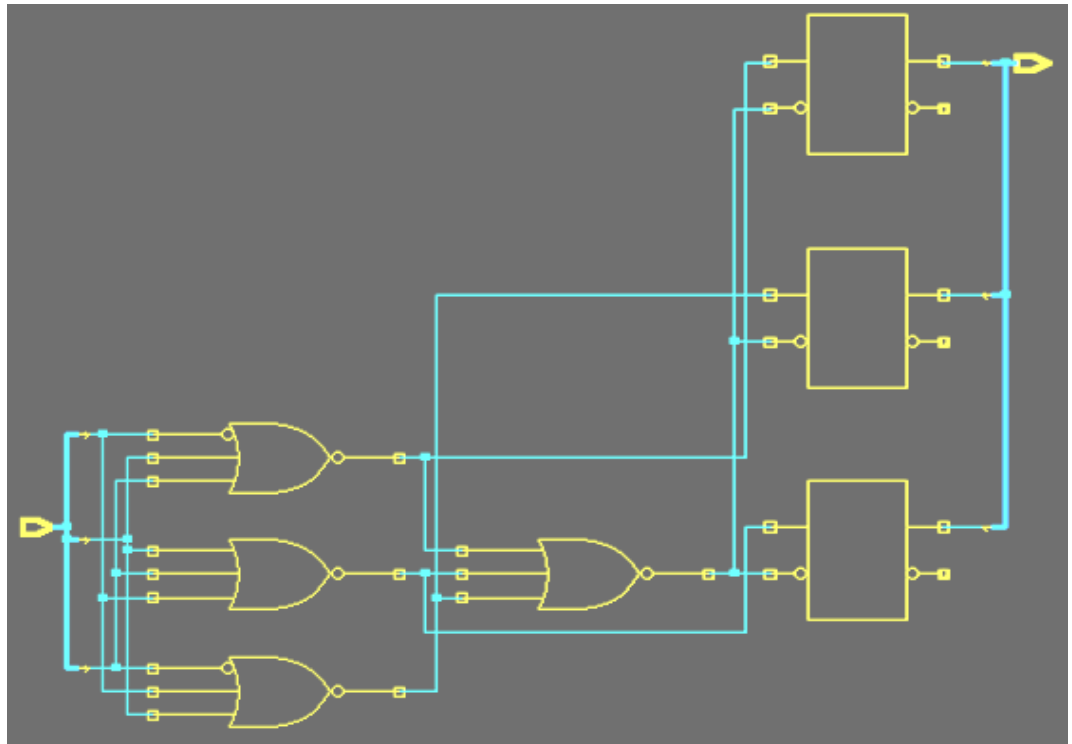
```
always @(bcd) begin
  case (bcd)
    4'd0: out = 3'b001;
    4'd1: out = 3'b010;
    4'd2: out = 3'b100;
  endcase
end
```




Case Statement (3/4)

26

- If you do not specify all possible branches, but you know the other branches will never occur, you can use “*//synopsys full_case*” directive to specify full case directive to specify full case
 
```
always @(bcd) begin
  case (bcd) //synopsys full_case
    4'd0:out=3'b001;
    4'd1:out=3'b010;
    4'd2:out=3'b100;
  endcase
end
```



Case Statement (4/4)

27

- **Note:** the second case item does not modify *reg2*, causing it to be inferred as a latch (to retain last value).

```
case (cntr_sig) // synopsys full_case
  2'b00 : begin
    reg1 = 0 ;
    reg2 = v_field ;
  end
```

```
  2'b01 : reg1 = v_field ; /* latch will be inferred for reg2 */
```

```
  2'b10 : begin
    reg1 = v_field ;
    reg2 = 0 ;
  end
endcase
```

Logical Don't-Care Conditions

28

- If the default or branch statement is an explicit assignment of an X or a Z
 - ▣ Simulation results may differ
 - ▣ Treated as don't care condition → lead to a more compacted circuit


ALU with Z1

29

```
module alu_with_z1 (alu_out, data_a, data_b,  
enable, opcode);  
  input  [2: 0] opcode;  
  input  [3: 0] data_a, data_b;  
  input          enable;  
  output         alu_out; // scalar for illustration  
  reg  [3: 0] alu_reg;
```

```
  assign alu_out = (enable == 1) ? alu_reg : 4'bz;
```

```
  always @ (opcode or data_a or data_b)  
  case (opcode)  
    3'b001: alu_reg = data_a | data_b;  
    3'b010: alu_reg = data_a ^ data_b;  
    3'b110: alu_reg = ~data_b;  
    default: alu_reg = 4'b0;  
  endcase  
endmodule
```

 


ALU with Z2

30

```
module alu_with_z1 (alu_out, data_a, data_b,  
enable, opcode);  
input  [2: 0] opcode;  
input  [3: 0] data_a, data_b;  
input    enable;  
output    alu_out;    // scalar for illustration  
reg  [3: 0] alu_reg;
```

```
assign alu_out = (enable == 1) ? alu_reg : 4'bz;
```

```
always @ (opcode or data_a or data_b  
case (opcode)  
3'b001: alu_reg = data_a | data_b;  
3'b010: alu_reg = data_a ^ data_b;  
3'b110: alu_reg = ~data_b;  
default: alu_reg = 4'bx;  
endcase  
endmodule
```

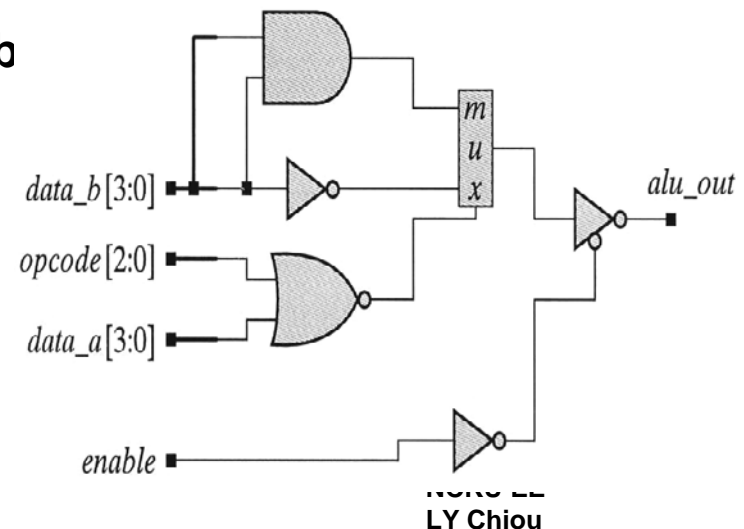

Notes for Don't Care Inference

31

- In some cases, using don't care values as default assignments can cause these problems:
 - ▣ Don't care values create a greater potential for mismatches between simulation and synthesis.
 - ▣ Defaults for variables can **hide** mistakes in the Verilog code.
 - ▣ **To a simulator, a don't care is a distinct value, different from a 1 or a 0.**
 - ▣ **In synthesis, a don't care becomes a 0 or a 1** (and hardware is built that treats the don't care value as either a 0 or a 1).
- The safest way to use don't care values is to
 - ▣ Assign don't care values only to output ports.
 - ▣ Make sure that the design never reads those don't care values.