

N26F300

VLSI SYSTEM DESIGN

(GRADUATE LEVEL)

[Material partly adapted
from lecture notes of
Prof. KJ Lee]

Fall 2010

Design of Cache

Outline

2

- **Memory Hierarchy**
- **Timing**
- **Building blocks**
- **Cache controller**
- **Test result**
- **A Complete Verilog Code**


Memories: Review

□ SRAM:

- ▣ value is stored on a pair of inverting gates
- ▣ very fast but takes up more space than DRAM (4 to 6 transistors)

□ DRAM:

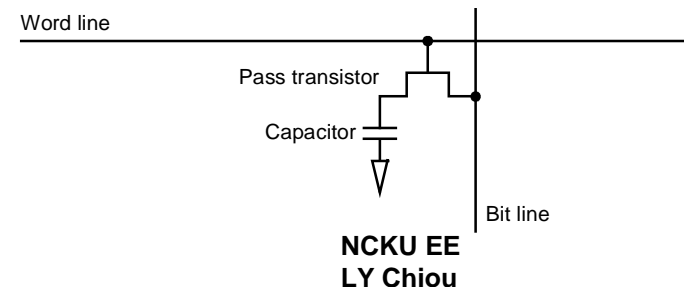- ▣ value is stored as a charge on capacitor (must be refreshed)
- ▣ very small but slower than SRAM (factor of 5 to 10)




Exploiting Memory Hierarchy

- Users want large and fast memories!
- Cost of memory varying!!

	SRAM	DRAM	DISK
Access Time (ns)	0.5 ~ 5	50 ~ 70	$(5 \sim 20) \times 10^6$
Cost (per GB)	\$10,000	\$100 to \$200	\$0.5 to \$2

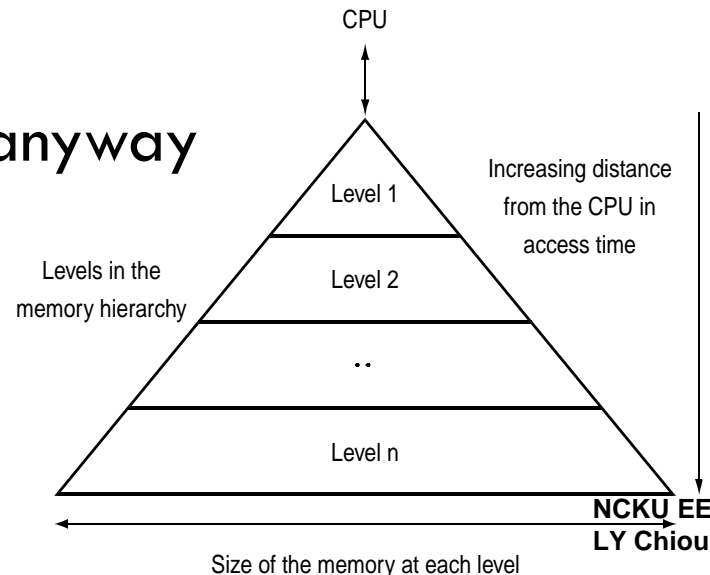- Try and give it to them anyway
 - ▣ build a memory hierarchy



Locality

- A principle that makes a memory hierarchy a good idea

- **If an item is referenced,**

temporal locality: it will tend to be referenced again soon

spatial locality: nearby items will tend to be referenced soon.

- Definition

- block: minimum unit of data
- hit: data requested is in the upper level
- miss: data requested is not in the upper level

Cache


- Two issues:
 - ▣ How do we know if a data item is in the cache?
 - ▣ If it is, how do we find it?
- Our first example:
 - ▣ block size is one word of data
 - ▣ "direct mapped"

**For each item of data at the lower level,
there is exactly one location in the cache where it might be.**

e.g., lots of items at the lower level share locations in the upper level


Direct Mapped Cache

 - Mapping: address is modulo the number of blocks in the cache



Direct Mapped Cache

□ For MIPS:

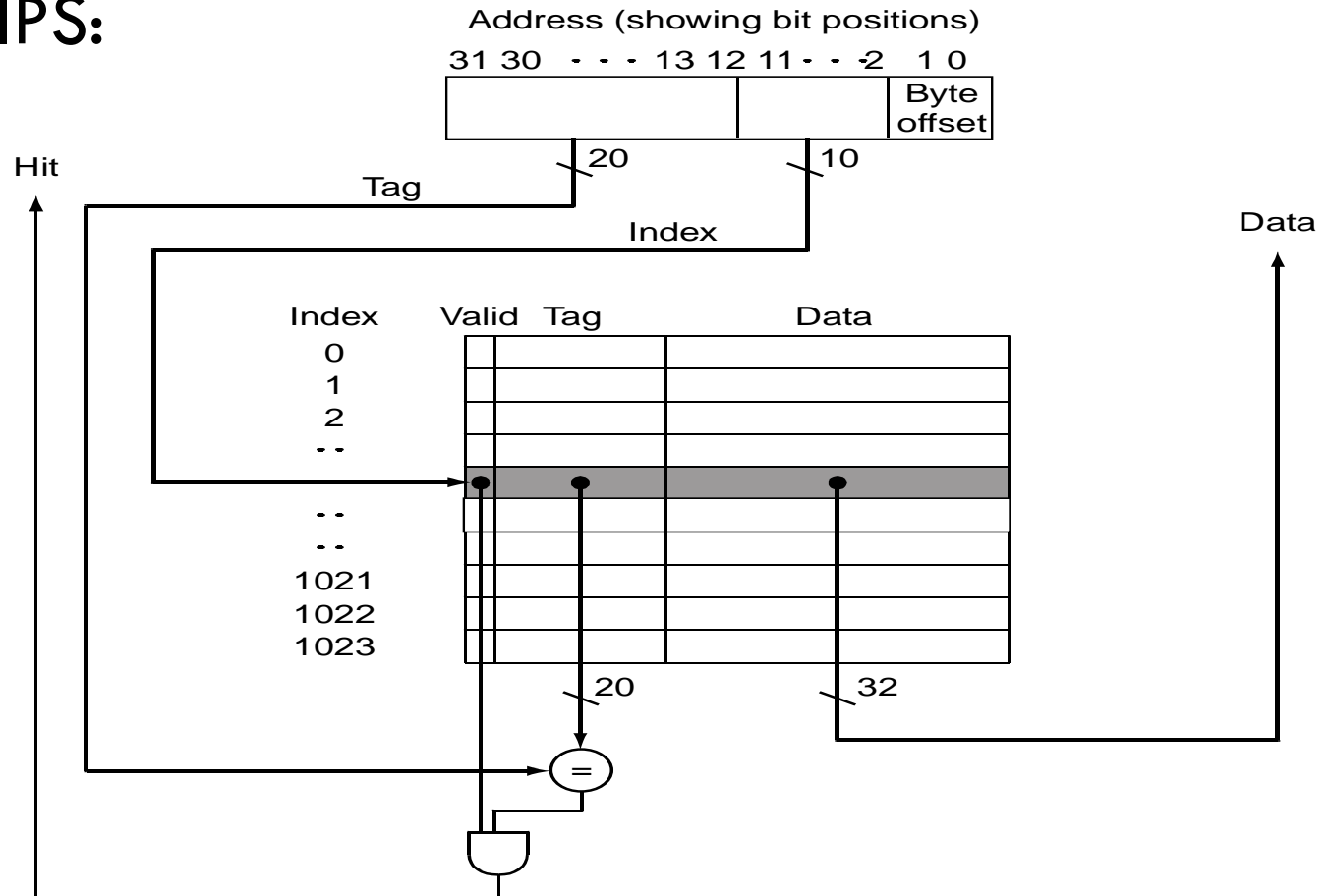


Cache Memory

- **Small, fast, local, expensive**
- **Usually static RAM.**
- **Most advanced CPUs have on_chip cache.**


Block Diagram of Cache

10

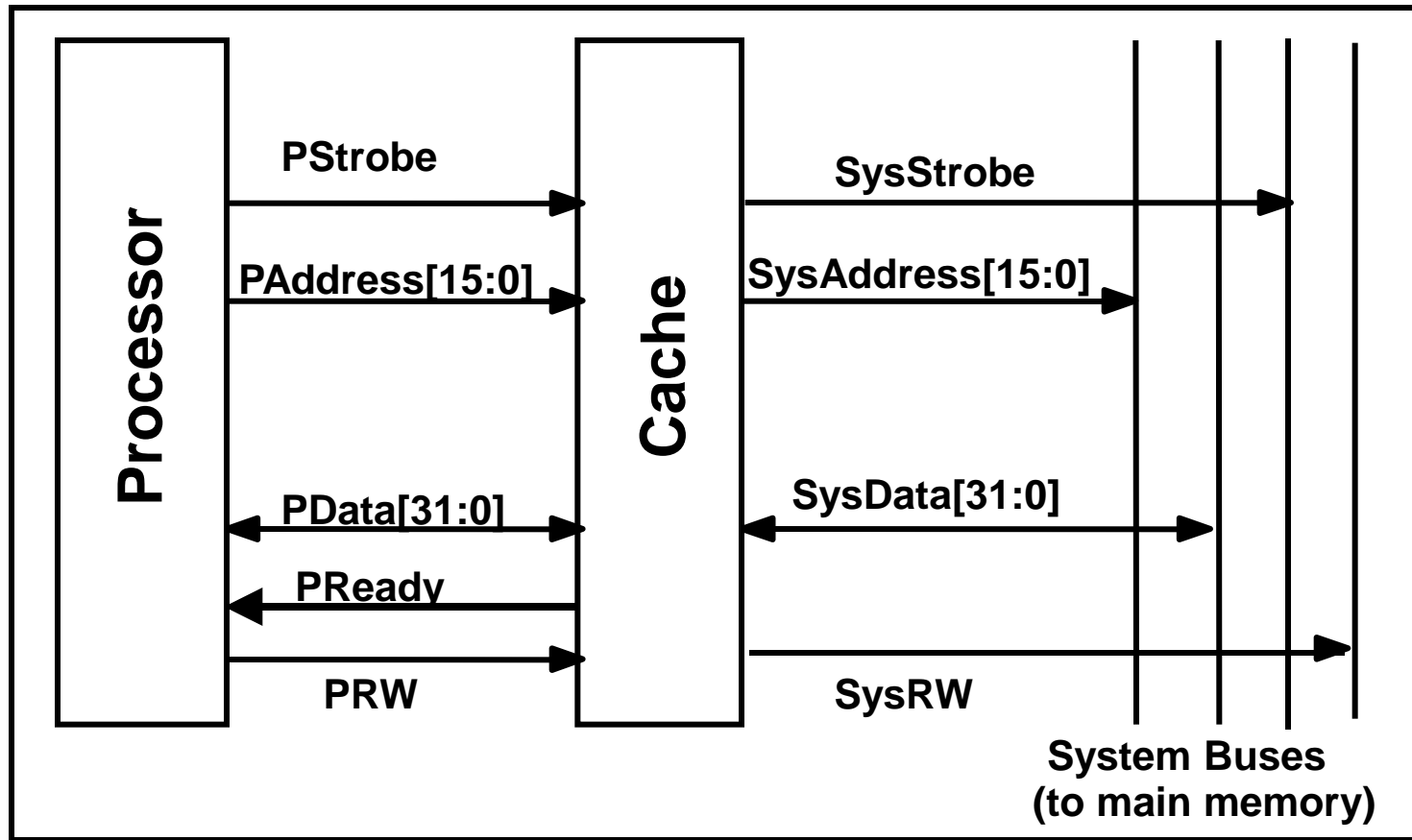


PRW=1 : read
PRW=0 : write

Timing of read operation from cache

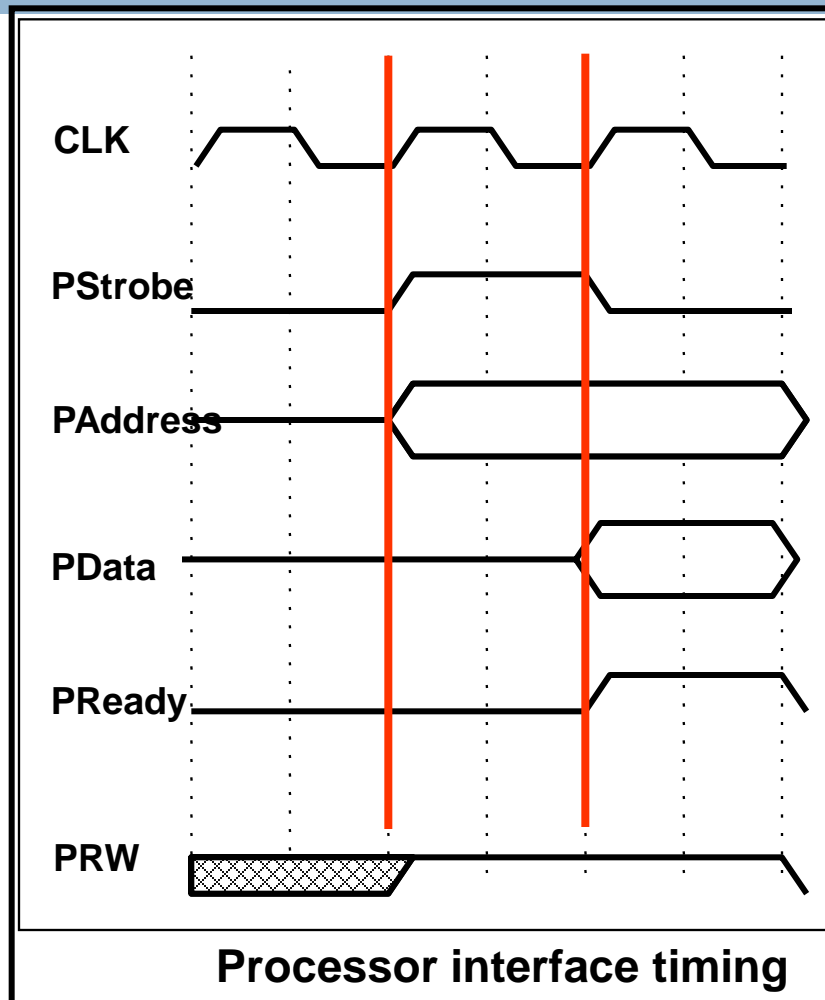

1. PStrobe is asserted by the processor when PAddress is ready and PRW is determined. (starting a bus transaction).
2. PReady is signaled to the processor when the DATA is available. (a bus transaction is completed)

Reading from main memory

 

Timing for a read cycle with one wait state

Usually a fixed number of wait states is used. ---- no ready signal.

A write operation is similar, but the data is driven onto the PData bus immediately by the Cache and then is held a number of wait states before another write operation is issued.


SysRW = 1 : read

SysRW = 0 : write

A Cache Example


- 64K main memory, 1K cache
- Direct mapping
- Write-through policy

Address field:

 


Only one word will be updated at a time in this design

 - Each location in the cache is mapped to 64 different locations in the memory.




Mapping between main memory and cache


Structure of a Typical Cache

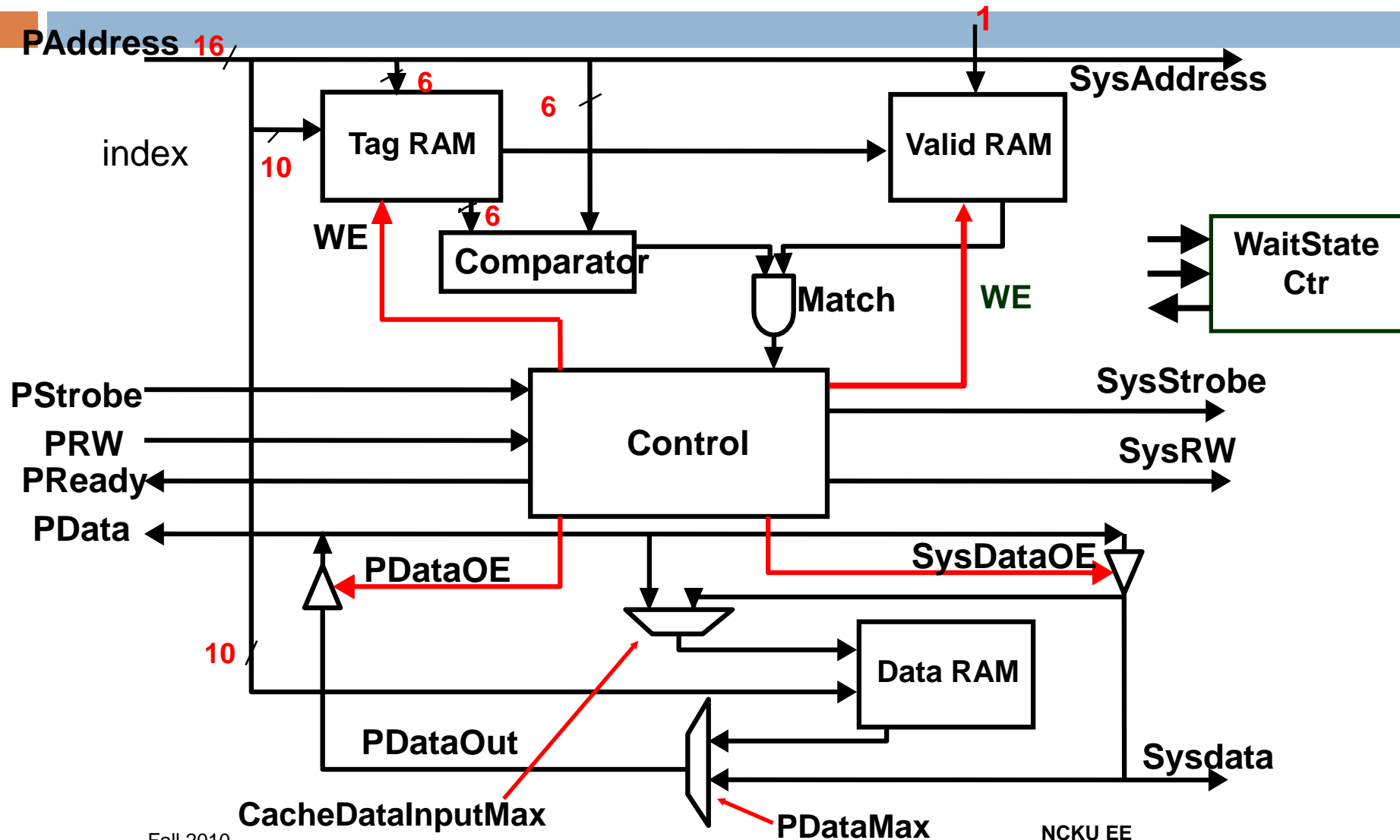

Operation of Cache (Read from Cache)

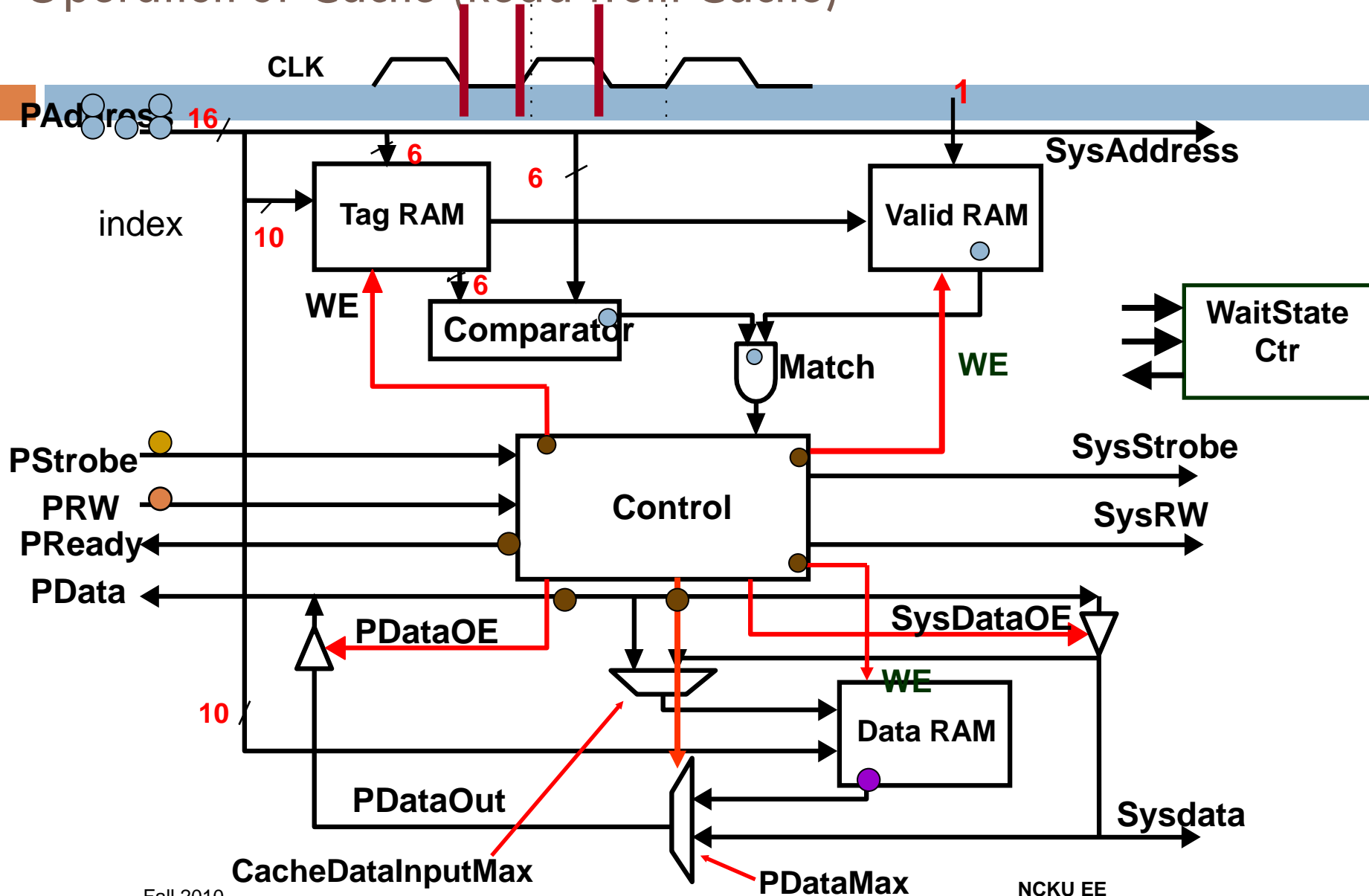

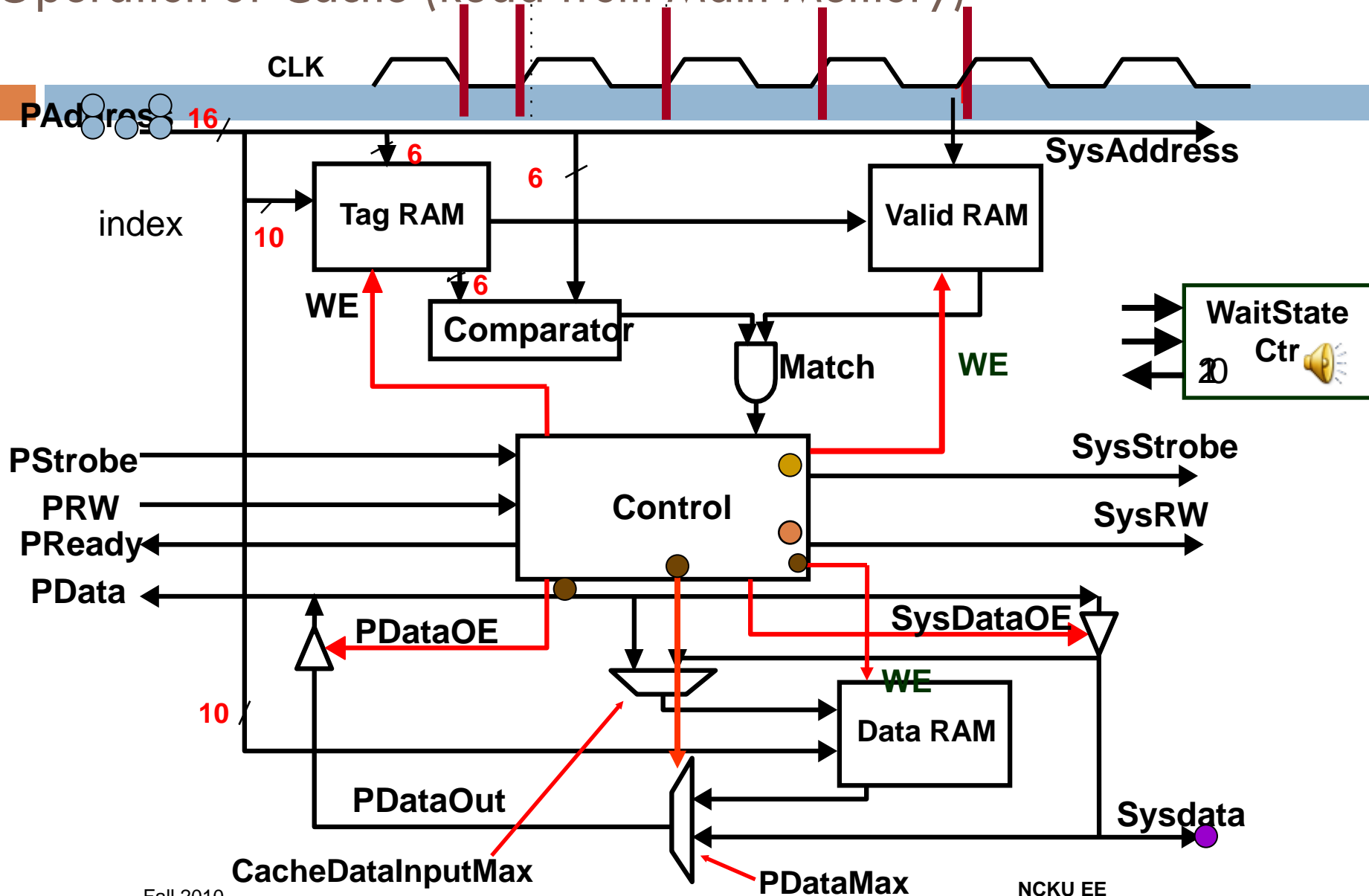Operation of Cache (Read from Main Memory)



Main Cache Module (1/3)

```
`define READ 1
`define WRITE 0
`define CACHESIZE 1024
`define WAITSTATES 2
//number of wait states
// required for system accesses
`define ADDR 15:0
`define INDEX 9:0
`define TAG 15:10
`define DATAWIDTH 32
`define DATA `DATAWIDTH-1:0
`define PRESENT 1
`define ABSENT !`PRESENT
module cache(
    PStrobe, PAddress,
    PData, PRW,
    PReady,
    SysStrobe, SysAddress,
    SysData, SysRW,
    Reset,
    Clk    );
```

```
Input PStrobe;
input [`ADDR] PAddress;
inout [`DATA] PData;
input    PRW;
output   PReady;

output   SysStrobe;
output   [`ADDR] SysAddress;
input    [`DATA] SysData;
output   SysRW;
input    Reset;
input    Clk;

//Bidirectional buses
wire PDataOE;
wire SysDataOE;
wire [`DATA] PDataOut;
wire [`DATA] PData=PDataOE ? PDataOut : 'bz;
wire [`DATA] SysData=SysDataOE? PData : 'bz;
wire [`ADDR] SysAddress = PAddress;
wire [`TAG]  TagRamTag;
```

Main Cache Module (2/3)

```
TagRam TagRam (  
    .Address (PAddress[`INDEX]),  
    .TagIn   (PAddress[`TAG]),  
    .TagOut  (TagRAMTag[`TAG]),  
    .Write   (Write),  
    .Clk     (Clk)
```

```
);
```

```
ValidRam ValidRam(  
    .Address (PAddress[`INDEX]),  
    .ValidIn  (1`b1),  
    .ValidOut (Valid),  
    .Write    (Write),  
    .Reset    (Reset),  
    .Clk      (Clk)
```

```
);
```

```
wire [`DATA] DataRamDataOut;
```

```
wire [`DATA] DataRamDataIn;
```

```
DataMux CacheDataInputMux(  
    .S(CacheDataSelect),  
    .A(SysData),  
    .B(Pdata),  
    .Z(DataRamDataIn)  
);
```

```
DataMux PDataMax(  
    .S(PDataSelect),  
    .A(SysData),  
    .B(DataRamDataOut),  
    .Z(PDataOut)  
);
```

Main Cache Module

(3/3)


```
DataRam DataRam (
    .Address(PAddress[INDEX
]),
    .DataIn  (DataRamDataIn),
    .DataOut (DataRamDataOut),
    .Write   (Write),
    .Clk     (Clk)
);
```

```
Comparator Comparator (
    .Tag1 (PAddress[TAG]),
    .Tag2 (TagRamTag),
    .Match (Match)
);
```

```
Control Control (
    .PStrobe(PStrobe),
    .PRW     (PRW),
    .Pready  (PReady),
    .Match   (Match),
    .Valid   (Valid),
    .CacheDataSelect(CacheDataSelect),
    .PDataSelect (PDataSelect),
    .SysDataOE   (SysDataOE),
    .Write       (Write),
    .PDataOE     (PDataOE),
    .SysStrobe   (SysStrobe),
    .SysRW       (SysRW),
    .Reset       (Reset),
    .Clk         (Clk)
);
```

endmodule

Tag RAM and Valid Bit

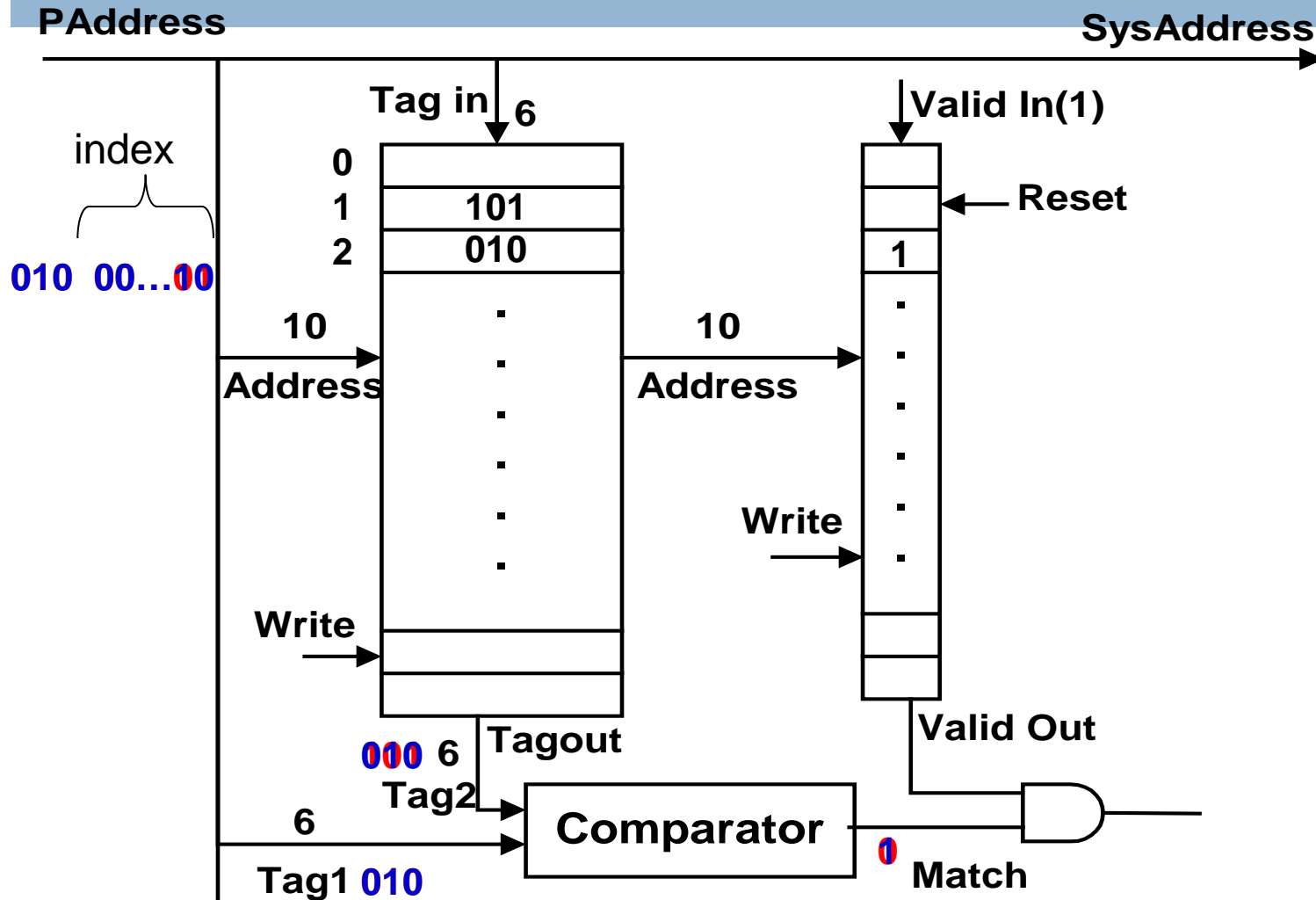

Tag RAM Module

```
module TagRam(Address, TagIn, TagOut, Write, Clk);

input  [`INDEX]Address;
input  [`TAG]  TagIn;
output [`TAG]  TagOut;
input          Write;
input          Clk;

reg  [`TAG]  TagOut;
reg  [`TAG]  TagRam  [0:`CACHESIZE-1];

always @ (negedge Clk)
    if (Write)
        TagRam[Address]=TagIn; // write

always @ (posedge Clk)
    TagOut = TagRam[Address]; // read
endmodule
```

Valid RAM module

```
module ValidRam (Address, ValidIn, ValidOut, Write,
                Reset, Clk );
    input  [`INDEX]      Address;
    input                ValidIn;
    output               validOut;
    input                Write;
    input                Reset;
    input                Clk;
    reg                 ValidOut;
    reg  [`CACHE_SIZE-1:0] ValidBits;
    integer i;
    always @ (negedge Clk) // Write
        if (Write && !Reset)
            ValidBits[Address]=ValidIn; // write
        else if (Reset)
            for (i=0;i<`CACHE_SIZE;i=i+1)
                ValidBits[i]=`ABSENT; //reset
    always @ (posedge Clk)
        ValidOut = ValidBits[Address]; // read
```

- A single bit for each index location indicating whether that location contains valid data.
- The main difference between the ValidRAM model and the TagRAM model is that all bits in ValidBits need to be reset to zero when Reset is asserted.

Comparator module

```
module Comparator (Tag1, Tag2, Match);  
  input  [`TAG]      Tag1;  
  input  [`TAG]      Tag2;  
  output                      Match;  
  wire    Match = (Tag1 == Tag2);  
endmodule
```

- The “==” is used rather than “===” so that unknown values are propagated to the Match output correctly.

Cache Data RAM module


```
module DataRam(Address, DataIn, DataOut, Write, Clk);
input  [`INDEX]  Address;
input  [`DATA]   DataIn;
output [`DATA]   DataOut;
input   Write;
input   Clk;
reg     [`DATA]  DataOut;
reg     [`DATA]  DataRam [`CACHESIZE-1:0];
always @ (negedge Clk)
    if (Write)
        DataRam[Address]=DataIn; // write
always @ (posedge Clk)
    DataOut = DataRam [Address]; // read
endmodule
```

- The Data RAM is identical in function and timing to the Tag RAM except that it is 32 bits wide.

Cache controller

1. Read Hit: return data from cache.

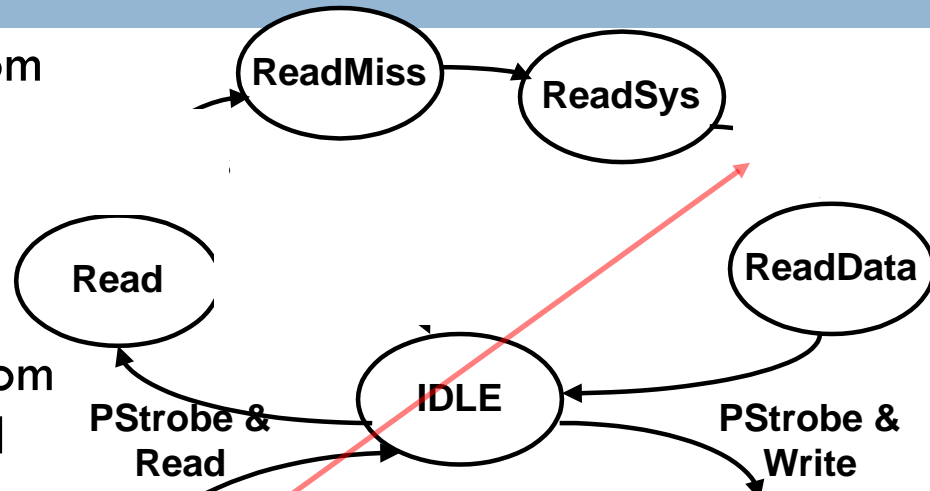2. Read Miss: fetch data from memory: return data and update cache.




Note that a counter is used to count the number of wait states

Cache controller

3. Write Hit: write to cache and to memory.

4. Write Miss: write to memory only.

 

Note that a counter is used to count the number of wait states

Brief Description of Controller (I)

- **Step 1:** During IDLE, the state machine waits for the processor to start a cycle via **Pstrobe**.
 - The signal is sampled at the **rising edge of the clock**.
- **Step 2:** When **Pstrobe** is asserted, the address is looked up in the cache.
 - If the tag **TagRAM** for this address matches the tag of the current processor address and the corresponding **ValidBit** is set, the data for this address is in the cache.
 - Based on whether the data is in cache and the **state** of the **PRW** line, the correct subsequent actions are determined.
- All transactions on the system bus take a pre-defined number of cycles regardless of the type of transaction.
- During each bus operation, the **wait state counter** is loaded.
 - The state machine does not advance state until the counter has overflowed.
 - The number of wait states is defined by the identifier **WAITSTATES**.
- At the end of each bus transaction, the controller asserts **PReady** for one cycle to indicate to the processor that the transaction is finished.

Brief Description of Controller (II)

- **Read Hit:** Happens most often due to locality of reference and more reads than writes.
 - In the cycle following the **PStrobe**, data is returned to the processor from the **Data RAM** along with the assertion of **PReady**.
- **Read Miss:** A miss occurs if the location in the cache corresponding to current **PAddress** is either **invalid** or contains data for a **different** address.
 - A memory cycle reads data from the main memory (after passing **wait state**).
 - The Tag RAM is updated to reflect the tag of the new data and **ValidBit** is set.
- **Write Hit:** Since the cache protocol is **write-through**, both cache and main memory must be updated.
 - A write cycle is performed on the system bus at the same time that data is written to the cache.
 - **PReady** is returned to the processor to indicate the completion of transaction.
- **Write Miss:** Only the main memory is updated.
 - This policy is chosen because the data read is most likely to be used again than the data is written.
 - It performs a write to memory only and returns **PReady** when the bus transaction is complete.

Cache Controller Module

30

```

module Control (
    PStrobe, PRW, PReady,
    Match, Valid, Write,
    CacheDataSelect,
    PDataSelect, SysDataOE,
    PDataOE,
    SysStrobe, SysRW, Reset,
    ph1, ph2 );

input      PStrobe, PRW;
output    PReady;
input     Match, Valid;
output    Write;
output    CacheDataSelect;
output    PDataSelect;
output    SysDataOE, PDataOE;
output    SysStrobe, SysRW;
input     Reset, Clk;
    
```

```

wire [1:0] WaitStateCtrInput =
    `WAITSTATES - 1;
reg  LoadWaitStateCtr;

WaitStateCtr WaitStateCtr(
    .load (LoadWaitStateCtr),
    .LoadValue (WaitStateCtrInput),
    .Carry (WaitStateCtrCarry),
    .Ph1 (Ph1),
    .Ph2 (Ph2) );

reg PReadyEnable;
reg SysStrobe, SysRW;
reg SysDataOE;
reg Write, Ready;
reg CacheDataSelect;
reg PDataSelect, PDataOE;
reg [3:0] State, NextState;
    
```

Cont'd

Cache Controller Module (cont.)

31

```
initial State = 0;
```

```
parameter
```

```
    STATE_IDLE = 0 ,  
    STATE_READ = 1,  
    STATE_READMISS = 2,  
    STATE_READSYS = 3,  
    STATE_READDATA = 4,  
    STATE_WRITE = 5,  
    STATE_WRITEHIT = 6,  
    STATE_WRITEMISS = 7,  
    STATE_WRITESYS = 8,  
    STATE_WRITEDATA = 9;
```

Cont'd

.

```

always @ (posedge Clk)
    State = NextState;

always @ (State)
    if (Reset) NextState = `STATE_IDLE;
    else
        case (State)
            STATE_IDLE: begin
                if (PStrobe && PRW)
                    NextState = `STATE_READ;
                else if (PStrobe && !PRW)
                    NextState = `STATE_WRITE;
            end
            STATE_READ : begin
                if (Match && Valid)
                    NextState = `STATE_IDLE;
                    //read hit
                else
                    NextState = STATE_READMISS;
                    $display ("state = read");
            end
        end
    end

```

```

STATE_READMISS : begin
    NextState = `STATE_READSYS;
    $display("state = readmiss");
end
STATE_READSYS : begin
    if (WaitStateCtrCarry)
        NextState = `STATE_READDATA;
    else NextState = `STATE_READSYS;
    $display ("state = readsys");
end
STATE_READDATA : begin
    NextState = `STATE_IDLE;
    $display ("state = readdata");
end
STATE_WRITE : begin
    if (Match && Valid)
        NextState = `STATE_WRITEHIT;
    else NextState = `STATE_WRITEMISS;
    $display ("state = WRITE");
end

```

Cont'd

```

`STATE_WRITEHIT : begin
    NextState = `STATE_WRITESYS;
    $display ("state = WRITEHIT");
end
`STATE_WRITEMISS : begin
    NextState = `STATE_WRITESYS;
    $display ("state = WRITEmiss");
end
`STATE_WRITESYS : begin
    if (WaitStateCtrCarry)
        NextState = `STATE_WRITEDATA;
    else
        NextState = `STATE_WRITESYS;
    $display ("state = WRITESys");
end
`STATE_WRITEDATA : begin
    NextState = `STATE_IDLE;
    $display ("State = WRITEdata");
end
endcase

```

```

task OutputVec;
input [9:0] vector;
begin
    LoadWaitStateCtr=vector[9];
    PReadyEnable=vector[8];
    Ready=vector[7];
    Write=vector[6];
    SysStrobe=vector[5];
    SysRW=vector[4];
    CacheDataSelect=vector[3]
    PDataSelect=vector[2]
    PDataOE=vector[1]
    SysDataOE=vector[0];
end
endtask

```

Cont'd


```

always @ (State)
case (State)
    9876543210
    `STATE_IDLE:      OutputVec(10`b0000000000);
    `STATE_READ:      OutputVec(10`b0100000010);
    `STATE_READMISS:   OutputVec(10`b1000110010);
    `STATE_READSYS:    OutputVec(10`b0000010010);
    `STATE_READDATA:   OutputVec(10`b0011011110);
    `STATE_WRITEHIT:   OutputVec(10`b1001101100);
    `STATE_WRITE:      OutputVec(10`b0100000000);
    `STATE_WRITEMISS:  OutputVec(10`b1000100001);
    `STATE_WRITESYS:   OutputVec(10`b0000000001);
    `STATE_WRITEDATA:  OutputVec(10`b0011001101);
endcase
9876543210
wire PReady = (PReadyEnable && Match && Valid)
               || Ready;
endmodule

```

System ready
Cache ready

```


LoadWaitStateCtr=vector[9];
PReadyEnable=vector[8];
Ready=vector[7];
Write=vector[6];
SysStrobe=vector[5];
SysRW=vector[4];
CacheDataSelect=vector[3]
PDataSelect=vector[2]
PDataOE=vector[1]
SysDataOE=vector[0];

```

Result of a Short Test

35

1.WM(miss), 2.RD(miss), 3.RD(hit)

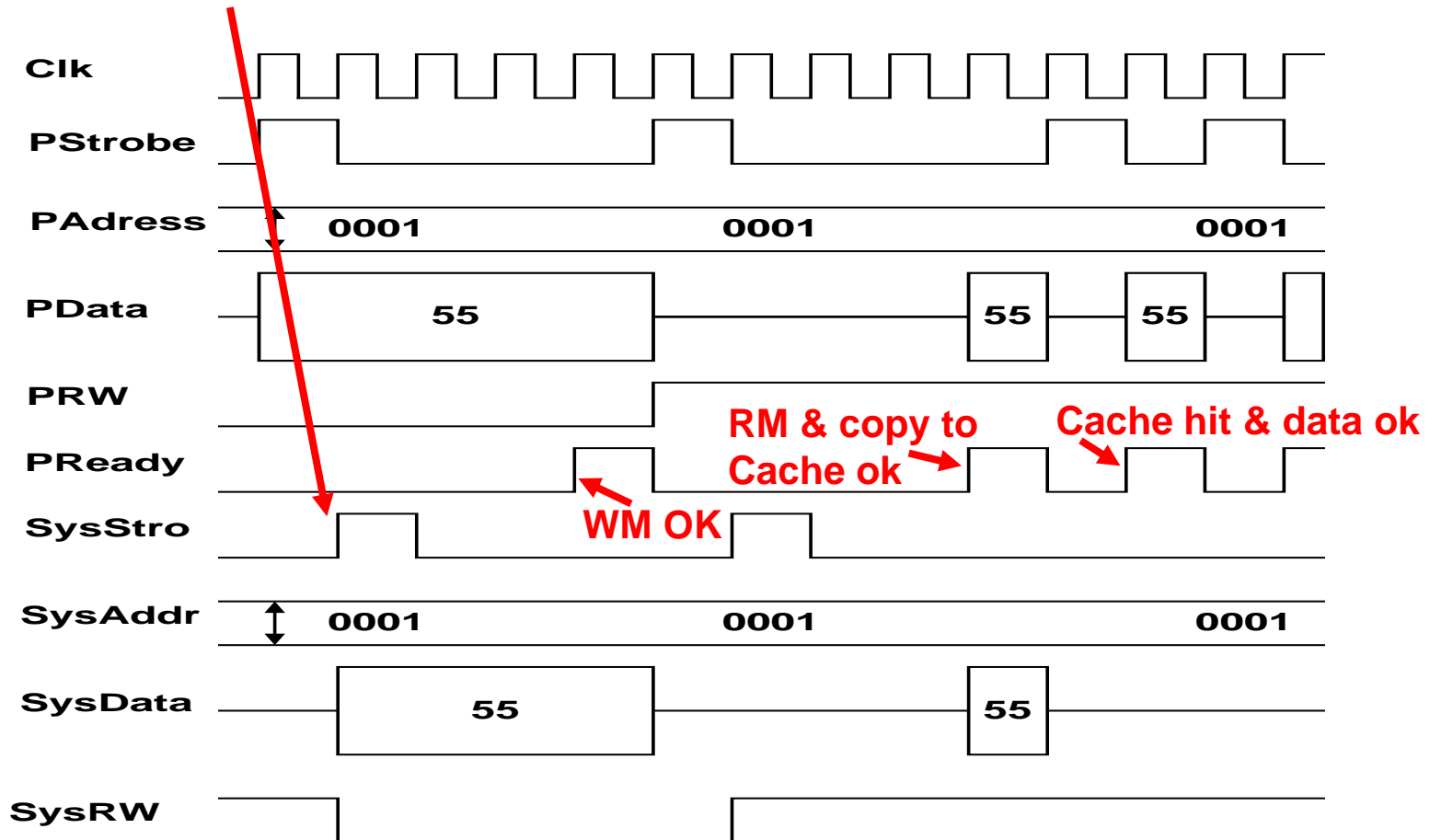

Modeling Cache Memories

```
//Defines
`define READ 1'b1
`define WRITE 1'b0
`define CACHESIZE 1024
`define WAITSTATE 2'd2
`define ADDR 15:0
`define ADDRWIDTH 16
`define INDEX 9:0
`define TAG 15:10
`define DATA 31:0
`define DATAWIDTH 32
`define PRESENT 1'b1
`define ABSENT !`PRESENT

module cache(
    PStrobe, Paddress,
    PData, PRW, PReady,
```

```
SysStrobe, SysAddress,
SysData, SysRW,
Reset, Clk
);
input  PStrobe;
input  [`ADDR] PAddress;
input  [`DATA] PData;
input  PRW;
output PReady;

output SysStrobe;
output [`ADDR] SysAddress;
input  [`DATA] SysData;
output SysRW;
input  Reset;
input  Clk;
```

continued

```

// Bidirectional Buses
wire PDataOE;
wire SysDataOE;
wire [`DATA] PDataOut;
wire [`DATA] PData = PDataOE ?
    PDataOut :
    `DATAWIDTH`bz;
wire [`DATA] SysData = SysDataOE ?
    PData : `DATAWIDTH`bz;

wire [`ADDR] SysAddress =
    PAddress;
wire [`TAG]    TagRamTag;

wire    Write;
wire    Valid;
wire    CacheDataSelect;
wire    PDataSelect;
wire    Match;

```

```

TagRam TagRam(
    .Address (PAddress[`INDEX]),
    .TagIn    (PAddress[`TAG]),
    .TagOut   (TagRamTag[`TAG]),
    .Write    (Write),
    .Clk      (Clk)
);

ValidTam ValidRam(
    .Address
    (PAddress[`INDEX]),
    .ValidIn  (1`b1),
    .ValidOut (Valid),
    .Write    (Write),
    .Reset    (Reset),
    .Clk      (Clk)
);

```

continued

```

wire[ DATA] DataRamDataOut;
wire[ DATA] DataRamDataIn;
DataMux CacheDataInputMux(
    .S      (CacheDataSelect),
    .A      (SysData),
    .B      (PData),
    .Z      (DataRamDataIn)
);
DataMux PDataMux(
    .S      (PDataSelect),
    .A      (SysData),
    .B      (DataRamDataOut),
    .Z      (PDataOut)
);
DataRam DataRam(
    .Address (PAddress[ INDEX]),
    .DataIn  (DataRamDataIn),
    .DataOut (DataRamDataOut),
    .Write   (Write),
    .Clk     (Clk)
);

```

```

Comparator Comparator(
    .Tag1    (PAddress[ TAG]),
    .Tag2    (TagRamTag),
    .Match   (Match)
);
Control Control(
    .PStrobe      (PStrobe),
    .PRW          (PRW),
    .PReady       (PReady),
    .Match(Match),
    .Valid (Valid),
    .CacheDataSelect (CacheDataSelect),
    .PDataSelect (PDataSelect),
    .SysDataOE    (SysDataOE),
    .Write (Write),
    .PDataOE      (PDataOE),
    .SysStrobe    (SysStrobe),
    .SysRW        (SysRW),
    .Reset (Reset),
    Clk    (Clk)
);
endmodule

```

continued

```

module Control(
    PStrobe, PRW, Ready,
    Match, Valid, Write,
    CacheDataSelect,
    PDataSelect,
    SysDataOE, PDataOE,
    SysStrobe, SysRW, Reset,
    Clk,
);

```

```

input PStrobe, PRW;
output PReady;
input Match, Valid;
output Write;
output CacheDataSelect;
output PDataSelect;
output SysDataOE, PDataOE;
output SysStrobe, SysRW;
input Reset;
input Clk;

```

```

wire [1:0] WaitStateCtrInput =
    `WAITSTATES -2`d1;
wire WaitStateCtrCarry;
reg LoadWaitStateCtr;

```

```

WaitStateCtr WaitStateCtr(
    .Load (LoadWaitStateCtr),
    .LoadValue (WaitStateCtrCarry),
    .Carry (WaitStateCtrCarry),
    .Clk (Clk)
);
reg PReadyEnable;
reg SysStrobe, SysRW;
reg SysDataOE;
reg Write;
reg Ready;
reg CacheDataSelect, PDataSelect;
reg PDataOE;
reg [3:0] State; nextState

```

continued

```
reg[3:0]NextState;
```

```
`define STATE_IDLE      4`d0
`define STATE_READ      4`d1
`define STATE_READMISS  4`d2
`define STATE_READSYS   4`d3
`define STATE_READDATA  4`d4
`define STATE_WRITE     4`d5
`define STATE_WRITEHIT  4`d6
`define STATE_WRITEMISS 4`d7
`define STATE_WRITESYS  4`d8
`define STATE_WRITEDATA 4`d9
```

```
always @ (posedge Clk)
    State = Reset ?
        `STATE_IDLE : NextState;
```

```
always @ (State or PStrobe or
    PRW or Match or
    Valid or WaitStateCtrCarry)
```

```
Case (State)
```

```
`STATE_IDLE: begin
    if (PStrobe && PRW == `READ)
        NextState = `STATE_READ;
    else if (PStrobe && PRW == `WRITE)
        NextState = `STATE_WRITE;
    else NextState = `STATE_IDLE;
end
`STATE_READ : begin
    if (Match && Valid)
        NextState = `STATE_IDLE;
    else NextState = `STATE_READMISS;
end
`STATE_READMISS : begin
    NextState = `STATE_READSYS;
end
`STATE_READSYS : begin
    if(WaitStateCtrCarry)
        NextState = `STATE_READDATA;
    else NextState = `STATE_READSYS;
end
```

continued

```

`STATE_READDATA : begin
    NextState = `STATE_IDEL;
end
`STATE_WRITE : begin
    if (Match && Valid)
        NextState = `STATE_WRITEHIT;
    else
        NextState = `STATE_READMISS;
    end
end
`STATE_WRITEHIT : begin
    NextState = `STATE_WRITESYS;
end
`STATE_WRITEMISS : begin
    NextState = `STATE_WRITESYS;
end
`STATE_WRITESYS : begin
    if (WaitStateCtrCarry)
        NextState = `STATE_WRITEDATA;
    else NextState = `STATE_WRITESYS;
end

```

```

`STATE_WRITEDATA : begin
    NextState = `STATE_IDLE;
end
default:NextState = `STATE_IDLE;
endcase
task OutputVec;
input [9:0] vector;
begin
    {LoadWaitStateCtr, PReadyEnable,
    Ready, Write, SysStrobe, SysRW,
    CacheDataSelect,
    DataSelect,PDataOE, SysDataOE} =
    vector;
end
endtask

```

continued


```

always @ (State)
case (State)
  `STATE_IDLE:          OutputVec(10`b0000000000);
  `STATE_READ:   OutputVec(10`b0100000010);
  `STATE_READMISS:      OutputVec(10`b1000110010);
  `STATE_READSYS:       OutputVec(10`b0000010010);
  `STATE_READDATA:      OutputVec(10`b0011011110);
  `STATE_WRITEHIT:      OutputVec(10`b1001101100);
  `STATE_WRITE:   OutputVec(10`b0100000000);
  `STATE_WRITEMISS:     OutputVec(10`b1000100001);
  `STATE_WRITESYS:      OutputVec(10`b0000000001);
  `STATE_WRITEDATA:     OutputVec(10`b0011001101);
  default:              OutputVec(10`b0000000000);
endcase

wire PReady = (PReadyEnable && Match && Valid) || Ready;

endmodule

module DataMux(S, A, B, Z);
  input S; //Select Line
  input [ `DATA] A, B, Z;
  wire [ `DATA] Z = S ? A: B;
endmodule

```

continued

```
module WaitStateCtr(Load,  
                    LoadValue, Carry, Clk);
```

```
input Load;  
input [1:0] LoadValue;  
output Carry;  
input Clk;  
reg [1:0] Count;
```

```
always @ (posedge Clk)  
    if (Load)  
        Count = LoadValue;  
    else  
        Count = Count - 2'b1;
```

```
    wire Carry = Count == 2'b0;  
endmodule
```

```
module TagRam(Address, TagIn, TagOut,  
              Write, Clk);
```

```
input [`INDEX]Address;  
input [`TAG] TagIn;  
output [`TAG] TagOut;  
input Write;  
input Clk;
```

```
reg [`TAG] TagOut;  
reg [`TAG] TagRam [`CACHESIZE-1:0];
```

```
always @ (negedge Clk)  
    if (Write) TagRam[Address]=TagIn; //write
```

```
always @ (posedge Clk)  
    TagOut = TagRam[Address]; //read  
endmodule
```

continued

```

module ValidRam(
    Address,
    ValidIn,
    ValidOut,
    Write,
    Reset,
    Clk
);
input    [`INDEX]Address;
input    ValidIn;
output   ValidOut;
input    Write;
input    Reset;
input    Clk;

reg ValidOut;
reg [`CACHESIZE-1:0] ValidBits;

integer i;

```

```

always @ (posedge Clk)
    if (Write && !Reset)
        ValidBits[Address]=ValidIn; // write
    else if (Reset)
        for (i=0; i<`CACHESIZE;i=i+1)
            ValidBits[i]=`ABSENT; //reset

always @ (posedge Clk)
    validOut = ValidBits[Address]; //read

endmodule

```

continued

```
module DataRam(Address, DataIn,  
                DataOut, Write, Clk);
```

```
input    [`INDEX] Address;  
input    [`DATA] DataIn;  
output   [`DATA] DataOut;  
input    Write;  
input    Clk;
```

```
reg [`DATA] Dataout;  
reg [`Data] Ram [`CACHESIZE-1:0];
```

```
always @ (posedge Clk)  
    if(Write)  
        Ram[Address]=DataIn; //write
```

```
    always @ (posedge Clk)  
        DataOut = Ram[Address]; //read  
endmodule
```

```
module Comparator(Tag1, Tag2,  
                  Match);
```


```
input [`TAG] Tag1;  
input [`TAG] Tag2;  
output Match;
```

```
wire Match = Tag1 == Tag2;
```

```
endmodule
```

2-Way Cache Organization

46

 

4-Way Cache Organization

