

N26F300
VLSI SYSTEM DESIGN
(GRADUATE LEVEL)

Fall 2010

Verilog (III)

Outline

2

- Behavioral Modeling Examples of Combinational Logic and Sequential Logic
- Tasks and Functions

Behavioral Modeling Examples

Multiplexor, Decoder, Priority Encoder

Adder, Parity Checker

Counter, Shifter

SSRAM

FIFO

Multiplexor

4

Net-list (gate-level)

```
module
mux2_1(out,a,b,sel)
  output out;
  input a,b,sel;
  not(sel_,sel);


  and(a1,a,sel_);
  and(b1,b,sel);
  or(out,a1,b1);
endmodule
```

Continuous assignment

```
module
mux2_1(out,a,b,sel)
  output out;
  input a,b,sel;
  assign out=
    (a&~sel)|(b&sel);
endmodule
```

RTL modeling
 
```
module
mux2_1(out,a,b,sel)
  output out;
  input a,b,sel;
  always @(a or b or sel)
  if (sel)
    out = b;
  else
    out = a;
endmodule
```



4-to-1 multiplexor

5

Continuous Assignment

• 4-to-1 multiplexor

```
module
mux4_1(out,in0,in1,in2,in3,sel) ;
    output out ;
    input in0,in1,in2,in3 ;
    input[1:0]sel ;
    assign out =
        (sel ==2'b00)? in0 :
        (sel ==2'b01)? in1 :
        (sel ==2'b10)? in2 :
        (sel ==2'b11)? in3 :
        1'bx;
endmodule
```

RTL

• 4-to-1 multiplexor

```
module mux4_1(out,in,sel) ;
    output out ;
    input[3:0] in ;
    input[1:0] sel ;
    reg out ;
    always @(sel or in)
    begin
        case(sel)
            2'd0: out = in[0];
            2'd1: out = in[1];
            2'd2: out = in[2];
            2'd3: out = in[3];
            default: 1'bx;
        endcase
    end
endmodule
```

```
always @(sel or in) out = in[sel];
```

Conditional Statements

6

□ Case Statement (in procedural block)

case (opcode)

3'b000 : result = rega + regb;

3'b001 : result = rega - regb;

3'b010 : result = rega * regb;

3'b100 : result = rega / regb;

default : begin

result = 'bx;

\$display ("no match");

end

endcase

Decoder

- **3-to-8 decoder with enable control**

```
module decoder(out,enb_,sel) ;  
    output [7:0] out ;  
    input enb_ ;  
    input [2:0] sel ;  
    reg [7:0] out ;  
    always @ (enb_ or sel)  
        if(enb_)  
            out = 8'b1111_1111 ;  
        else  
            case(sel)  
                3'b000:out=8'b1111_1110 ;  
                3'b001:out=8'b1111_1101 ;  
                3'b010:out=8'b1111_1011 ;  
                3'b011:out=8'b1111_0111 ;  
                3'b100:out=8'b1110_1111 ;  
                3'b101:out=8'b1101_1111 ;  
                3'b110:out=8'b1011_1111 ;  
                3'b111:out=8'b0111_1111 ;  
                default:out=8'bx;  
            endcase  
        endmodule
```

Priority Encoder I

8

```
always @ (d0 or d1 or d2 or d3)
  if(d3 == 1)
    {x,y,v} = 3'b111 ;
  else
    if(d2 == 1)
      {x,y,v} = 3'b101 ;
    else
      if(d1 == 1)
        {x,y,v} = 3'b011 ;
      else
        if(d0 == 1)
          {x,y,v} = 3'b001 ;
        else
          {x,y,v} = 3'bxx0 ;
```

inputs				outputs		
D ₀	D ₁	D ₂	D ₃	x	y	v
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Priority Encoder II (1 / 2)

9

```
module priority (Code, valid_data, Data);
    output      [2: 0] Code;
    output      valid_data;
    input       [7: 0] Data;
    reg         [2: 0] Code;

    assign      valid_data = |Data; // "reduction or" operator
    always @ (Data)
    begin
        if (Data[7]) Code = 7; else
        if (Data[6]) Code = 6; else
        if (Data[5]) Code = 5; else
        if (Data[4]) Code = 4; else
        if (Data[3]) Code = 3; else
        if (Data[2]) Code = 2; else
        if (Data[1]) Code = 1; else
        if (Data[0]) Code = 0; else
            Code = 3'bx;
    end
end
```

Priority Encoder II (2/2)

10

```
/*// Alternative description is given below
always @ (Data)
    casex (Data)
        8'b1xxxxxxx : Code = 7;
        8'b01xxxxxx : Code = 6;
        8'b001xxxxx : Code = 5;
        8'b0001xxxx : Code = 4;
        8'b00001xxx : Code = 3;
        8'b000001xx : Code = 2;
        8'b00000001x : Code = 1;
        8'b000000001 : Code = 0;
        default : Code = 3'bx;
    endcase
*/
endmodule
```

4-bit Adder

11

```
module fouradd(A,B,Ci,S,Co);  
    input    [3:0]  A,  B;  
    input    Ci;  
    output   [3:0]  S;  
    output   Co;  
    reg      [3:0]  S;  
    reg      Co;  
    integer   i;  
  
    always begin  
        i=A+B+Ci;  
        S = i;  
        Co = i[4];  
    end  
endmodule
```

Or

```
assign {Co, S} = A + B + Ci;
```

Parity Checker

12

```
module parity_chk(data,parity);
input[0:7] data ;
output parity ;
reg parity ;
always @(data)
    begin:check_parity
        reg partial;
        integer n;
        partial=data[0];
        for(n=1;n<8;n=n+1)
            begin
                partial=partial^data[n];
            end
        parity<=partial;
    end
endmodule
```

Parity checker : a simple error detection method by adding an extra parity bit to a word of n bits.

Even parity: If there are odd number of 1s, then the parity =1. If there are already even number of 1s, then the parity =0.

Counter


13

```
module bcd_count(count,ripple_out,clr,clk); //0-9 Counter
output [3:0] count;
output ripple_out;
reg [3:0] count;
input clr,clk;
wire ripple_out=(count==4'b1001)?0:1; //combinational
always @(posedge clk or posedge clr) //combi.+sequential
    if(clr);
        count=0;
    else if(count==4'b1001)
        count=0;
    else
        count=count+1;
endmodule
```

Shifter

14
 
```
module shifter(so,si,d,clk,ld_,clr_);
output so;
input [7:0] d;
input si,clk,ld_,clr_; //asynchronous clear & synchronous load
reg [7:0] q;
assign so = q[7];
always @ (posedge clk or negedge clr_)
    if(~clr_)
        q=0;
    else if (~ld_)
        q=d;
    else
        q[7:0]={q[6:0],si};
endmodule
```





Memory Types

- Random-Access Memory (RAM)
 - ▣ Can read and write
 - ▣ Static RAM (SRAM)
 - Stores data so long as power is supplied
 - Asynchronous SRAM: not clocked
 - Synchronous SRAM (SSRAM): clocked
 - ▣ Dynamic RAM (DRAM)
 - Needs to be periodically refreshed
- Read-Only Memory (ROM)
 - ▣ Combinational
 - ▣ Programmable and Flash rewritable
- Volatile and non-volatile

Asynchronous SRAM

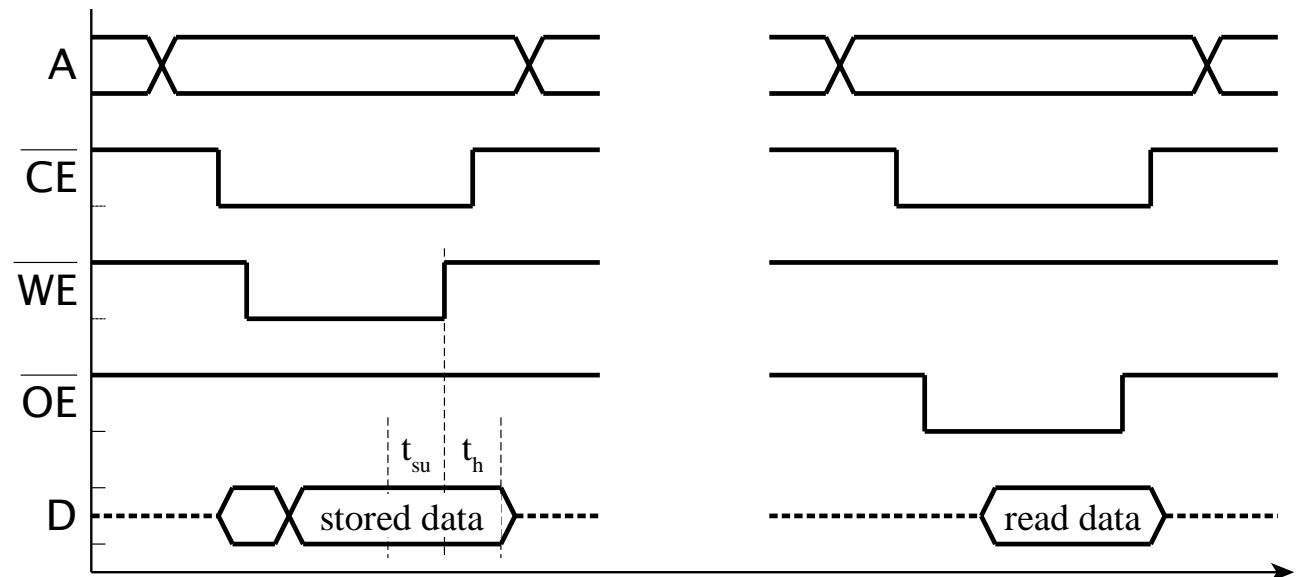 - Data stored in 1-bit latch cells
 - ▣ Address decoded to enable a given cell
- Usually use active-low control inputs
- Not available as components in ASICs or FPGAs



Asynch SRAM Timing


- Timing parameters published in data sheets
- Access time
 - ▣ From address/enable valid to data-out valid
- Cycle time
 - ▣ From start to end of access
- Data setup and hold
 - ▣ Before/after end of WE pulse
 - ▣ Makes asynch SRAMs hard to use in clocked synchronous designs

Synchronous SRAM (SSRAM)

- Clocked storage registers for inputs
 - ▣ address, data and control inputs
 - ▣ stored on a clock edge
 - ▣ held for read/write cycle

■ Flow-through SSRAM

- no register on data output

 

FIFO Memories


□ First-In/First-Out buffer

- ▣ Connecting producer and consumer
- ▣ Decouples rates of production/consumption




■ Implementation using dual-port RAM

 - Circular buffer
- Full: $\text{write-addr} = \text{read-addr}$
- Empty: $\text{write-addr} = \text{read-addr}$



Example: FIFO Datapath

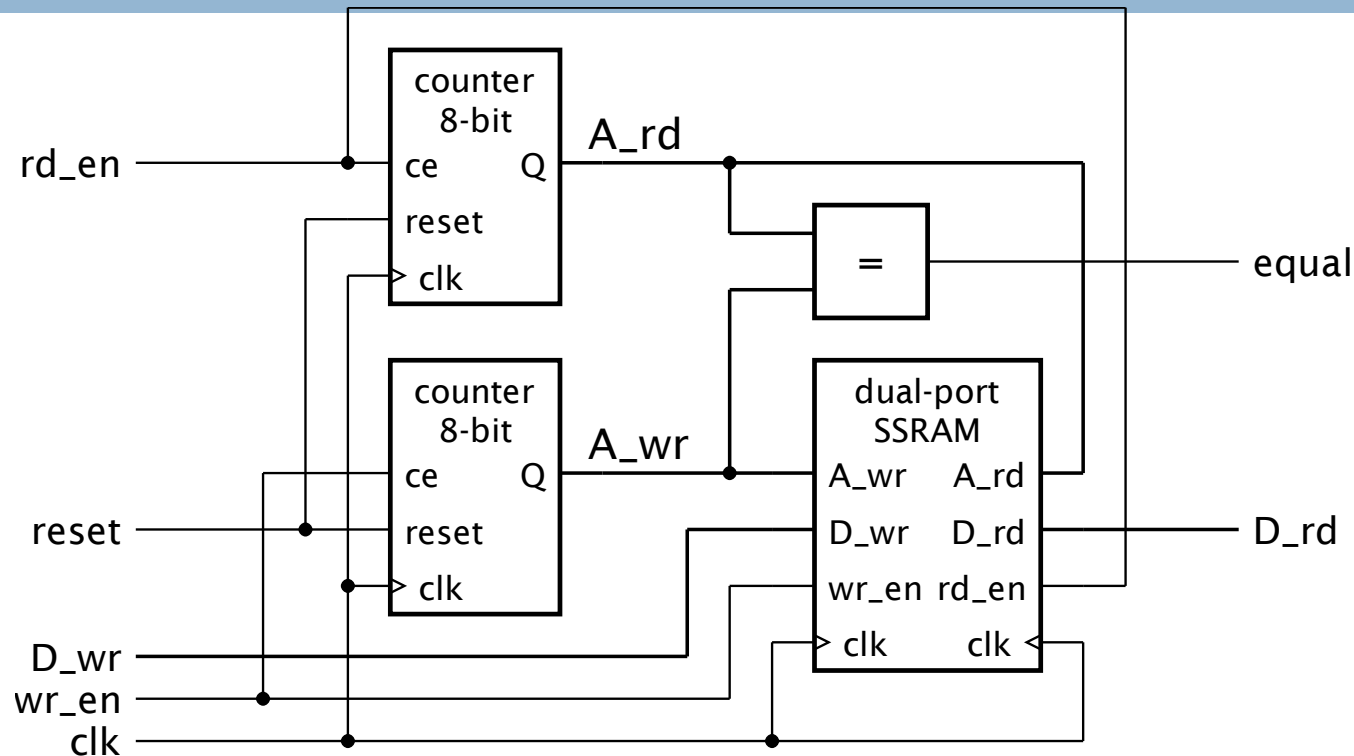


□ Equal = full or empty

▣ Need to distinguish between these states — How?

 Example: FIFO Control

□ Control FSM

- ▣ → filling when write without concurrent read
- ▣ → emptying when without concurrent write
- ▣ Unchanged when concurrent write and read



full = filling and equal
empty = emptying and equal

Multiple Clock Domains

- Need to resynchronize data that traverses clock domains
 - ▣ Use resynchronizing registers
- May overrun if sender's clock is faster than receiver's clock
- FIFO smooths out differences in data flow rates
 - ▣ Latch cells inside FIFO RAM written with sender's clock, read with receiver's clock

Assignment to be Completed by Yourself

23

- Design a FIFO that would use two cycles or less for each of its operations
 - ▣ Reset: set write pointer and read pointer to zero
 - ▣ Insert (wr_en): write to memory; then increment the write pointer
 - ▣ Remove (rd_en): read from memory; then increment the read pointer
- wordsize = 16 bit; capacity = 16

24

Task and Function

Overview

Difference and Similarity

Examples

Overview

25

- Verilog provides *tasks* and *functions* to break up large behavioral designs into smaller pieces.
- Just like procedures or subroutines in most programming languages
- Tasks
 - ▣ consists of input, output and inout arguments
- functions
 - ▣ have input arguments

Differences and Similarity

26

Functions	Tasks
Can enable another function but not another task	Can enable other tasks and functions
Always execute in 0 simulation time	May execute in non-zero simulation time
Contain no delay, event or timing control statements	May contain delay,
At least one input argument	Have zero or more arguments
Return a single value only	No return, but pass through output and input

Differences and Similarity

27

Functions	Tasks
In an expression, e.g., <code>i=func(a, b, c)</code>	A statement e.g., <code>task(out, in);</code>
Combinational	Break long procedural blocks
Synthesizable	Not synthesizable
Define within a module and local to the module	Define within a module and local to the module
NO wires, always or initial inside	NO wires, always or initial inside

Example I

28

```
task tsk;
    input i1, i2;
    output o1, o2;
    $display("Task tsk, i1=%0b,
            i2=%0b",i1,i2);
    #1 o1 = i1 & i2;
    #1 o2 = i1 | i2;
endtask
```

```
function [7:0] func;
    input i1;
    integer i;
    reg [7:0] rg;
    begin
        rg = 1;
        for (i=1; i<=i1; i=i+1)
            rg = rg+1;
        func = rg;
    end
endfunction
```

Example II

29

```
task Idle;  
    input [7:0] i;  
    begin  
        repeat (i)  
            @(posedge clk);  
        end  
    endtask
```

Example III

30

```
task Release_bus;
begin
    write =1;
    trans = 2'b00;
    addr = 0;
    burst = 0;
    size = 0;
    w_index = 0;
    w_data = 32'h0;
    write_en =0;
    read_en =0;
end
endtask
```

Example IV

31

```
module parity;
....
reg [31:0] addr;
reg parity;
always @(addr) begin
    parity = calc_parity(addr);
    $display("Parity calculated = %b", calc_parity(addr))
end
...
function calc_parity;
input [31:0] address;
begin
    calc_parity = ^address; // reduction xor
end
endfunction
endmodule
```