

N26F300
VLSI SYSTEM DESIGN
(GRADUATE LEVEL)

Fall 2010

FSM and Controller

Outline

2



- **Moore & Mealy Revisited**
- **Examples of FSM**
- **Control external hardwares**
 - ▣ **Controller for timer, ADC and memory access**
 - ▣ **WatchDog Timer**
 - ▣ **DMAC**

[Material adapted from “FSM based Digital Design Using Verilog HDL” by Minns and Elliott]

Finite State Machine (FSM)

3

  - A digital sequential block controlled by one or more inputs with predefined finite states. The machine can move from one state to another state.




Synchronous FSM

4

- An FSM that can only change states only if a clock pulse occurs.
- States can be identified by using a number of flip-flops inside the FSM block.


$$\# \text{ of states} = 2^{\text{Number of FFs}}$$


$$\# \text{ of FFs} = \log_2(\# \text{ of states})$$


Moore and Mealy Machines

5

- **Moore model**

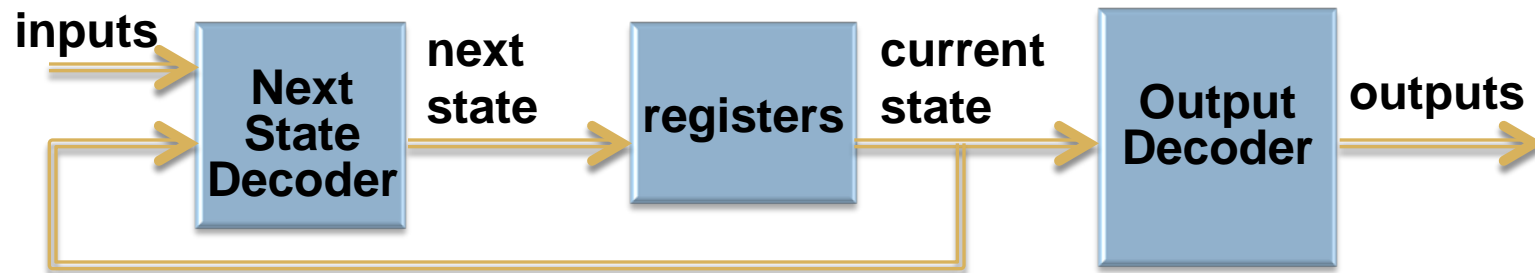

- **Mealy model**

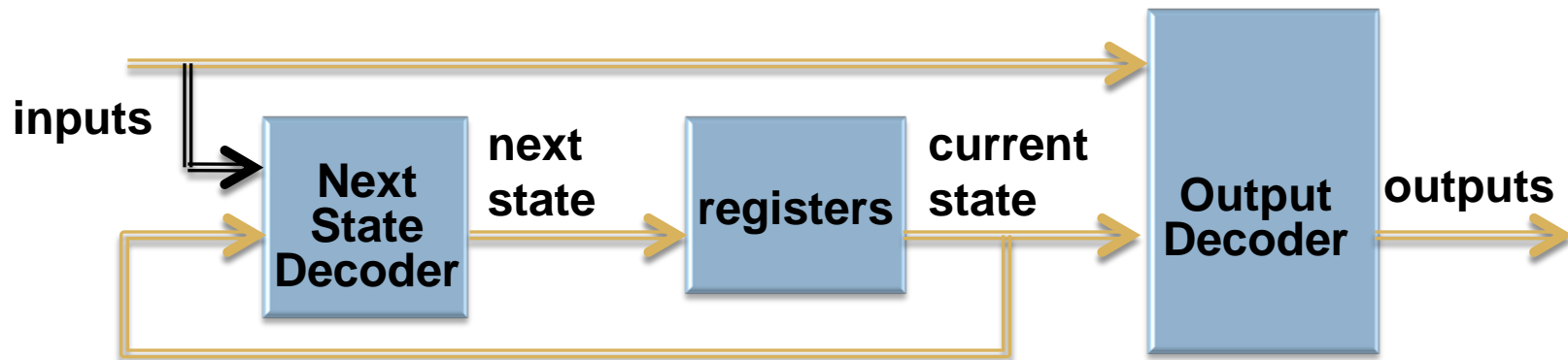


Mealy vs. Moore models

6

- Moore is safer to use
 - ▣ Outputs change at clock edge
 - ▣ Not like Mealy, output follow input in asynchronous way
- - ▣ Output = function of inputs and the present state
 - ▣ Not like Moore, output depends only on the present state
- - ▣ Complete in the same cycle
 - ▣ Not like Moore, more logic may be needed to decode state into outputs



Synchronous Mealy Model

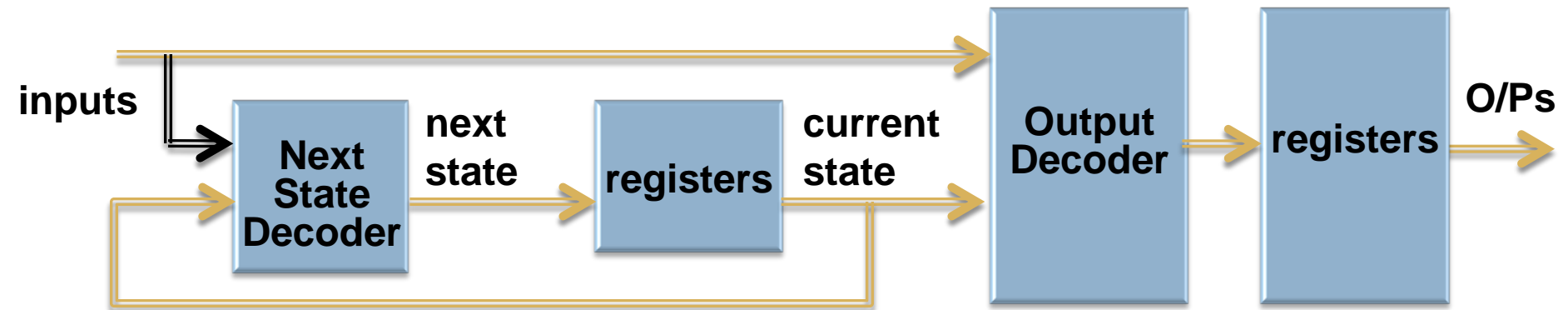

- Synchronous Mealy machines avoid the potential glitches and change of outputs asynchronously

Moore Machines


8

 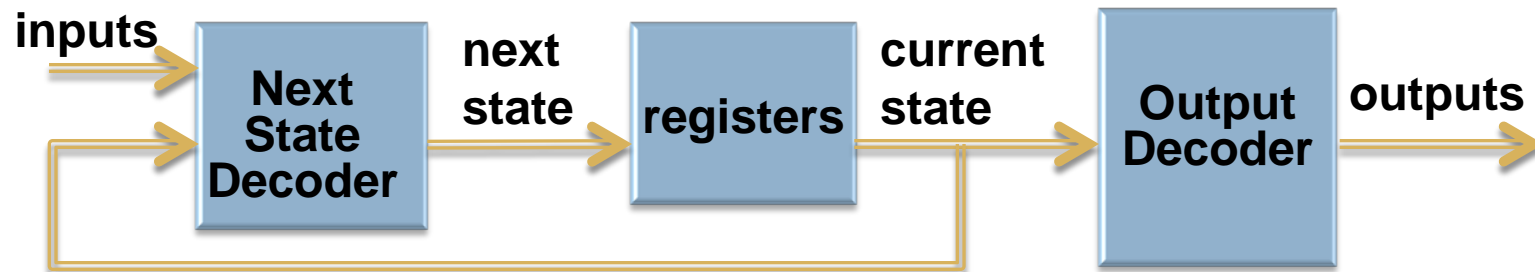

One of basic forms of many asynchronous counters

State Transition Graph (STG)

9

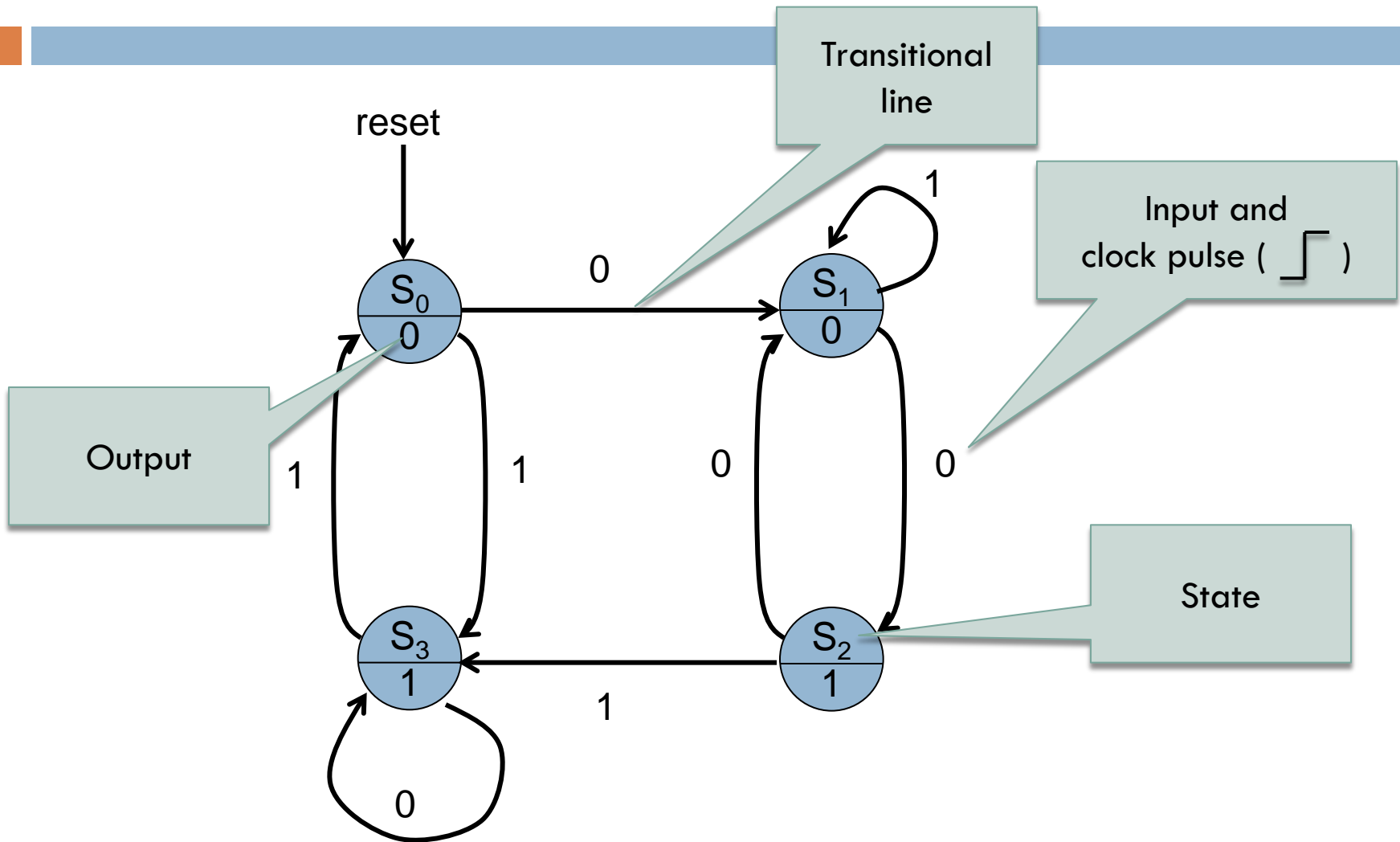


EXM1: A Single-Pulse Generator Circuit with Memory (SPGM)

10


□ Problem:

 - When input $s = 1$,
 - produce a single output pulse at the output P
 - Set output L to 1
- When output $s = 0$,
 - Clear output L to zero
- L: memory indicator



STG for SPGM (SPGM-1)

11

 


$$P = A \cdot /B$$

$$L = A \cdot /B + /A \cdot B$$

STG for SPGM complying with Unit Distance Pattern (SPGM-2)

12

 


EXM2: A Single-Pulse Generator Circuit with Memory (SPGM-3)

13


□ Problem:

 - When input $s = 1$,
 - produce a single output pulse at the output P
 - Set output L to 1
- When output $s = 0$,
 - Clear output L to zero
- When input $r = 1$,
 - Let $P = \text{clk}$
- When input $r = 0$,
 - Resume its single pulse



STG for SPGM complying with Unit Distance Pattern (SPGM-3MR)

14

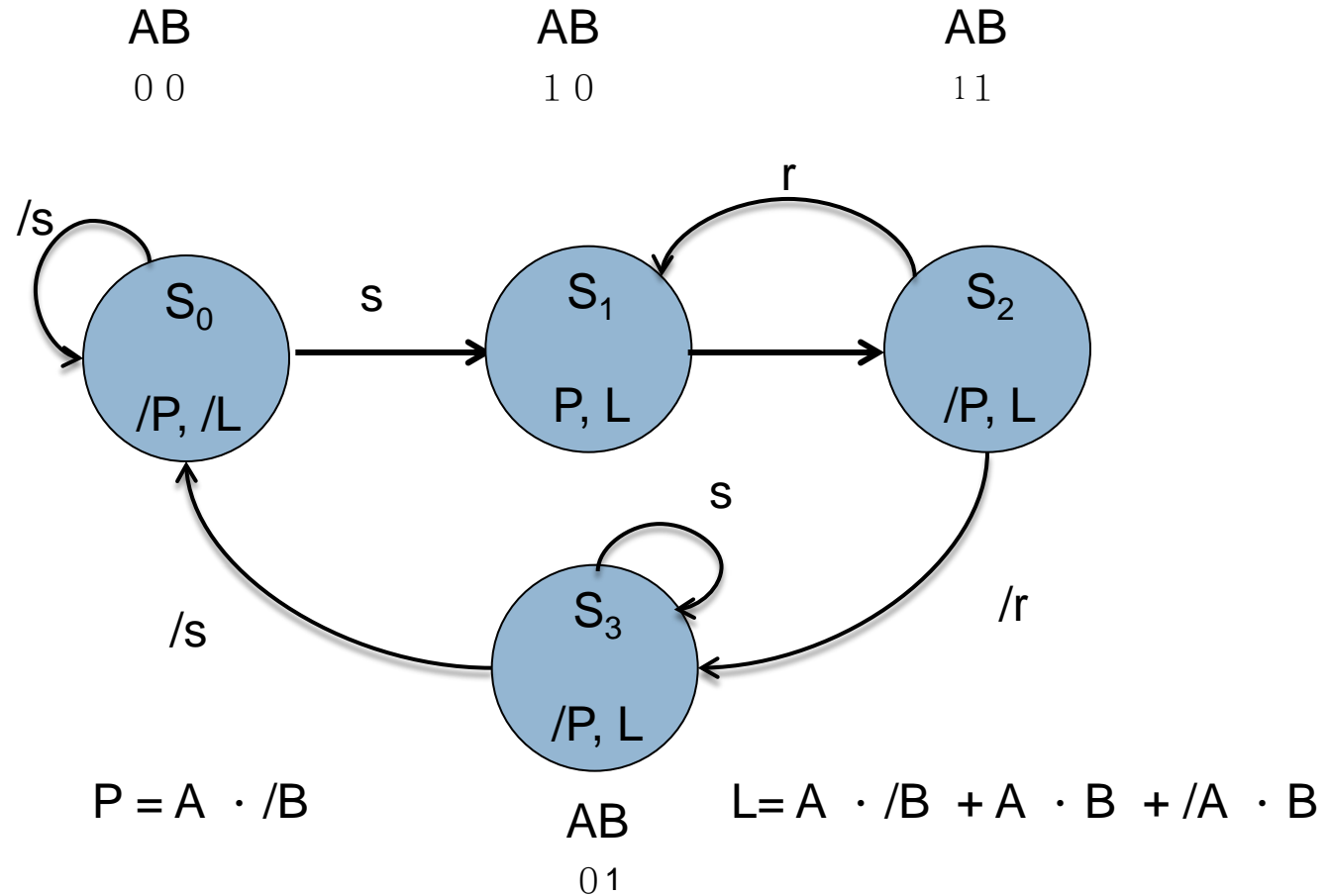


Moore to Mealy

15

- Make the output P depend on the state 1 as well as clk
- That is to say a direct control path from the input to the output


SPGM Using Mealy Model (SPGM-3ML)

16

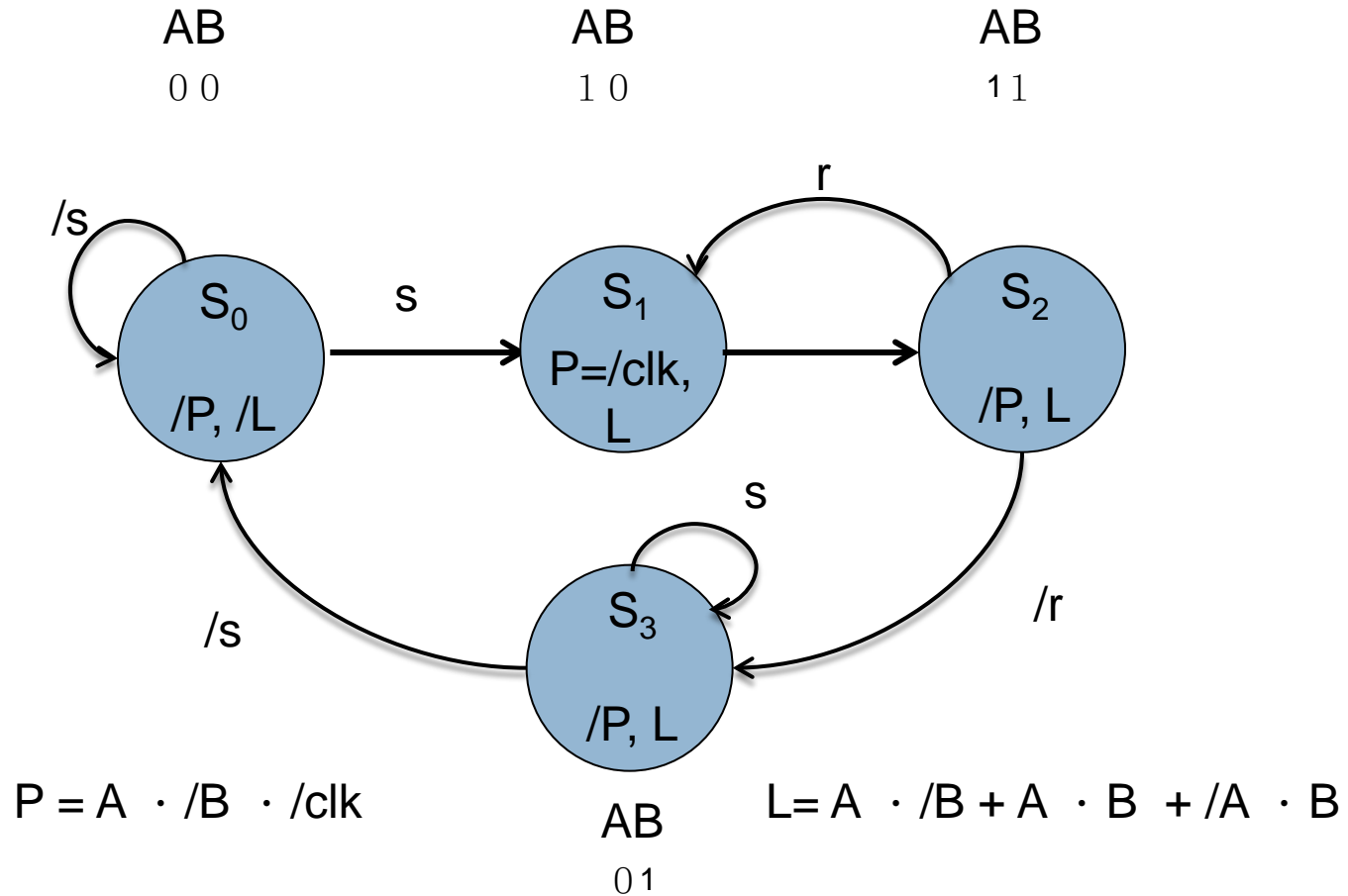

Waveform of Moore and Mealy

17

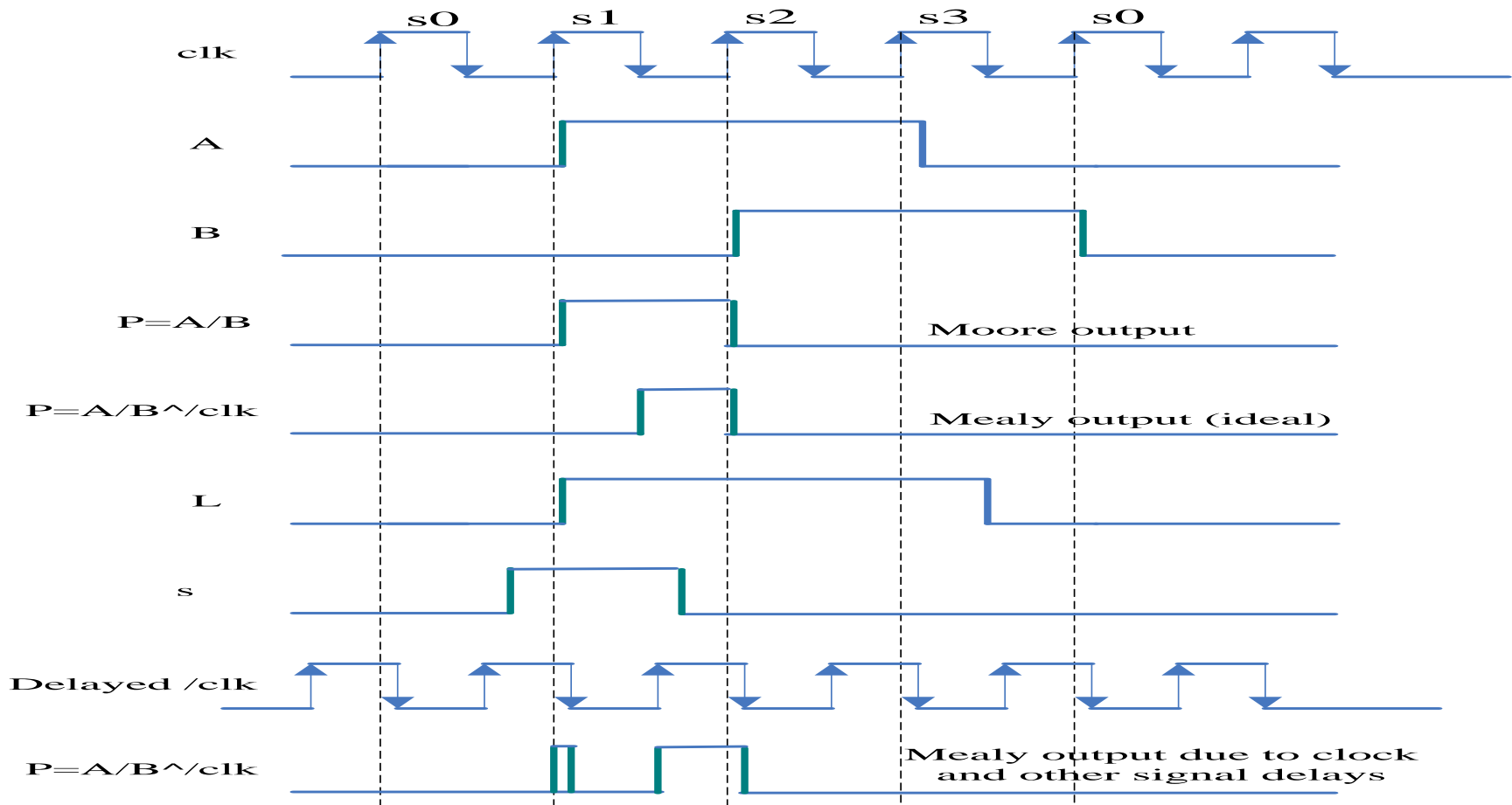

EXM3: 101 Pattern Generator


18

□ Problem

- ▣ Produce a state diagram for an FSM that will generate 101 pattern when input s goes high. The input s must be returned low before another 101 pattern can be produced.


Development of 101 PG

19

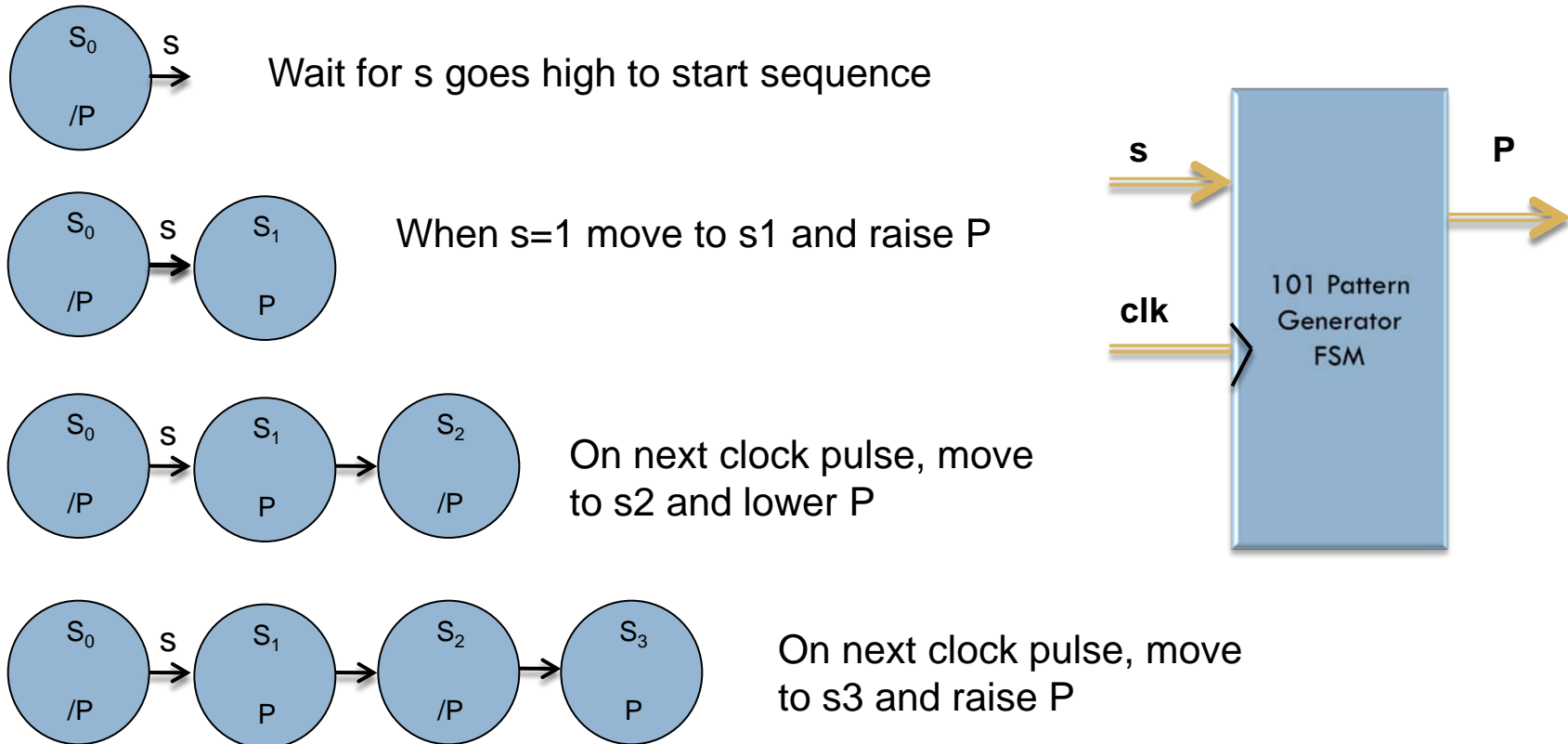

Complete State Diagram



20

 

Implementation of Wait


21

  - How to let a FSM to wait in a state for predefined period?
 - ▣ Allocate a number of consecutive states
 - ▣ Use an external timer unit that can be controlled by the FSM




Timer Unit and FSM

22

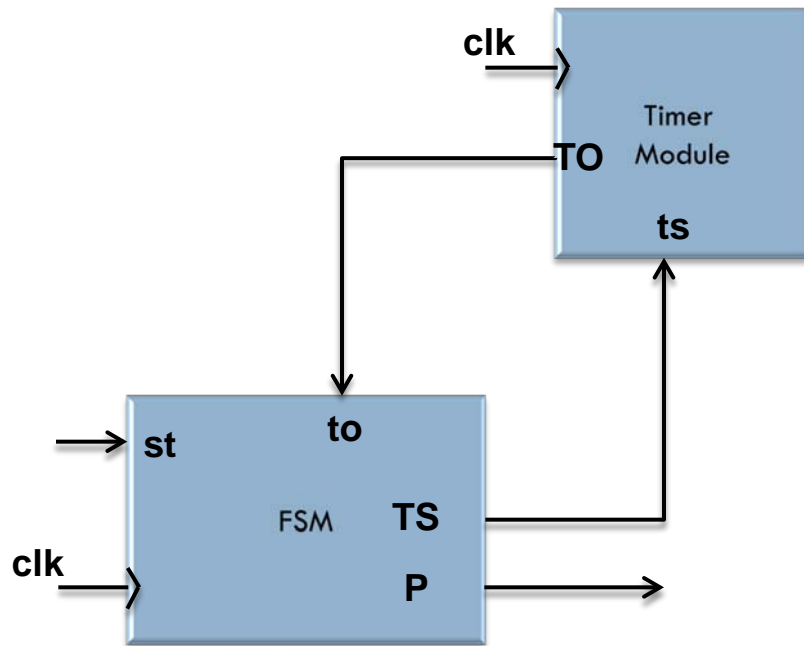

 - State sequence to control the timing module






Prior to
starting
timer

Start the
timer

Time-out state
wait here until
timer times out

   Controlling an Analog-to-Digital Conversion (ADC)





Generic Memory Device

I/O


R

Memory Timing

  


Timing Waveform of a Memory Device


I/O

 

Memory Timing

 


FSM for Mem Write

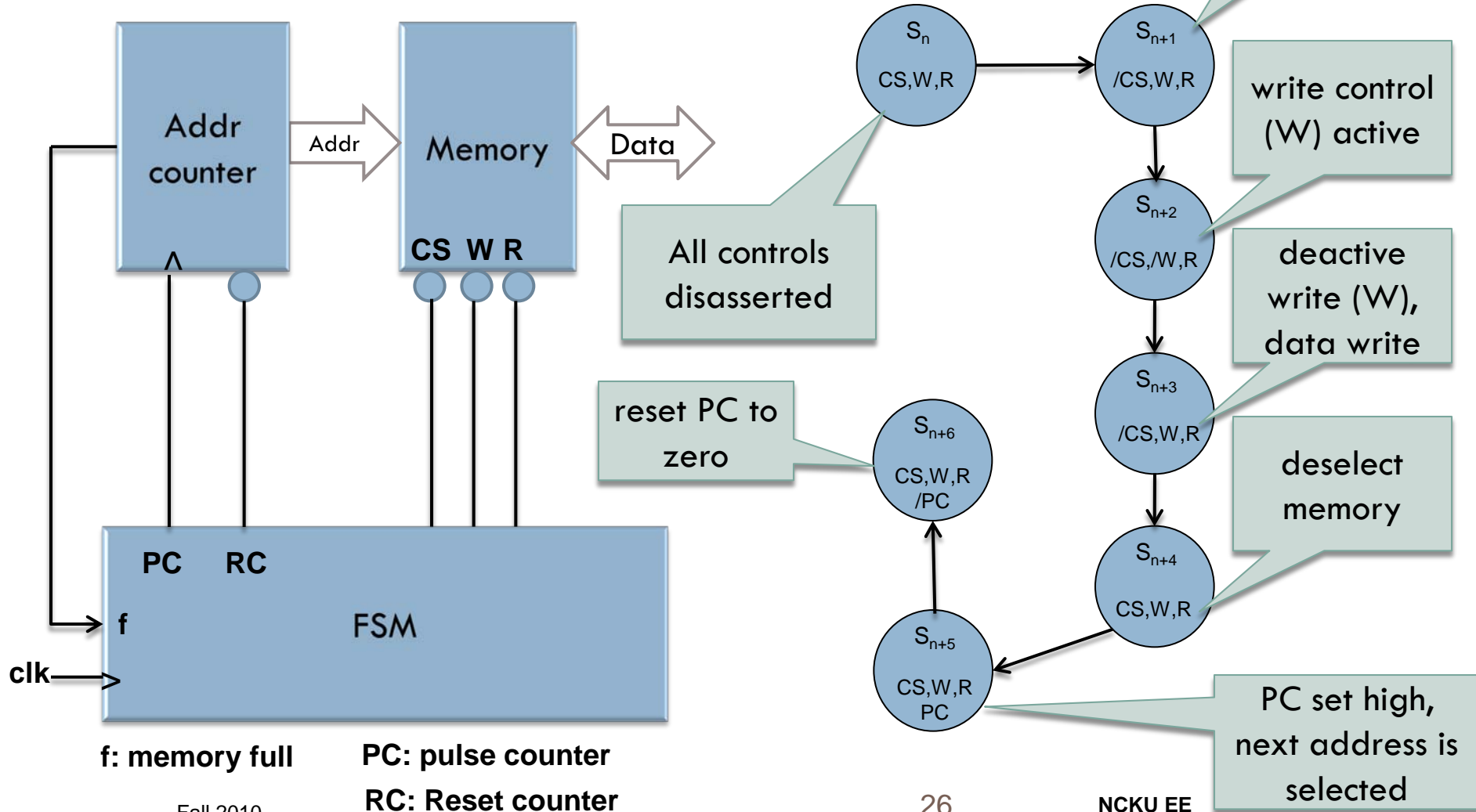

Small Data Acquisition System (DAS)

27

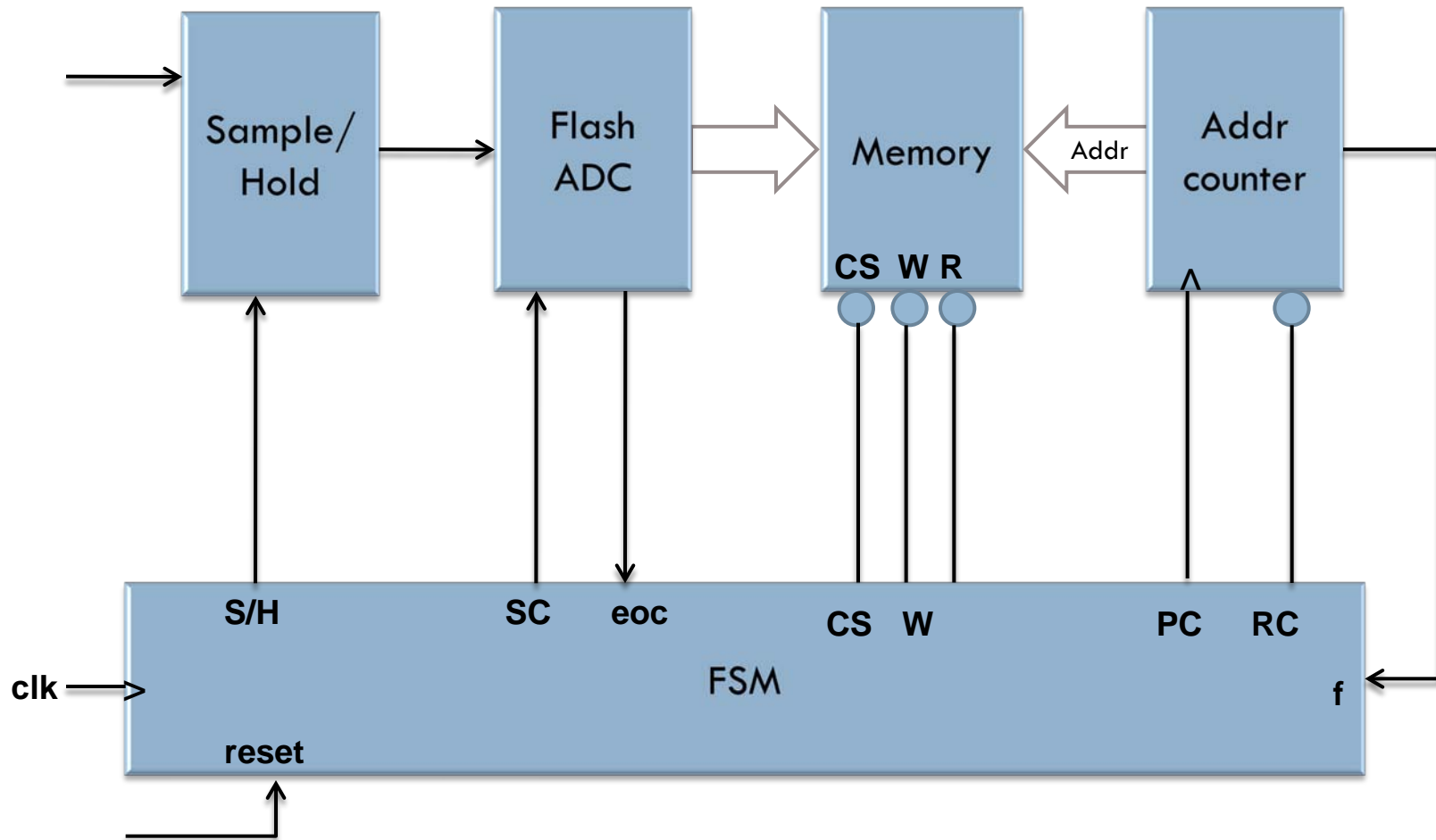

Exercise!


Clocked Watchdog Timer (WDT)

28

- Addressable device that can be written to on a regular basis
- Regularly reinitialize to a known count value
- If the μ controller does not write to the WDT between counting-down period and WDT reach zero, the μ controller will be reset.


Block Diagram for a WDT

29

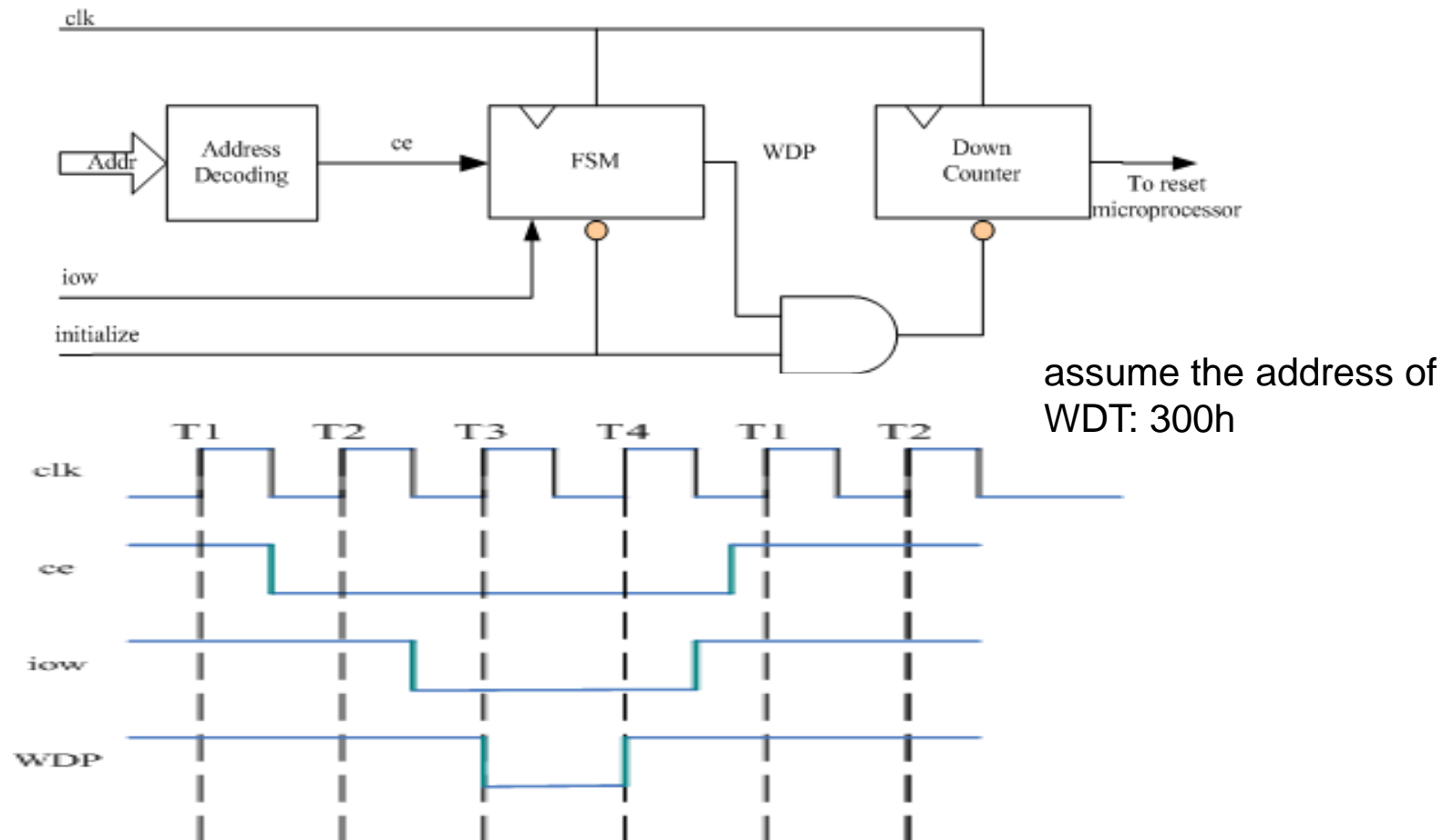

State Diagram for the WDT

30

 


One Hot Technique

31

- Assign a flip-flop for each state
- Disadvantage: wasteful if the number of states is large
- Advantage:
 - ▣ in theory avoid the generation of output glitches
 - ▣ require fewer logic levels
- Often use in FPGAs since its architecture consists of many cells that can be programmed to be FFs

DMA Controller (DMAC)


32

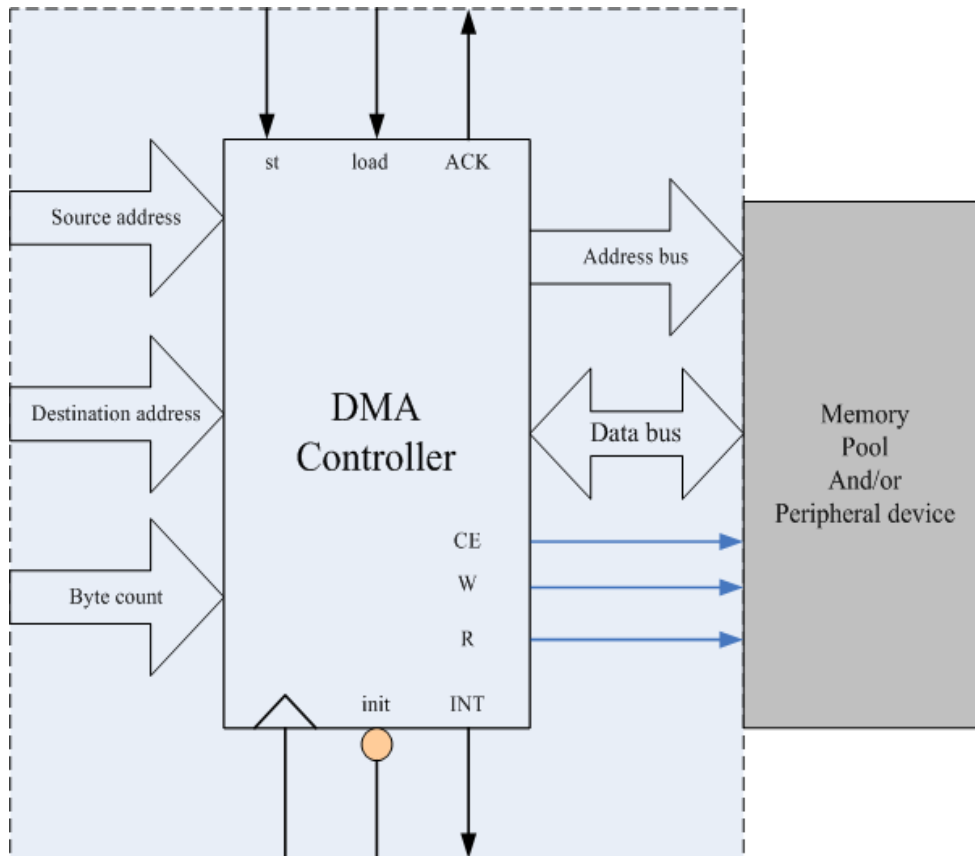

- The DMAC can share the loading of the microprocessor
- Allow data to be move from one part of the memory system to another or to a peripheral device

Possible Detailed Block Diagram

33

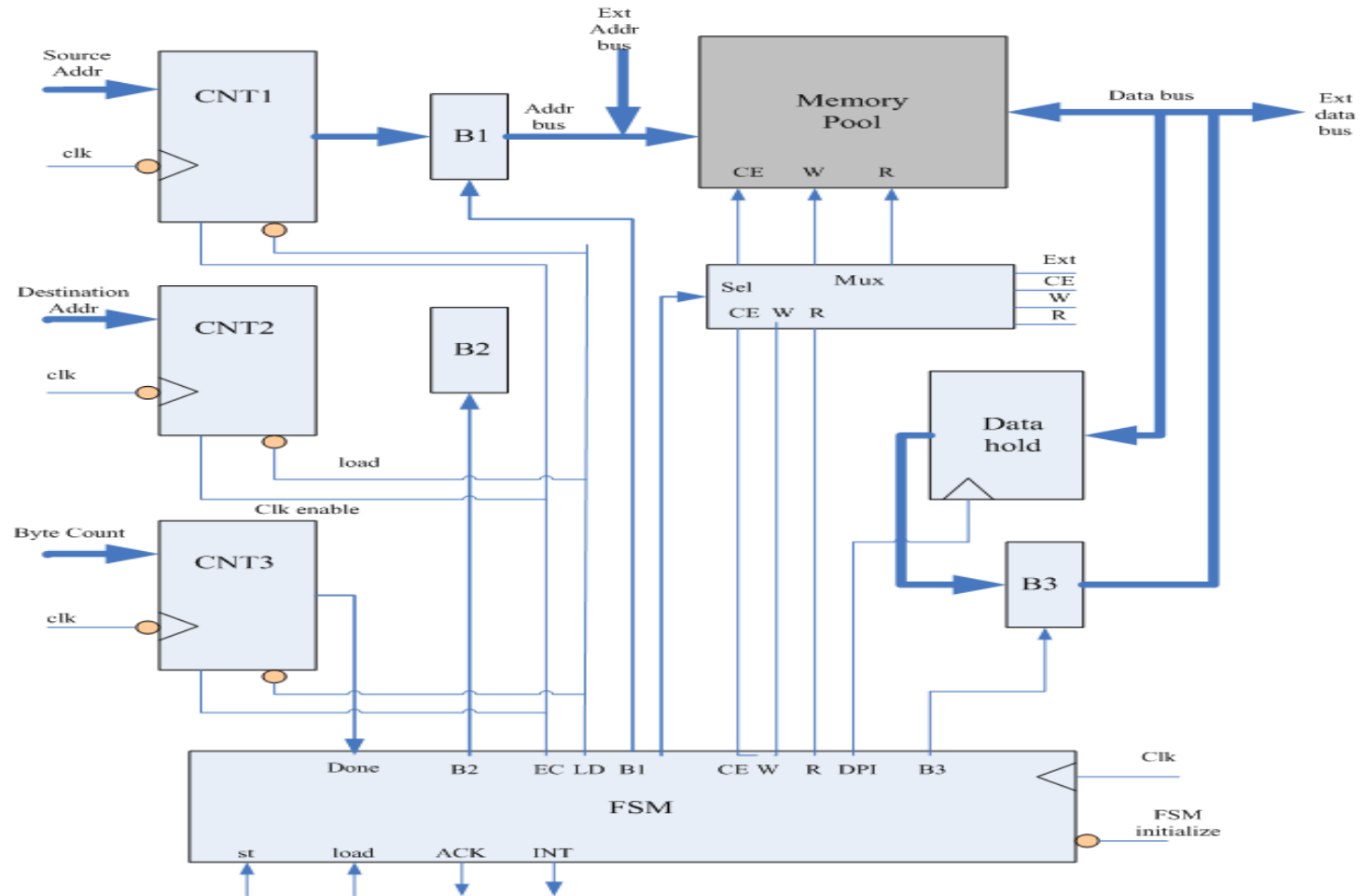

General Steps

34

- Start (st) DMA
- Accept source, destination, and words/byte to be transferred
- Interrupt the microprocessor to let it know it is to take over the memory/peripheral
- Microprocessor isolates itself from these devices and send the load signal to DMA

Transactions

35

1. Select the source address and read its contents into a buffer
2. Select the destination address and deposit the buffer content into this address
3. Decrement the byte counter and advance the source & destination counter
4. Repeat 1 to 3 until all data transactions are complete (i.e., byte counter \rightarrow 0)

Steps for FSM

36

1. Wait for the start signal st
2. Provide an interrupt to the μP to get it isolate itself from the memory
3. Wait for a load signal from the μP ; when obtained, loading the source, destination, and byte count into the relevant counters
4. Source memory needs to be selected and data read from the memory into data holding registers

Steps for FSM

37

5. Source address needs to be isolated from the memory and the destination memory selected
6. Data in the holding register needs to be transferred into the output buffer B3 and store into the memory destination address

Steps for FSM

38

7. Decrement byte counter and checked if all bytes of data have been transferred
8. If there are more bytes to transfer, repeat 1 to 7 again. This is to continue until all bytes are transferred


Control DMAC from μP

39

- Previous DMAC starts with a signal, st. Useful in avoiding address decoding logic
- A more appropriate way – via the memory (or I/O) map of the μP .
- In the following example, assume the spare address for DMAC is 380h


St from μP for the FSM

Block Diagram

 


I/O location 380h appears as a o/p port representing the input st.
This needs to be latched into a 1-bit buffer so it can be ready by the FSM.

Timing waveform

 

Whole Block Diagram

41

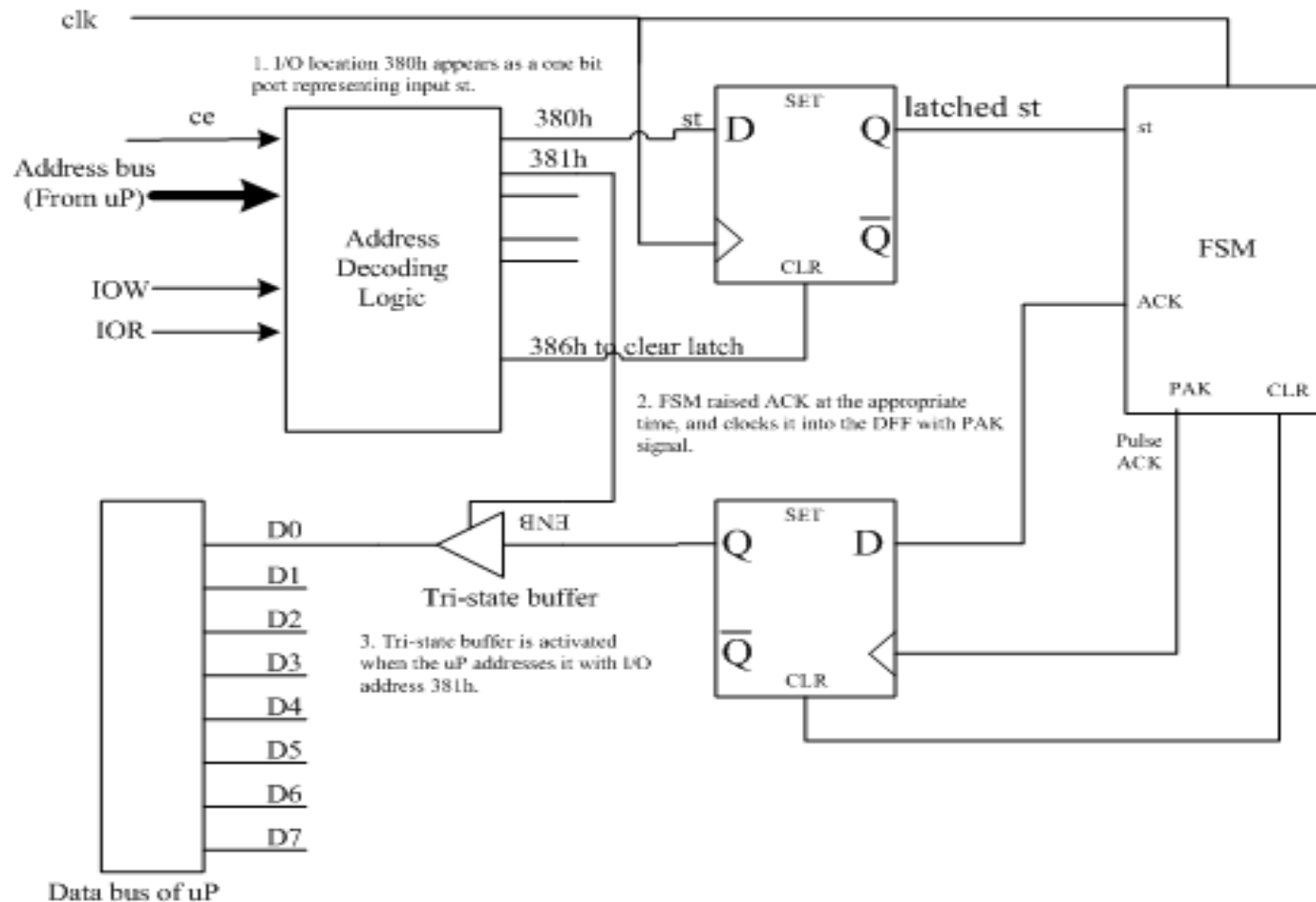

Algorithmic State Machine



Rationale for ASM Charts

43

- STG do not directly display the evolution of states resulting from an input
- Algorithmic State Machine (ASM): an abstraction of the functionality of a sequential machine
- ASM charts reveal the sequential steps of a **machine's activity**
- Focus on machine's activity, rather than contents of registers
- ASM charts can represent Mealy and Moor machines


ASM Chart

44

  

Excess-3 ASM Chart

45

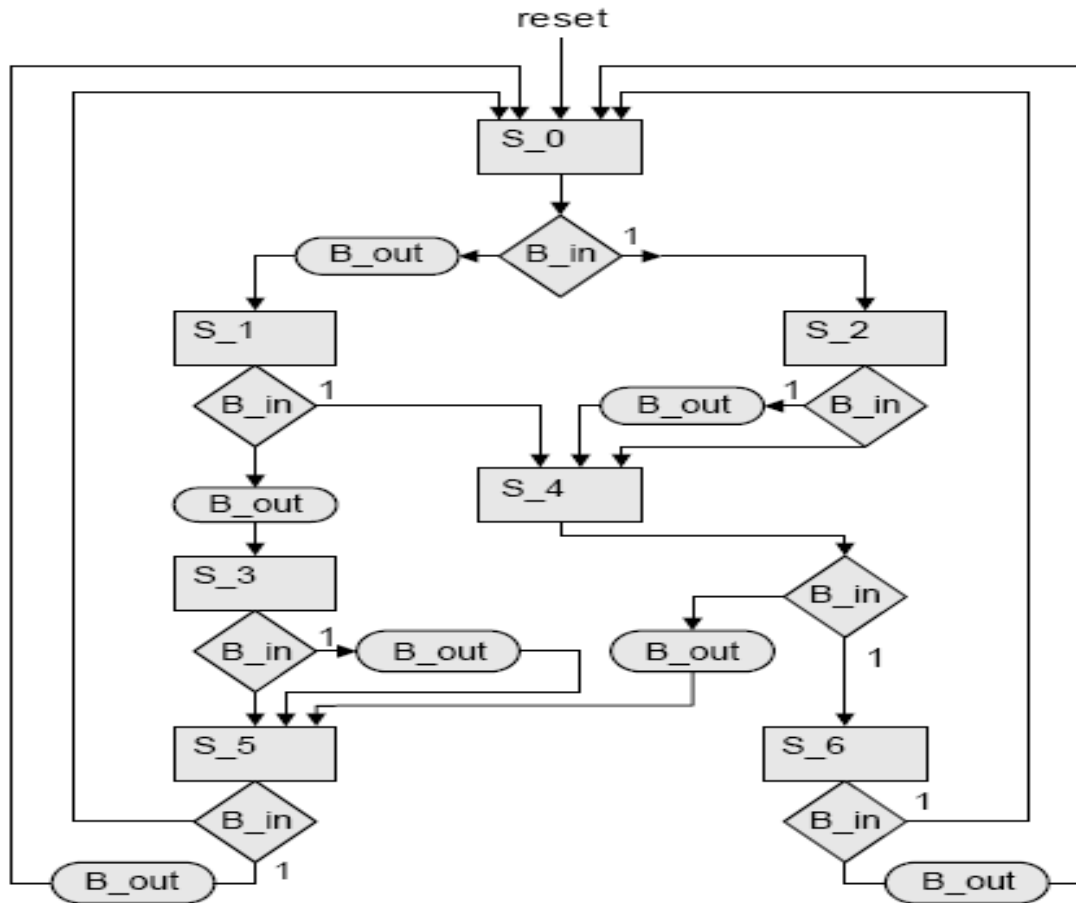

BCD_to_Excess_3b

46

```
module BCD_to_Excess_3b (B_out, B_in, clk, reset_b);
    output          B_out;
    input           B_in, clk, reset_b;
    parameter       S_0 = 3'b000,    // State assignment
                  S_1 = 3'b001,
                  S_2 = 3'b101,
                  S_3 = 3'b111,
                  S_4 = 3'b011,
                  S_5 = 3'b110,
                  S_6 = 3'b010,
                  dont_care_state = 3'bx,
                  dont_care_out = 1'bx;

    reg [2:0]       state, next_state;
    reg             B_out;

    always @ (posedge clk or negedge reset_b)
        if (reset_b == 0) state <= S_0; else state <= next_state;
```

always @ (state or B_in) begin

B_out = 0;

case (state)

S_0: if (B_in == 0) begin next_state = S_1; B_out = 1; end
else if (B_in == 1) begin next_state = S_2; end

S_1: if (B_in == 0) begin next_state = S_3; B_out = 1; end
else if (B_in == 1) begin next_state = S_4; end

S_2: begin next_state = S_4; B_out = B_in; end

S_3: begin next_state = S_5; B_out = B_in; end

S_4: if (B_in == 0) begin next_state = S_5; B_out = 1; end
else if (B_in == 1) begin next_state = S_6; end

S_5: begin next_state = S_0; B_out = B_in; end

S_6: begin next_state = S_0; B_out = 1; end
endcase
end


endmodule

Reading: M. Ciletti Chap 7

Controller for Datapath

FSM Controller for a Datapath

49

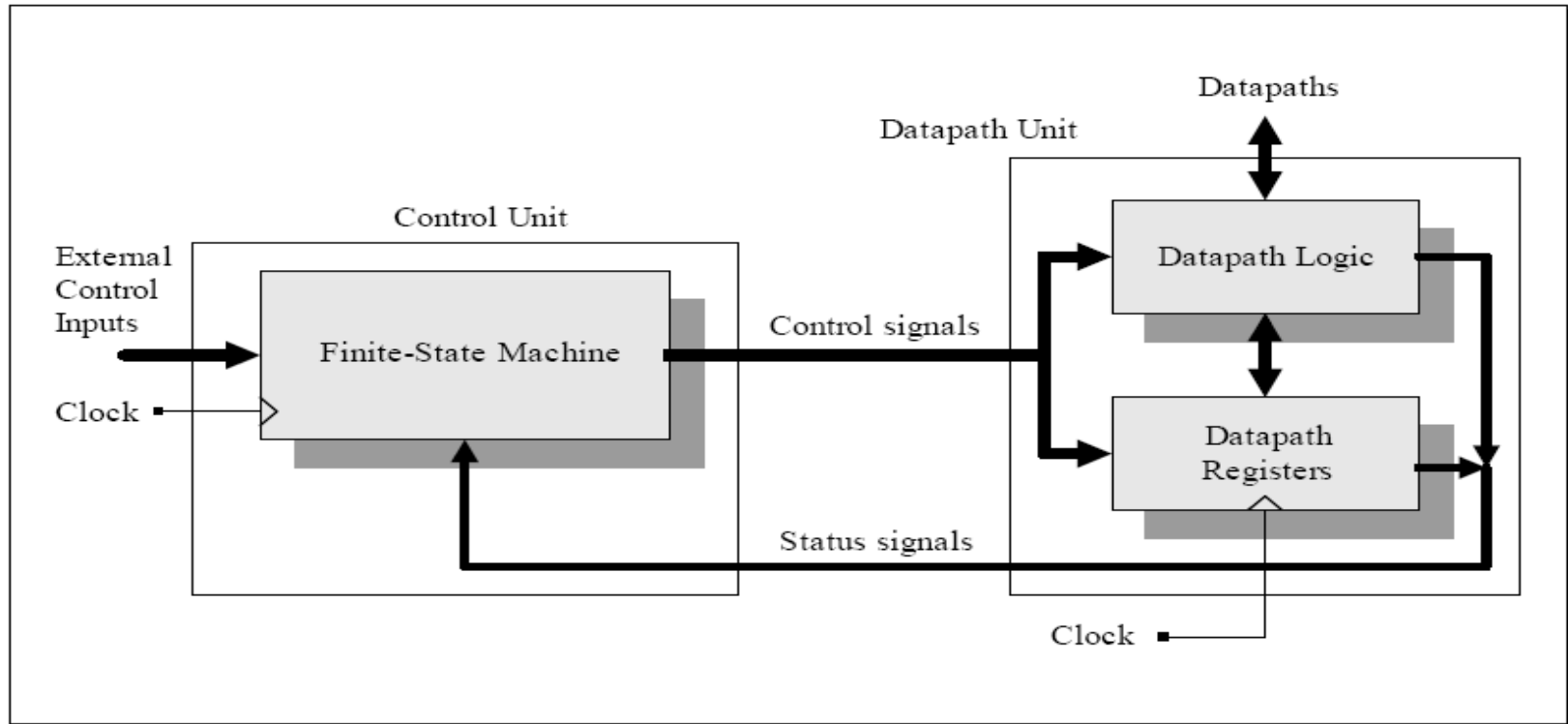

The controller dictates the timing of all activity in a system.


Datapath Control Signals

For stored-program computer, control signals need to

- ▣ Load, read, shift contents of registers
- ▣ Fetch instruction from memory
- ▣ Store data in memory
- ▣ Steer signals through muxes
- ▣ Control 3-state devices
- ▣ Select/execute ALU operations

Conceptual Steps of Designing Application-Driven HW Systems

51

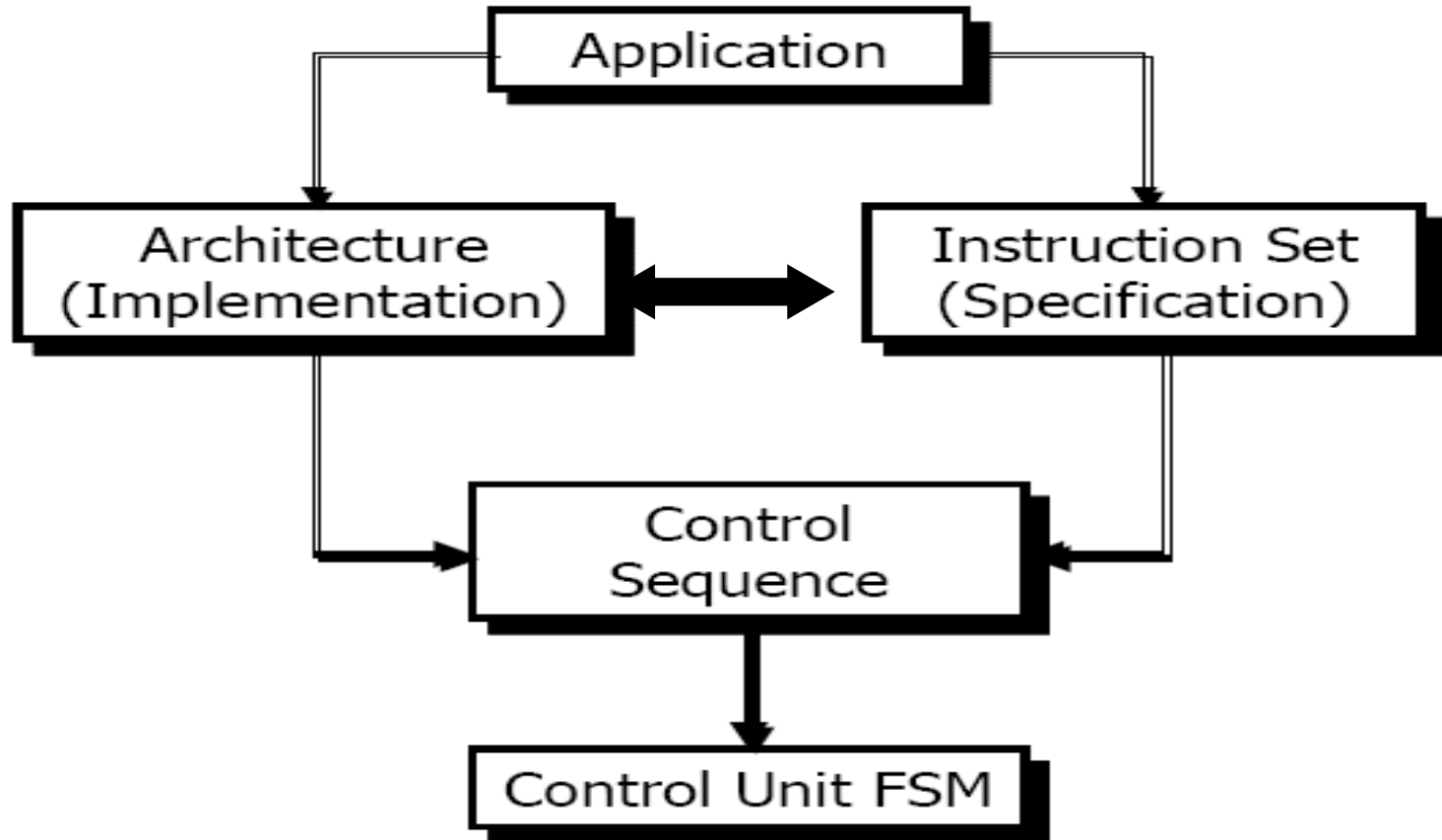

Design Example: Binary Counter

52

□ Problem statement:


- Design a 4-bit binary counter with features
 - Incremented by 1 at each active edge of the clock
 - Wrapped around to 0 when reaching 1111_2

□ Ideas to write the controller's code

- Use implicit state machine
- Use explicit state machine
- Separate control unit and datapath
 - RTL structure model
 - RTL behavioral model


Approach One: Explicit-state Machine

53

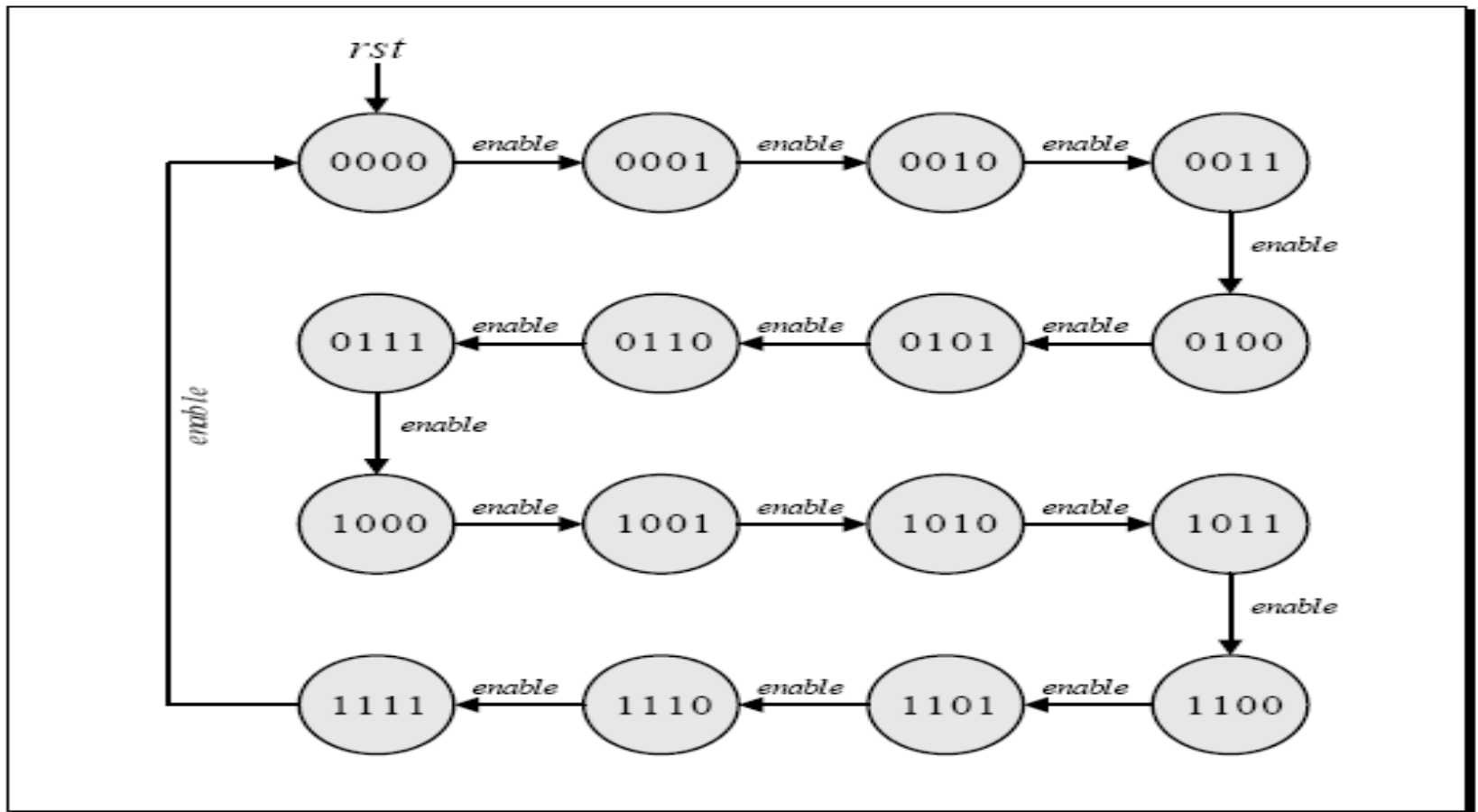

Approach Two: Datapath and Controller

54

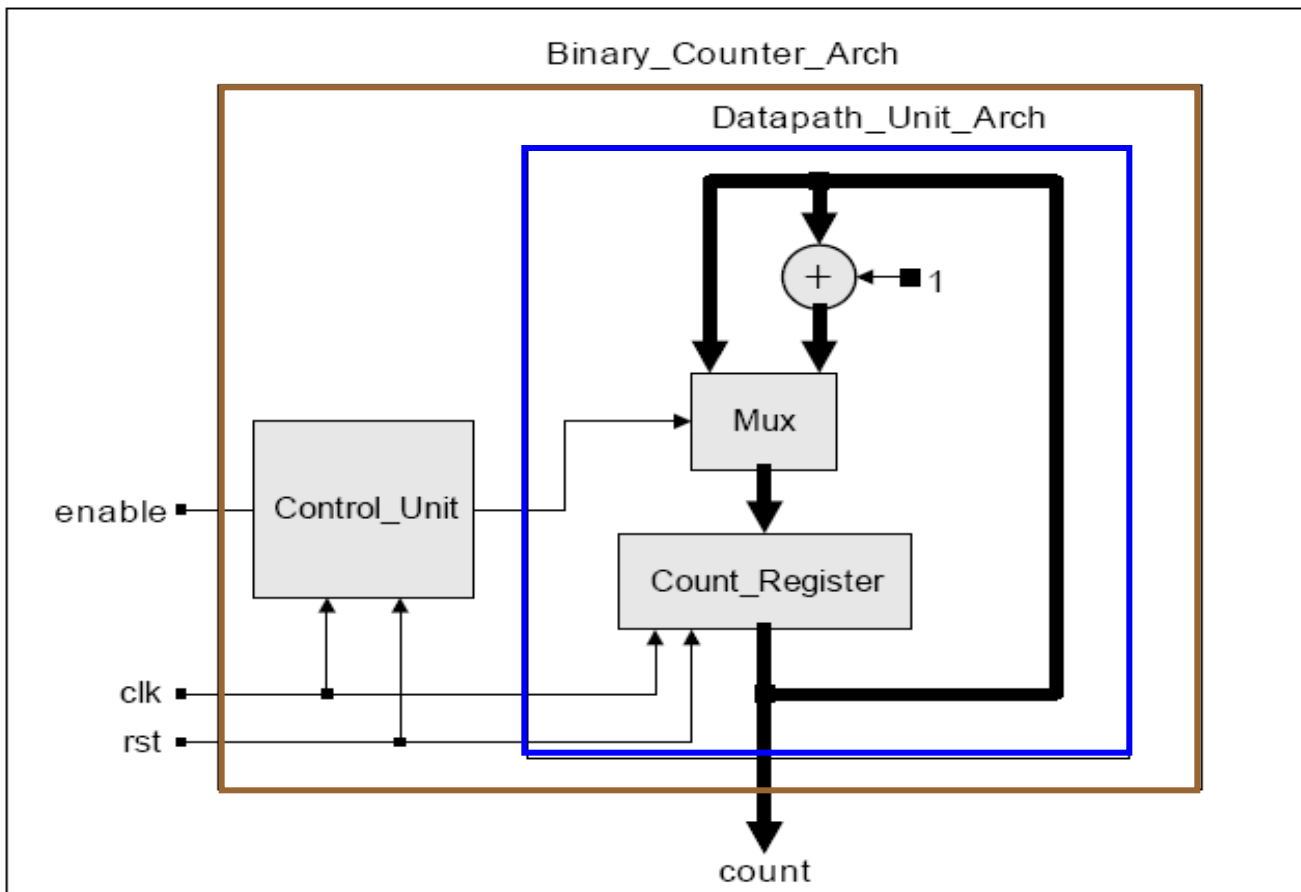

Approach Three: Implicit State Machine

55

```
module binary_counter_imp(cnt, enable, reset, clock);
input enable, reset, clock;
output cnt;


reg [3:0]cnt;

always @(posedge reset or posedge clock)
    if(reset==1)
        cnt <= 4'b0;
    else
        if (enable==1)
            cnt <= cnt+1;


endmodule
```

ASM Views of Two Machines

56

 

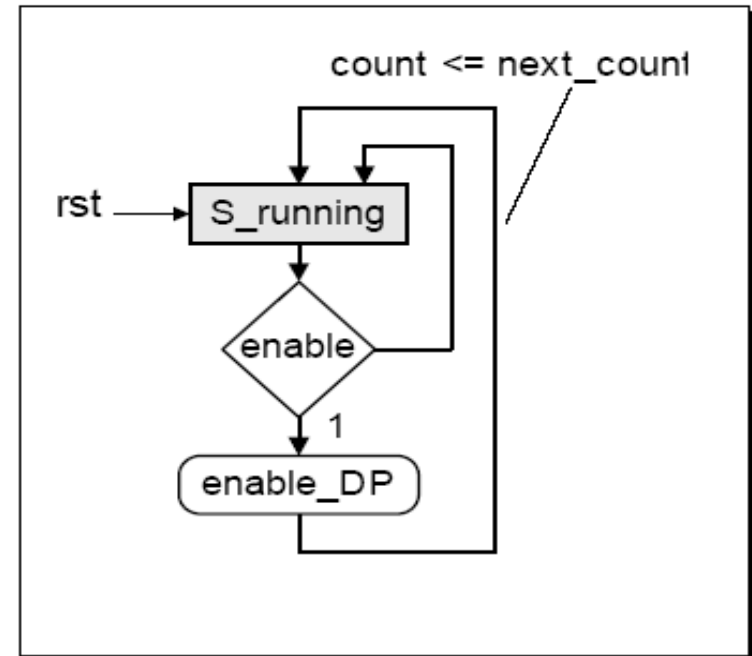Confusion: Mixed Datapath Operations and FSM



Clarity: Partitioned Datapath and Controller

ASM-Based Verilog Model (1/2)

57

```
module Binary_Counter_Part_RTL (count, enable, clk, rst);  
parameter      size = 4;  
output [size-1: 0] count;  
input  enable;  
input  clk, rst;  
wire   enable_DP;
```

```
Control_Unit M0 (enable_DP, enable, clk, rst);  
Datapath_Unit M1 (count, enable_DP, clk, rst);  
endmodule
```

```
module Control_Unit (enable_DP, enable, clk, rst);  
output enable_DP;  
input  enable;  
input  clk, rst;    // Not needed
```

```
    wire enable_DP = enable;
```

```
endmodule
```

ASM-Based Verilog Model (2/2)

58


```
module Datapath_Unit (count, enable, clk, rst);
parameter  size = 4;
output    [size-1: 0] count;
input     enable;
input     clk, rst;
reg       count;
wire      [size-1: 0] next_count;

always @ (posedge clk)
    if (rst == 1) count <= 0;
    else if (enable == 1) count <= next_count(count);

function [size-1: 0] next_count;
input [size-1:0] count;
begin
    next_count = count + 1;
end
endfunction
endmodule
```


State Diagram for Implementation using DFFs (for SPGM-2)

59

 

RTL for SPG with Asyn. Reset

60

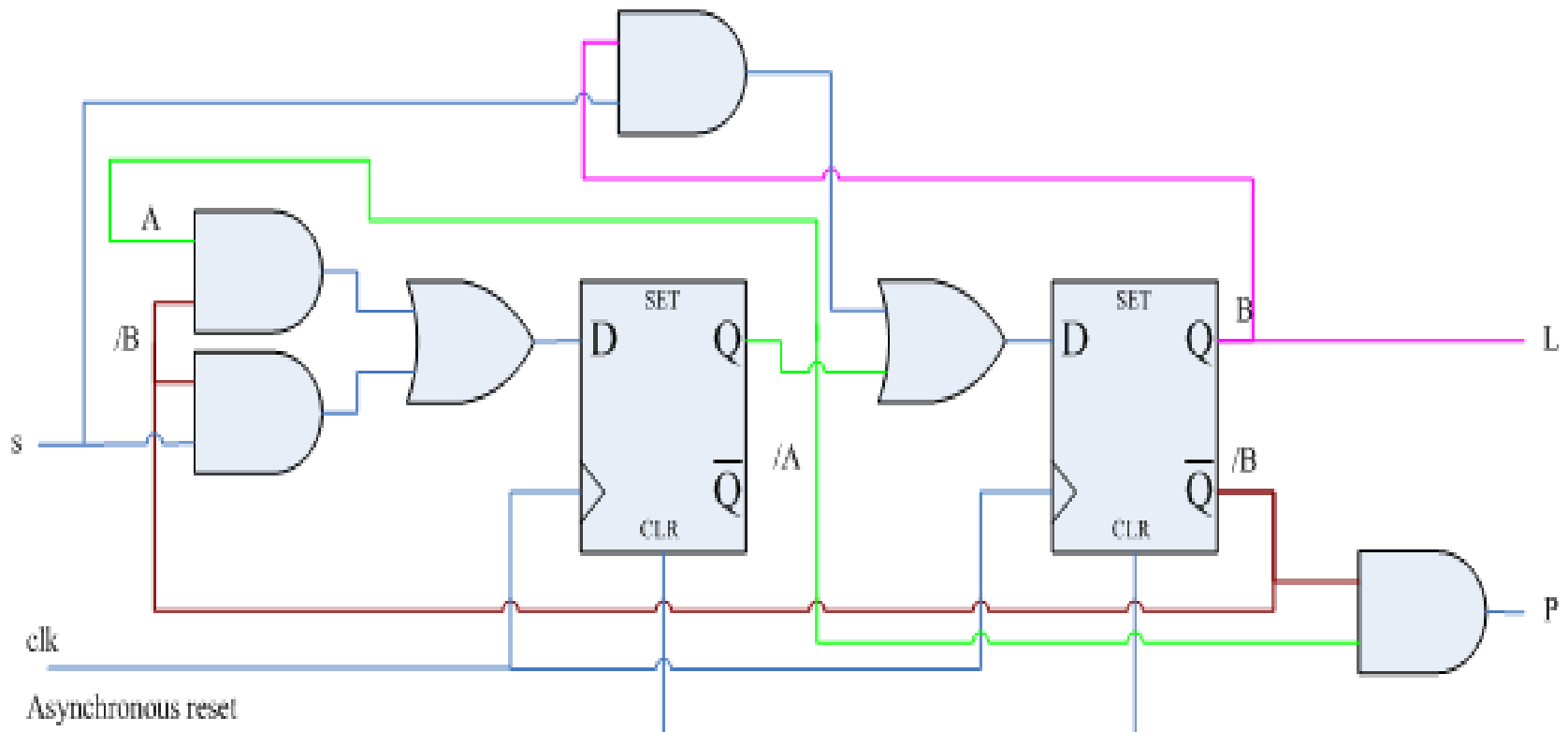

RTL for SPG with Syn. Reset

61

