

N26F300  
VLSI SYSTEM DESIGN  
(GRADUATE LEVEL)

Fall 2010

**Synthesis for Verilog (II)**

# Outline

2

- Synthesis of Sequential Logic
- Coding Guidelines

# 3 Synthesis of Sequential Logic

# Synthesis of Sequential Logic with Latches

4

## □ Accidentally

A synthesis tool unexpectedly inferred latch-based logic from a Verilog statements that are intended to be combinational logic.

## □ Intentionally

A synthesis tool did what the designers want from a Verilog statements.

# When Combinational Becomes Sequential?

5

- A feedback-free netlist of combinational primitives  
→ NO latch
- A set of feedback-free continuous assignments → NO latch
- A continuous assignment using a conditional operator with feedback → latch

# Intentional Synthesis of Latches

6


- Incompletely specified assignment
  - ▣ In level-sensitive cyclic behavior
  - ▣ In conditional branch (if or case)

# Clean Combinational Logic

```
module or4_behav (y, x_in);  
  parameter    word_length = 4;  
  output       y;  
  input        [word_length - 1: 0]  x_in;  
  reg          y;  
  integer      k;
```

```
  always @ x_in  
  begin: check_for_1  
    y = 0;  
    for (k = 0; k <= word_length -1; k = k+1)  
      if (x_in[k] == 1) begin  
        y = 1;  
        disable check_for_1;  
      end  
    end  
  end  
endmodule
```

Event Control Sensitive  
to x\_in[3:0]

 


# Output NOT Completely Specified by ALL Inputs

```
module or4_behav_latch (y, x_in);  
    parameter    word_length = 4;  
    output        y;  
    input    [word_length - 1: 0]  x_in;  
    reg          y;  
    integer      k;
```

Event Control Sensitive Only  
to  $x\_in[3:1]$
 
```
always @ (x_in[3:1])  
begin: check_for_1  
    y = 0;  
    for (k = 0; k <= word_length - 1; k = k+1)  
        if (x_in[k] == 1)  
            begin  
                y = 1;  
                disable check_for_1;  
            end  
    end  
endmodule
```





# Incompletely Specified Case

```

module mux_latch (y_out, sel_a, sel_b, data_a,
data_b);
  output      y_out;
  input       sel_a, sel_b, data_a, data_b;
  reg         y_out;

```

```

always @ ( sel_a or sel_b or data_a or data_b)

```

```

  case ({sel_a, sel_b})

```

```

    2'b10: y_out = data_a;

```

```

    2'b01: y_out = data_b;

```

```


  endcase

```


```

endmodule

```

 

(a) Generic parts

 


(b) Parts from cell library, i.e., after technology mapping
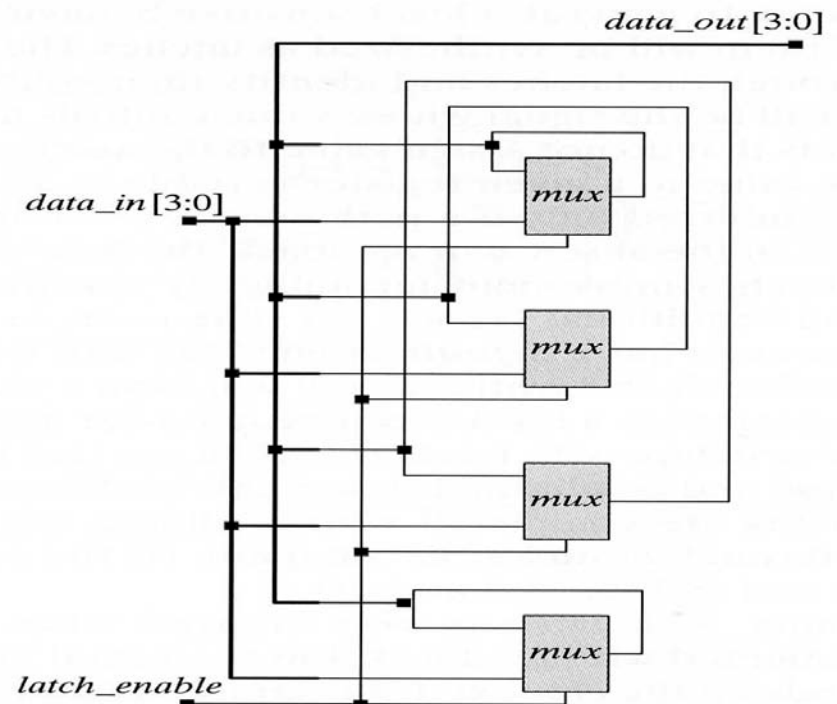
# MUXES vs LATCHES

- If a **case** statement has a **default assignment with feedback**
- Or If an **if** statement in a level-sensitive behavior **assign a value to itself** → a **mux**

```
module latch_if1(data_out, data_in,  
latch_enable);  
  output    [3: 0] data_out;  
  input     [3: 0] data_in;  
  input          latch_enable;  
  reg       [3: 0] data_out;  
  
  always @ (latch_enable or data_in)  
    if (latch_enable) data_out = data_in;  
    else data_out = data_out;  
endmodule
```




```

module latch_if2 (data_out, data_in,
latch_enable);
    output  [3: 0] data_out;
    input   [3: 0] data_in;
    input    latch_enable;
    reg     [3: 0] data_out;

    always @ (latch_enable or data_in)
        if (latch_enable) data_out = data_in;
        // Incompletely specified
endmodule

```

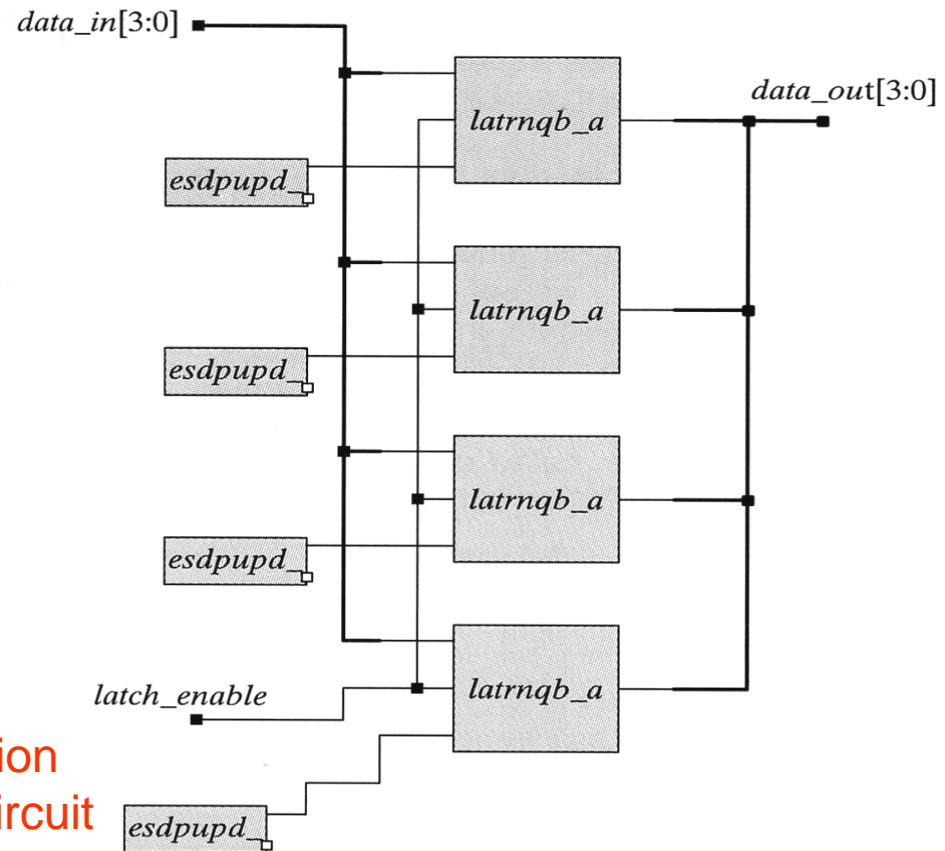A slight change in the behavioral description  
→ Change structure of the synthesized circuit



# A latch file

```
module sn54170 (data_out, datajn, wr_sel, rd_sel,
wr_enb, rd_enb);
```

```
output      [3:0] data_out;
```

```
input      wr_enb, rd_enb;
```

```
input      [1:0] wr_sel, rd_sel;
```

```
input      [3:0] datajn;
```

```
reg        [3:0] latched_data  [3:0];
```

```
always @ (wr_enb or wr_sel or datajn) begin
```

```
    if(!wr_enb)
```


```
        latched_data[wr_sel] = datajn;
```

```
    end
```

```
assign data_out = (rd_enb) ? 4'b1111 :
```

```
latched_data[rd_sel];
```

```
endmodule
```

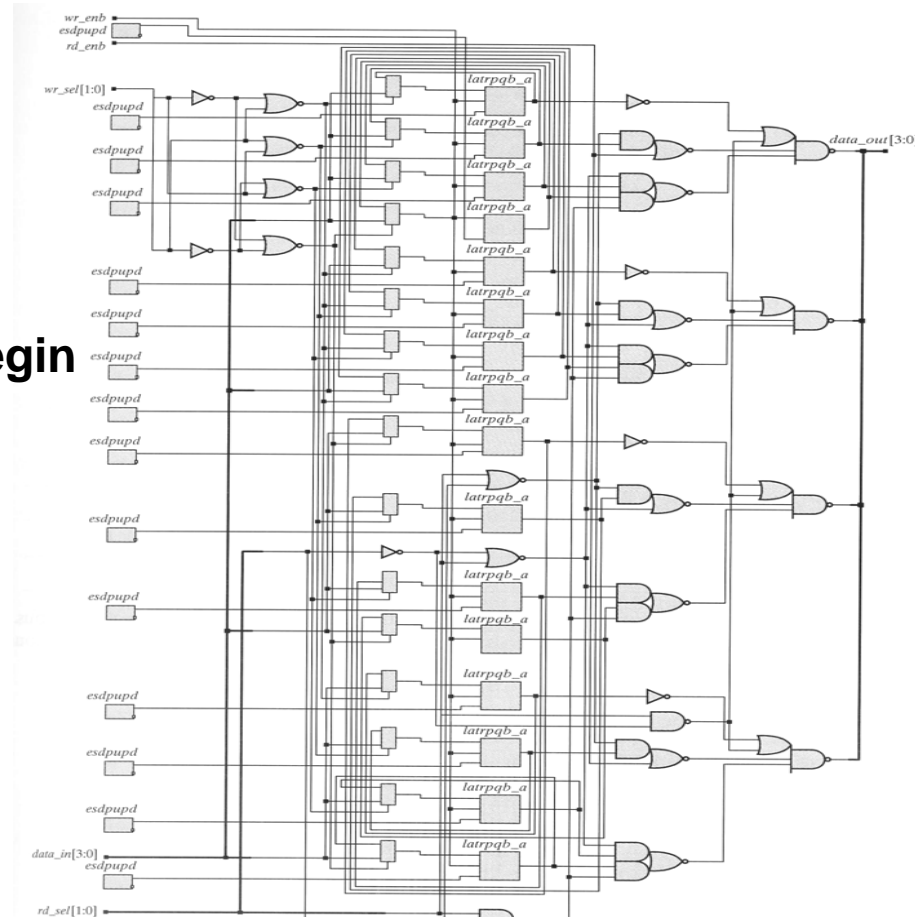

# Synthesis of Sequential Logic with Flip-Flops

13

- Flip-flops are synthesized only from **edge-sensitive cyclic behaviors**, but not every register variable that is assigned value in an edge-sensitive block is synthesized to a flip-flop.
- A register variable in an edge-sensitive block will be synthesized as a flip-flop if
  - ▣ it is **referenced outside the scope of the block**, or
  - ▣ it is **referenced within the block before it is assigned value**, or
  - ▣ it is **assigned value in only some of the branches of the activity within the block**.

# Synthesis of Sequential Logic with Flip-Flops

14

- For an incomplete conditional statement (i.e., an if ... else statement or a case statement), if the block is edge-sensitive, it will be synthesized to a logic that implements a “clock enable”
- If the event-control expression is sensitive to the edge of more than one signal, an if statement must be the first statement in the block.

# Referenced Outside the Scope of the Block

```
module empty_circuit (D_in, clk);  
input D_in;  
input clk;  
reg D_out;  
always @ (posedge clk) begin D_out <= D_in; end  
endmodule
```

D\_out is not referenced outside the scope → eliminate D\_out

```
module circuit_FF (D_out, D_in, clk);  
Output D_out;  
input D_in;  
input clk;  
reg D_out;  
always @ (posedge clk) begin D_out <= D_in; end  
endmodule
```

D\_out is referenced outside the scope → synthesized as a FF.

# Referenced Before Values Assigned

```
module swap_synch (set1, set2, clk, data_a, data_b);  
  output      data_a, data_b;  
  input       clk, set1, set2, swap;  
  reg        data_a, data_b;
```

```
  always @ (posedge clk)
```

```
  begin
```

```
    if (set1) begin data_a <= 1; data_b <= 0; end else
```

```
    if (set2) begin data_a <= 0; data_b <= 1; end else
```

```
    else
```

```
      begin
```


```
        data_b <= data_a;
```

```
        data_a <= data_b;
```

```
      end
```

```
    end
```

```
endmodule
```

 




# D Flip-Flop With Asynchronous Set

17

- When inferring a D flip-flop with an asynchronous set or reset, include edge expressions for the clock and the asynchronous signals in the sensitivity list of the always block.
 
```
module dff_async_set (DATA, CLK, SET, Q);  
  input DATA, CLK, SET;  
  output Q;  
  reg Q;  
  always @(posedge CLK or negedge SET)  
    if (~SET)  
      Q <= 1'b1;  
    else  
      Q <= DATA;  
endmodule
```




# D Flip-Flop With Synchronous Set

18

- When inferring a D flip-flop with an synchronous set or reset, include only the clock in the sensitivity list of the always block.
 
```
module dff_sync_set (DATA, CLK, SET, Q);  
  input DATA, CLK, SET;  
  output Q;  
  reg Q;  
  //synopsys sync_set_reset "SET"  
  always @(posedge CLK)  
    if (SET)  
      Q <= 1'b1;  
    else  
      Q <= DATA;  
endmodule
```




# D Flip-Flop With Syn. and Asyn. Load Controls

19

- D flip-flops can have asynchronous or synchronous controls.
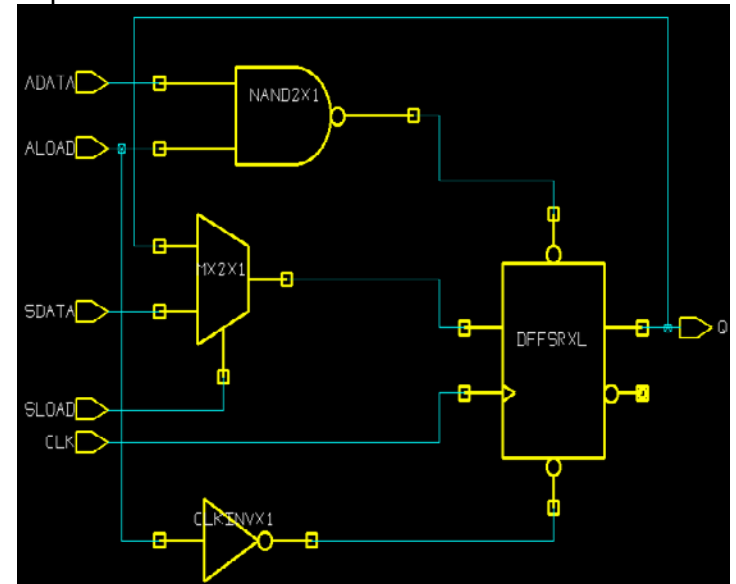
```
module dff_a_s_load (ALOAD, SLOAD, ADATA,
SDATA, CLK, Q);
input ALOAD, ADATA, SLOAD, SDATA, CLK;
output Q;
reg Q;
always @ (posedge CLK or posedge ALOAD)
    if (ALOAD)
        Q <= ADATA;
    else if (SLOAD)
        Q <= SDATA;
endmodule
```




# Multiple Flip-Flops With Asyn. and Syn. Controls

20

- If a signal is synchronous in one block but asynchronous in another block,
 
```
//synopsys sync_set_reset "RESET"  
always @(posedge CLK)  
begin : infer_sync  
  if (~RESET)  
    Q1 <= 1'b0;  
  else if (SLOAD)  
    Q1 <= DATA1; // note: else hold Q  
  end  
always @(posedge CLK or negedge RESET)  
begin: infer_async  
  if (~RESET)  
    Q2 <= 1'b0;  
  else if (SLOAD)  
    Q2 <= DATA2;  
end
```



# Limitations of D Flip-Flop Inference

21

- An if statement must occur at the top level of the always block.

```
always @(posedge clk or posedge reset)
begin
  q = d;
  if (reset)
    . . .
end
```

Error: The statements in this 'always' block are outside the scope of the synthesis policy (%s). Only an 'if' statement is allowed at the top level in this 'always' block. (ELAB-302)

# Writing Efficient Circuit Description

- Restructure a design that makes repeated use of several large components, to minimize the number of instantiations.
- In a design that needs some, but not all, of its variables or signals stored during operation, minimize the number of latches or flip-flops required.
- Consider collapsing hierarchy for more-efficient synthesis for small circuit, but use hierarchy for large circuit.

# Minimizing Registers (1 / 2)

- In an **always** block that is triggered by a clock edge, every variable that has a value assigned has its value held in a flip-flop.

```
always @(posedge clock) begin
    if (reset)
        count = 0; // reg [2:0] count;
    else
        count = count + 1;
        and_bits = & count;
        or_bits = | count;
        xor_bits = ^ count;
    end
endmodule
```

- Use six flip-flops; however, and\_bits, or\_bits, and xor\_bits depend solely on the value of count.

# Minimizing Registers (2/2)

- Assign the outputs from within an asynchronous **always** block to avoid implying extra registers

```
always @(posedge clock) begin
    //synchronous
    if (reset)
        count = 0;
    else
        count = count + 1;
end
always @(count) begin
    //asynchronous
    and_bits = & count;
    or_bits = | count;
    xor_bits = ^ count;
end
```



# Separating Sequential and combinational Ckts

- Make a separate *always* block within edge trigger (synchronous) and no edge trigger (asynchronous)

```
always @(posedge clk or negedge reset) // state vector flip-flops
(sequential)
    if (!reset)
        current_state = 0;
    else
        current_state = next_state;

always @(in1 or in2 or current_state)
// output and state vector decode
(combinationnal)
    case (current_state)
        0: begin
            next_state = 1;
            out = 1'b0;
            end
        1: begin
            next_state = 1'b2;
            out = in1;
            end
        2: .....
    endcase
```

# Why cannot synthesize?(1 / 2)

- Verilog code is not pure RTL code.

- Cannot use “#” delay command

Ex: always@(posedge clk) begin

**#20** a=c;

end

**# delay** cannot be  
synthesis to gate

- Cannot use initial block in your design.

Ex: module count(clk,c);

**initial** begin

c=0;

end

**Initial** block only can be  
used in testfixture

- Cannot use the same reg in different always blocks.

Ex: always@(posedge clk) begin

a=c;

end

always@(posedge clk or negedge reset) begin


a=d;

end

**One value cannot be driven  
by 2 conditions**

# Why cannot synthesize?(2/2)

- Avoid using “**task**” command.

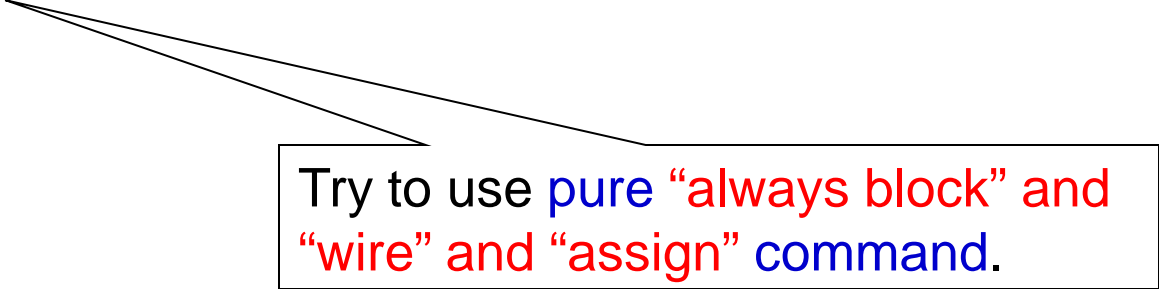

Try to use pure “**always block**” and “**wire**” and “**assign**” command.

- **Note:**

The warning message like “... cannot be synthesized” will **appear when reading a verilog code that cannot be synthesized in Synopsys**. So please carefully check the messages when warned during synthesis.

# Coding Guideline

Severity Levels Definition	
Mandatory 1 (M1)	Rules must be followed. If not, design must be fixed.
Mandatory 2 (M2)	Rules should be followed. If not, documentation must be provided.
Recommended (R)	Recommended deliverable items.

**Ref : Reuse Methodology Manual (RMM) Keating & Bricaud, 3<sup>rd</sup> ed., 2002.**

# Basic Coding Practices

29

## □ Naming convention

- Lower case for signals, variables, ports
- Upper case for constants (**define** directive)
- Meaningful names  
Ex: **ram\_addr** for RAM address, **sys\_bus** for system bus.
- Short but descriptive parameters (for synthesis)
- Prefix **clk** for clocks, prefix **rst** for reset.
- **\*\_x** for active low, e.g., **rst\_n**, **act\_b**.
- Use **[x:0]** rather than **[0:x]**
- Use **\*\_r** for output of a register, e.g., **count\_r**
- Use **\*\_z** for tristate signal

## □ Do not use HDL reserved words.

# Basic Coding Practices (cont.)

- State variables: **<name>.cs** for current state, **<name>.ns** for next state
- Use **informational header** for each source file:
  - Legal information (confidentiality, copyright, restriction, etc.), filename, author, date, version history, main contains.
- Use **concise but explanatory comments** where appropriately.
- Avoid multiple statements in one line.
- Use **indentation** to improve readability.
  - Use indentation of 2 spaces; do not use tab
- Port (core I/O) ordering
  - One port per line; a comment followed each port declaration
  - Follow the following order:
    - clocks, resets, enables, other control signals, data & Address lines

# Basic Coding Practices (cont.)

31

- Port mapping
  - ▣ Use explicit mapping
  - ▣ Use **named association** rather than positional association

Ex:

```
TagRam TagRam (  
  .Address    (PAddress[`INDEX]),  
  .TagIN      (PAddress[`TAG]),  
  .Tagout     (TagRAMTag[`TAG]),  
  .Write      (Write),  
  .Clk        (Clk)  
);
```

# Basic Coding Practices (cont.)

32

- Use functions wherever possible (for reusability and avoid repetition).
- Use **vector operations** (array) rather than loops for faster simulation.

Ex:

Poor:    `for (i = 1, i < k, i ++)`  
          `c_vec[i] = a_vec[i] ^ b_vec[i];`

Better: `c_vec = a_vec ^ b_vec;`



# Clocks & Resets

33

- Preferably use a single global clock and positive edge-triggered flip-flops only.
- **Avoid both positive and negative edge-triggered flip-flops.**
- Separate positive-edge and negative-edge triggered flip-flops into different modules — **make scan design easier.**
- Avoid clock buffers — **leave it to clock insertion tool.**
- Avoid gated clock — **to avoid false clock or glitch, and improve testability.**
- Avoid internally generated clocks — **for testability.**
- If internally generated clocks are necessary, separate it in a top-level module.
- Avoid internally generated resets.

# Coding for Synthesis

34

- Registers (flip-flops) are preferred.
- Latch should be avoided.
- Use design tools to check for latches.
- Poor coding may infer latches:
  - ▣ Missing **else** statement in **if-then-else** structures.
  - ▣ Missing assignments or conditions in **case** structures.
- To avoid the undesired inferred latches:
  - ▣ Assign default values at the beginning of a process.
  - ▣ Assign outputs for all input conditions.
  - ▣ Use default statements for case structures.
  - ▣ Always consider the else case in a if-then-else structure.
- If a latch must be used, well document it and prepare to make it testable via a mux.

# Coding for Synthesis (cont.)

35

- ❑ Avoid combinational loops.
- ❑ Specify complete sensitivity lists.
- ❑ Always use nonblocking assignments in **always @(posedge clk)** blocks.
- ❑ Use **case** instead of nested **if-then-else** statements.
- ❑ Separate FSM and non-FSM logic in different modules.
- ❑ Keep late-arriving signals with critical timing closest to the output of a module, e.g., earlier in if-then-else structures.
- ❑ Do not use delay constants in RTL code to be synthesized.

# Partitioning for Synthesis

36

- Partitioning can result in better synthesis results, faster compile and simulation time, and enable simpler synthesis strategy to meet timing requirement.
- Locate related combinational logic in a single module
- Separate modules that have different design goals.
- Avoid asynchronous design except reset.
- If asynchronous is required, put it in a separate module.
- Put relevant resources to be shared in the same module.

# Coding Style (1/2)

37

- **[M1] Use a separate line for each HDL statement**

```
// Use:  
    out1 = a1 & b1; // AND operation  
    out2 = a2 | b2; // OR operation  
// Do not use:  
    out1 = a1 & b1; out2 = a2 | b2;
```

- **[M1] Avoid expression in port connections**

```
foo u_foo ( .bad ((m & n) ^ ((p | q) > 4'hc)),  
           .good (good)); // expressions in port connections
```

- **[M1] Wire must be explicitly declared**

```
wire int_signal_a; // internal signal for block signal_a  
wire int_signal_b; // internal signal for block signal_b  
block u_block( .signal_a (int_signal_a), .signal_b (int_signal_b) );
```

# Coding Style (2/2)

38

## □ [M1] Operand size must match

```
wire [32:0] signal_a; // internal signal_a with 33 bit width
wire [7:0] signal_b; // internal signal_b with 8 bit width
// Do not use:
signal_x <= signal_a & signal_b;
signal_a <= 1;
// Use:
signal_a <= 33'h0_0000_0001;
```

## □ [R] Expression in condition should be 1- bit value

```
// Do not use:
if (bus)
    data_enable = 1; /* The signal data_enable is set to 1 whenever the
multi-bit condition bus has the known value other than 0 */
// Use:
if (bus > 0)
    data_enable = 1;
/* This is the condition represents in 1-bit value expression, which is
instinctively easier to understand and avoid confusion */
```

# Coding for Synthesis (1 / 3)

39

## □ **[M1] Use only synthesizable statement**

- NOT waveform statements (initial)
- NOT system task and function (\$display, \$monitor, ..)
- NOT wait statement and # delay statement
- NOT real, time, and event
- ONLY one clock per always sensitivity list
- ONLY loop with a static range

# Coding for Synthesis (2/3)

40

- [M2] NO full\_case and parallel\_case directive statements
- [M2] Avoid unexpected latch inference
- [M1] NO User-Defined-Primitive (UDP)
- [M1] All unused module inputs must be driven


Either by some other signal or by a fixed logic zero or one



# Coding for Synthesis (3/3)

41

- [M2] Avoid top-level glue logic

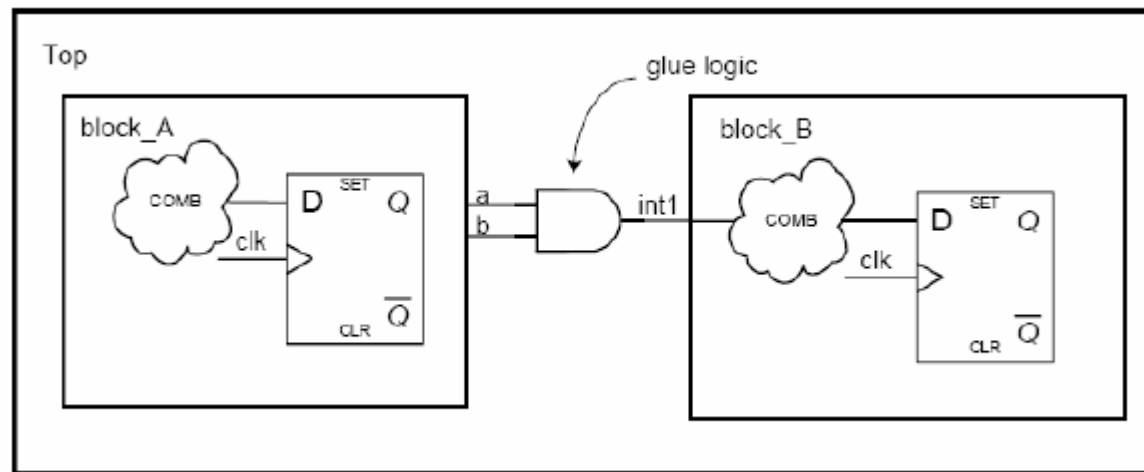

# Coding for Simulation

42

- **[M1] Use non-blocking assignments in sequential always block**
- **[M1] Use blocking assignments in combinational always block**
- **[M1] Avoid missing sensitivity lists in combinational always block**
- **[M1] Avoid redundant sensitivity lists**

The presence of a signal in the sensitivity list that is not used in the process may cause unneeded evaluations in simulation and result in longer simulation times.


- **[M1] Do not assign signals don't care (x) value**

If there exists x value in a control path, it may potentially cause the chain of unknown state for all related circuits in simulation. Furthermore, it is extremely possible cause the problem of pre-simulation and post-simulation mismatch.

# Design Style (1 / 2)

43
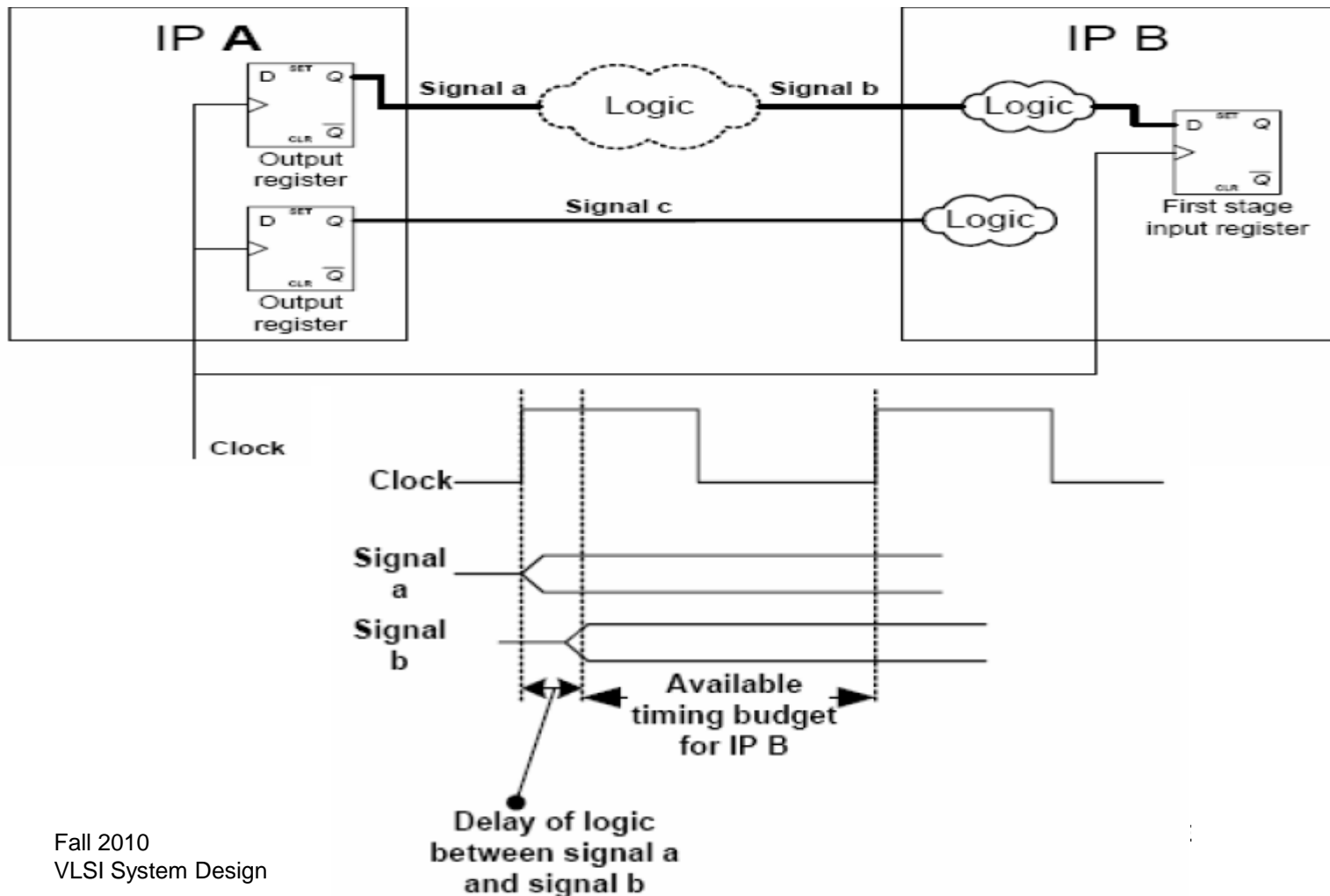
## □ [M2] Output signals must be registered



# Design Style (2/2)

44

- [R] Registers in an IP's interface should be clocked in a single edge of the same clock
- [M1] Clock strategy must be documented

